

# design ideas

Edited by Bill Travis and Anne Watson Swager

## Voltage reference sets current limit

Joe Engle, Burr-Brown Corp, Tucson, AZ

Power op amps have a real need for active output-current limiting. Most power-amplifier designs rely on the voltage drop across a user-supplied sense resistor to turn on an internal transistor. This method has several drawbacks, notably, an inability to change the current-limit point under program control. The current-limit circuit in **Figure 1** allows you to establish the setpoint by applying a voltage to one of the amplifier's pins. With this design, it is possible to set the current-limit point with the output of a DAC, possibly under the control of an embedded  $\mu$ C.

The OPA547 is a true op amp; thus, it does not need a connection to power ground. The current-limit-setting voltage for this IC uses the negative supply as a reference. For single-supply applications in which the negative supply is ground, this referencing technique presents no problem, but for circuits that use a negative supply below ground potential, you need a different technique. The circuit in **Figure 1** shifts the reference potential for the control signal from ground to the negative supply. For simplicity, **Figure 1** shows the OPA547 as an inverting amplifier, but you

can use any op-amp application circuit. The circuit uses an OPA340 for reference shifting because it is capable of rail-to-rail operation on both input and output.

To understand the operation of the reference-shifting circuit, first recognize that the  $R_3$ -to- $R_4$  voltage divider sets the voltage at  $IC_2$ 's Pin 3. Thus, the intermediate voltage ( $V_i$ ), as measured from the negative supply, is given by

$$V_i = V_C \frac{R_4}{R_3 + R_4} \quad (1)$$


To find the voltage at  $IC_2$ 's pin 2, note that the current through  $R_3$  equals the sum of the currents in  $R_1$  and  $R_5$ , leading to the following expression:

$$\frac{V_1 - V_i}{R_2} = \frac{V_i - V_O}{R_1} + \frac{V_i}{R_5} \quad (2)$$

As long as op amp  $IC_2$  operates in the linear region, the voltage at Pin 2 equals the voltage at Pin 3, so the value of  $V_i$  in each of the expressions is equal. When you substitute the first term into the sec-

**Figure 1**

I (mA)	$V_C$
0	4.75
100	4.12
375	2.38
500	1.59
750	0.01

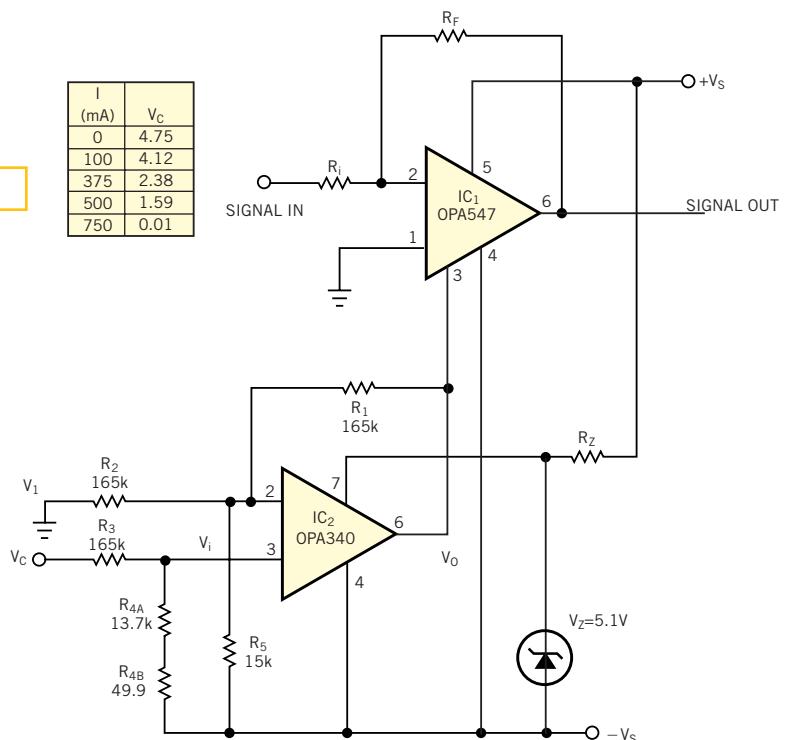

Voltage reference sets current limit .....	129
Accelerometer output gives temperature info.....	130
Voltage comparator forms pulse demodulator .....	132
Watchdog-reset catcher aids embedded-system debugging .....	132
Easily display bit-map images on small-graphic LCDs .....	134
CMOS inverter VCO tunes octave to UHF.....	138
Pushbutton or logic controls nonvolatile DAC .....	140

You can use a difference amplifier with wide common-mode range to control a power amplifier's current limit.

ond, set  $R_1$  equal to  $R_2$ , and combine terms, the resulting expression is

$$V_O = V_C \left( \frac{R_1}{R_5} + \frac{R_4}{R_3 + R_4} \right) V_1 \quad (3)$$

In **Figure 1**,  $V_1$  connects to ground, and you obtain unity gain by setting the coefficient of  $V_C$  in **Equation 3** to 1. If you expand and combine terms, the expression becomes

$$1 + \frac{R_1}{R_5} = \frac{R_3}{R_4} \quad (4)$$

To change the scalar relationship between the controlling voltage applied to the power op amp, simply set the coefficient term to the desired value and solve **Equation 3**. To determine the resistor values, consider the worst-case common-mode voltage that  $IC_2$  can encounter. OPA547 allows a maximum supply differential of 60V. In an extreme case, the positive supply of the OPA547 connects to ground and the current-limit set voltage is +5V. **Equation 1** becomes

$$5 = 65 \frac{R_4}{R_3 + R_4}, \quad (5)$$

which reduces to  $R_3 = 12R_4$ . Applying this ratio to **Equation 4** and setting  $R_3$  equal to  $R_1$  produces  $R_1 = 11R_5$ . Selecting from a list of standard 1% resistor values yields the values in **Figure 1**. Note that the stage operates with a common-mode voltage that equals the negative supply. Errors in the resistor values can produce a significant offset shift. With this circuit, it is possible to set the current limit of the power op amp to a known, repeatable value under program control. (DI #2270).

To Vote For This Design,  
Circle No. 406