


# Sense automobile high-side current with discrete components

Larry Beaty, Beatys Mills, Comer, Georgia

 This Design Idea came about as a result of my not having access to those wonderful new ICs that sense current. I needed a discrete circuit that I could build easily but that would still be as accurate as the new ICs. This circuit seems to do the job.

$Q_2$  is the first current amplifier; it has a gain of 6.2 (Figure 1).  $Q_1$  is the temperature-compensation amplifier controlled by  $IC_{1B}$ , which keeps the  $Q_1$  collector voltage constant no matter what the temperature does to the circuit. The reference voltage for the circuit is the 5V system supply. The voltages noted on the schematic are as built.

$IC_{1A}$  differentially amplifies the  $Q_1$  and  $Q_2$  collector voltages. The op amp has a gain of 4.9.

$R_3$  comprises two surface-mount power resistors, stacked one atop the other. The circuit has a range of 25A in for 5V out.

This setup works nicely with an analog input to the microprocessor.

The two zener diodes protect the circuit from the automobile electrical system. Such systems have been known to spike to  $-90V$ .

If you want to get critical, match  $R_6$  and  $R_7$ ; more critical again, also match  $R_1$  and  $R_4$ . I didn't do this step, and the mismatch did not seem to affect the operation. All resistors except  $R_3$  are 1% 0805 SMT.

Observe sufficient copper weight and width on your PCB traces for maximum current-carrying capacity, and be sure to use Kelvin connections to  $R_3$ . This circuit ran slightly warm to the touch at 25A. **EDN**

