

**UNITRODE  
APPLICATION NOTE**

# A 25 WATT OFF-LINE FLYBACK SWITCHING REGULATOR

## Introduction

This Application Note describes a low cost (less than \$10.00) switching power supply for applications requiring multiple output voltages, e.g. personal computers, instruments, etc. The discontinuous mode flyback regulator used in this application provides good voltage tracking between outputs, which allows the use of primary side voltage sensing. This sensing technique reduces costs by eliminating the need for an isolated secondary feedback loop.

The low cost, (8 pin) UC3844 current mode control chip employed in this power supply provides performance advantages such as:

- 1) Fast transient response
- 2) Pulse by pulse current limiting
- 3) Stable operation

To simplify drive circuit requirements, a TO-220 power MOSFET (UFN833) is utilized for the power switch. This switch is driven directly from the output of the control chip.

## Power Supply Specifications

1. Input voltage: 95VAC to 130VAC (50Hz/60Hz)
2. Output voltage:
  - A. +5V,  $\pm 5\%$ : 1A to 4A load  
Ripple voltage: 50mV P-P Max.
  - B. +12V,  $\pm 3\%$ : 0.1A to 0.3A load  
Ripple voltage: 100mV P-P Max.
  - C. -12V,  $\pm 3\%$ : 0.1A to 0.3A load  
Ripple voltage: 100mV P-P Max.
3. Line Isolation: 3750 Volts
4. Switching Frequency: 40KHz
5. Efficiency @ Full Load: 70%

## Basic Circuit Operation

The 117VAC input line voltage is rectified and smoothed to provide DC operating voltage for the circuit. When power is initially applied to the circuit, capacitor C2 charges through R2. When the voltage


across C2 reaches a level of 16V the output of IC1 is enabled, turning on power MOSFET Q1. During the on time of Q1, energy is stored in the air gap of transformer (inductor) T1. At this time the polarity of the output windings is such that all output rectifiers are reverse biased and no energy is transferred. Primary current is sensed by a resistor, R10, and compared to a fixed 1 volt reference inside IC1. When this level is reached, Q1 is turned off and the polarity of all transformer windings reverses, forward biasing the output rectifiers. All the energy stored is now transferred to the output capacitors. Many cycles of this store/release action are needed to charge the outputs to their respective voltages. Note that C2 must have enough energy stored initially to keep the control circuitry operating until C4 is charged to a level of approximately 13V. The voltage across C4 is fed through a voltage divider to the error amplifier (pin 2) and compared to an internal 2.5V reference.

Energy stored in the leakage inductance of T1 causes a voltage spike which will be added to the normal reset voltage across T1 when Q1 turns off. The clamp consisting of D4, C9 and R12 limits this voltage excursion from exceeding the BVDS rating of Q1. In addition, a turn-off snubber made up of D5, C8 and R11 keeps power dissipation in Q1 low by delaying the voltage rise until drain current has decreased from its peak value. This snubber also damps out any ringing which may occur due to parasitics.

Less than 3.5% line and load regulation is achieved by loading the output of the control winding, Nc, with R9. This resistor dissipates the leakage energy associated with this winding. Note that R9 must be isolated from R2 with diode D2, otherwise C2 could not charge to the 16V necessary for initial start-up.


A small filter inductor in the 5V secondary is added to reduce output ripple voltage to less than 50mV. This inductor also attenuates any high frequency noise.

### 25W OFF-LINE FLYBACK REGULATOR

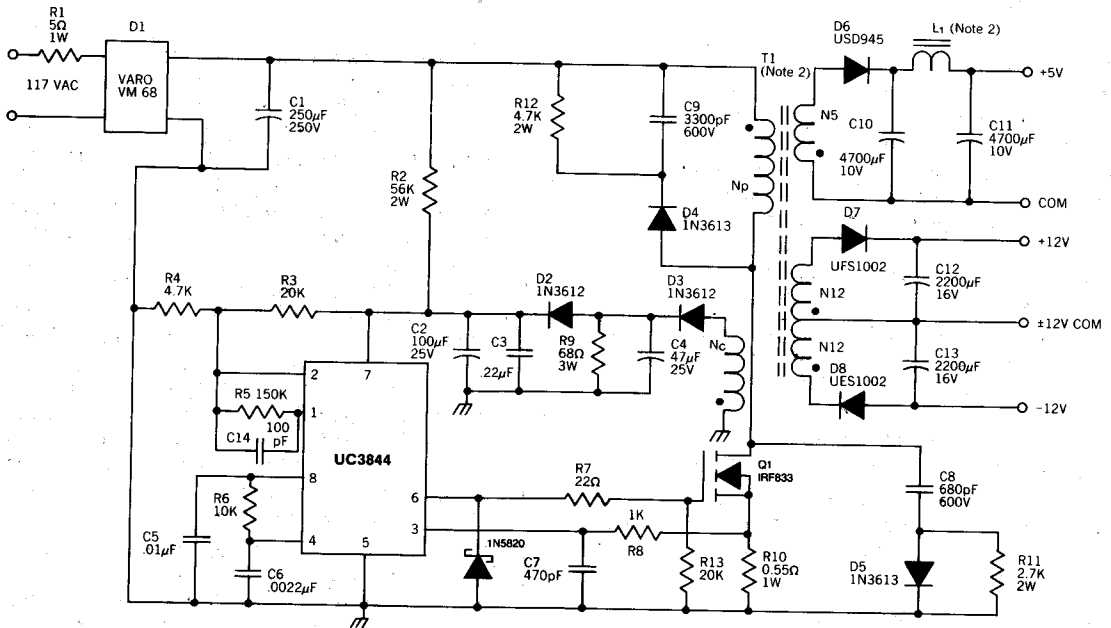

- Notes: 1. All resistors are 1/4 watt unless noted  
 2. See Appendix for construction details

### BLOCK DIAGRAM

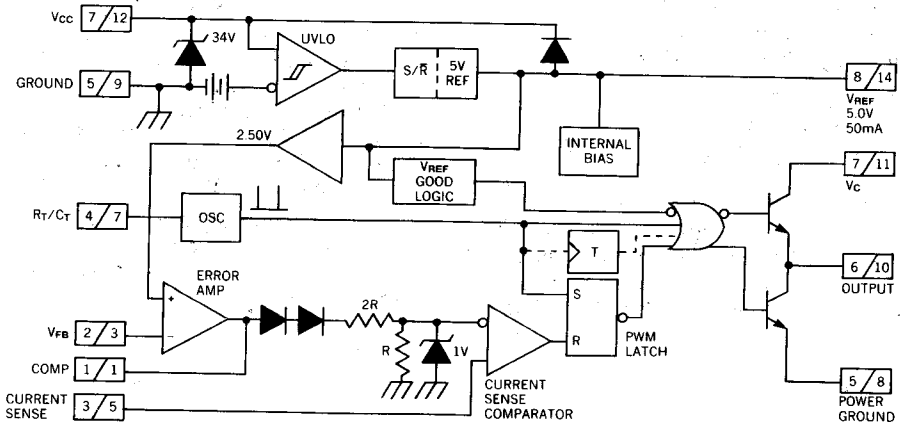


- Note: 1. A/B A = DIL-8 Pin Number, B = SO-14 Pin Number.  
 2. Toggle flip flop used only in 1844 and 1845.

### UC3842/3/4/5 CURRENT MODE PWM CONTROLLER


# TYPICAL SWITCHING WAVEFORMS

$T_{on}$  — Drive waveforms

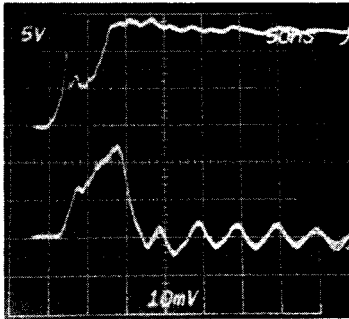


Upper trace:  $Q_1$  — Gate to source voltage  
Lower trace:  $Q_1$  — Gate current

$T_{off}$  — Drive waveforms

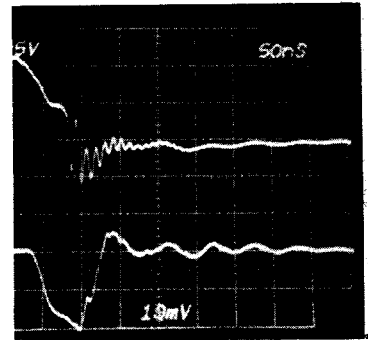


Upper trace:  $Q_1$  — Gate to source voltage  
Lower trace:  $Q_1$  — Gate current

5V/DIV  
200mA/DIV

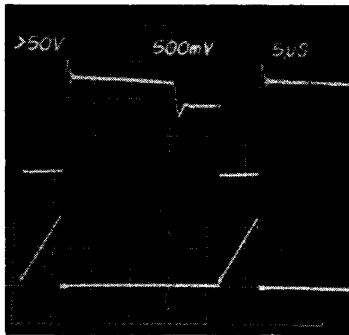

Upper trace:  $Q_1$  — Drain to source voltage  
Lower trace: Primary current —  $I_D$

100V/DIV  
5A/DIV  
50mV/DIV

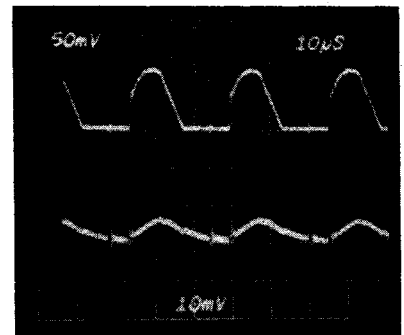

Upper trace: +5V charging current  
Lower trace: +5V output ripple voltage

## PERFORMANCE DATA

CONDITIONS		5V out	12V out	- 12V out
<b>Low Line (95VAC)</b>				
± 12 @ 100mA	+5V @ 1.0A	5.211	12.05	- 12.01
	4.0A	4.854	12.19	- 12.14
± 12 @ 300mA	+5V @ 1.0A	5.199	11.73	- 11.69
	4.0A	4.950	11.68	- 11.63
<b>Nominal Line (120VAC)</b>				
± 12 @ 100mA	+5V @ 1.0A	5.220	12.07	- 12.03
	4.0A	4.875	12.23	- 12.18
± 12 @ 300mA	+5V @ 1.0A	5.208	11.73	- 11.68
	4.0A	4.906	11.67	- 11.62
<b>High Line (130VAC)</b>				
± 12 @ 100mA	+5V @ 1.0A	5.207	12.06	- 12.02
	4.0A	4.855	12.21	- 12.15
± 12V @ 300mA	+5V @ 1.0A	5.200	11.71	- 11.67
	4.0A	4.902	11.66	11.61
<b>Overall Line and Load Regulation</b>		±3.5%	±2.3%	±2.4%

## PARTS LIST

<b>IC's</b>	<b>CAPACITORS</b>	C10, C11	4700 $\mu$ F, 10V	R7	22 $\Omega$	
IC1 UC3844	C1	250 $\mu$ F, 250V	C12, C13	2200 $\mu$ F, 16V	R8	1K
<b>POWER MOSFET</b>	C2	100 $\mu$ F, 25V	C14	100pF, 25V	R9	68 $\Omega$ , 3W
Q1 UFN833	C3	0.22 $\mu$ F, 25V	<b>RESISTORS</b>	R10	0.55 $\Omega$ , 1W	
<b>RECTIFIERS</b>	C4	47 $\mu$ F, 25V	R1	5 $\Omega$ , 1W	R11	2.7K, 2W
D1 VM68 varo	C5	.01 $\mu$ F, 25V	R2	56K, 2W	R12	4.7K, 2W
D2, D3 1N3612	C6	.0047 $\mu$ F, 25V	R3	20K	R13	20K
D4, D5 1N3613	C7	470pF, 25V	R4	4.7K	<b>MAGNETICS</b>	
D6 USD945	C8	680pF, 600V	R5	150K	T <sub>1</sub>	see appendix
D7, D8 UES1002	C9	3300pF, 600V	R6	10K	L <sub>1</sub>	see appendix


## APPENDIX

### POWER TRANSFORMER—T1

Core: Ferroxcube EC-35/3C8  
 Gap: 10 mil in each outer leg

*NOTE: For reduced EMI put gap in center leg only.  
 Use 20 mil.*

Ferroxcube  
 EC-35/3C8

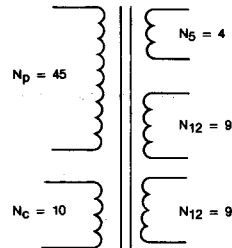


### TRANSFORMER CONSTRUCTION

Control Winding  
 N = 10, AWG 30  
 2 in parallel

+5V out, N = 4, AWG 26,  
 6 in parallel

2 layers 3M mylar tape

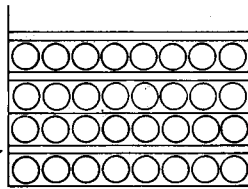


Bobbin—35PCB1

2 layers, 3M mylar tape

±12V windings N = 9, AWG30  
 2 wires in parallel, bifilar wound

Primary N = 45, AWG 26

### 5V OUTPUT INDUCTOR

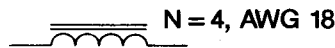

Ferroxcube  
 204 T 250 — 3C8 (toroid)