

# R.F. Coil

**No more hit-or-miss coil**

**W**HILE there's nothing wrong with the time-honored cut-and-try technique of winding coils for a receiver or transmitter, you can save yourself a lot of time and trouble by building this simple "R.F. Coil Frequency-Finder" for use with an external signal source such as an r.f. signal generator, a VFO, or a grid dipper.

The design of the unit is straightforward. The unknown coil is connected in parallel with  $C2$ , a midget 140- $\mu\text{pf}$ . variable capacitor, through  $J2$  and  $J3$ . The only power required is the r.f. furnished by the signal source through  $J1-C1$ . When the coil and  $C2$  resonate with the external r.f. source, energy is absorbed by the circuit and rectified by  $D1$ , giving a reading on the 50- or 100- $\mu\text{a}$ . meter,  $M1$ .


**Construction.** Cut a hole for  $M1$  near one end of the 2 $\frac{1}{2}$ " x 2 $\frac{1}{2}$ " x 4" Minibox.

Drill a hole to mount  $C2$  close to the other end of the box. Locate holes for the coil jacks,  $J2$  and  $J3$ , in the end of the box near  $C2$ . Terminal  $J1$  is mounted at the opposite end near the meter. Both  $J1$  and  $J2$  must be insulated from the metal box. Wiring is done point-to-point, keeping leads as short as possible; use a heat sink when soldering  $D1$ .

Although a 100- $\mu\text{a}$ . meter was used in the author's model, a 50- $\mu\text{a}$ . movement will give better sensitivity (although possibly at greater cost). In any case, a miniature meter of the relatively inexpensive imported variety should prove perfectly satisfactory.

Install a knob with a pointer on  $C2$ 's shaft, and calibrate  $C2$ , marking the minimum point ( $C2$  fully open) 10  $\mu\text{pf}$ . and the maximum point 150  $\mu\text{pf}$ . ( $C2$  fully closed). From these two points, estimate the 75 and 100  $\mu\text{pf}$ . points

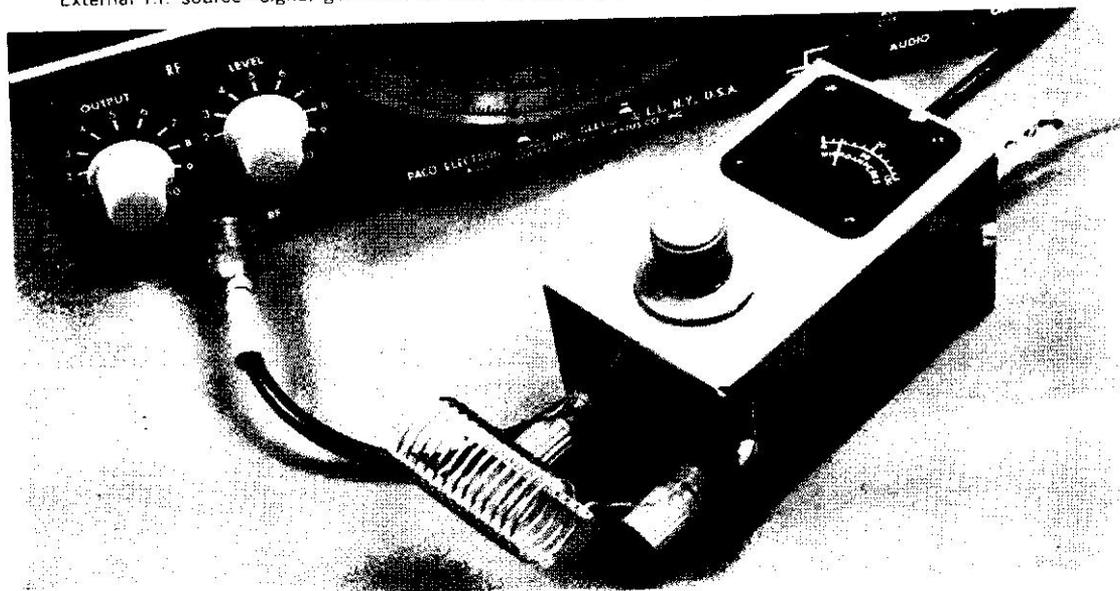External r.f. source—signal generator or VFO—is the only power required to operate the unit.



# Frequency-Finder

winding—all it takes is a meter, a few parts, and r.f. source

By LEON A. WORTMAN

and mark them on the panel. Decals, if available, will make a professional-looking scale. The markings (slightly greater than  $C2$ 's maximum and minimum capacities to compensate for the unit's internal capacity) will be only roughly accurate, but quite adequate in this application.

**Operation.** To use the Frequency-Finder with an r.f. generator, simply connect the center conductor of the output cable to  $J1$ , leaving the shield unconnected. Connect the unknown coil to  $J2$ - $J3$ , keeping leads as short as possible. If the coil is to be used with a capacitor of any type, set  $C2$  to that value; otherwise, at minimum.

Sweep across the desired frequency range with the r.f. signal generator until you find the resonant point indicated by a maximum reading on  $M1$ . The resonant frequency of the coil and  $C2$  can then


be read directly on the dial of the r.f. generator. Keep the output low, consistent with a readable indication on  $M1$ . A VFO can be used in the same manner. If the r.f. source is poorly calibrated, you can double-check by tuning its signal in on an accurate receiver.

To use the Frequency-Finder with a grid-dip oscillator, plug the appropriate coil into the dipper, set it in the oscillating mode, and bring it to within a few inches of the unknown coil. Adjust the tuning dial of the grid dipper for peak indication on  $M1$ . Read the resonant frequency from the dial of the grid dipper, ignoring, for this test, the dipper's own meter and sensitivity control.


**Other Uses.** Another method of using the Frequency-Finder is to set the r.f. source at a predetermined frequency, and adjust  $C2$  to determine how much capacitance is required to make the unknown coil resonate.

The value of a small capacitor can be estimated with the unit. Connect a coil to  $J2$ - $J3$ , set  $C2$  at 150  $\mu\text{p.f.}$ , and tune the r.f. source for maximum indication. Connect the unknown capacitor in parallel with the coil at  $J2$ - $J3$ , and reset  $C2$  for maximum indication. The value of the unknown capacitor is approximately equal to the maximum value of  $C2$  (150  $\mu\text{p.f.}$ ) minus the new setting of  $C2$  that restores  $M1$  to maximum reading.

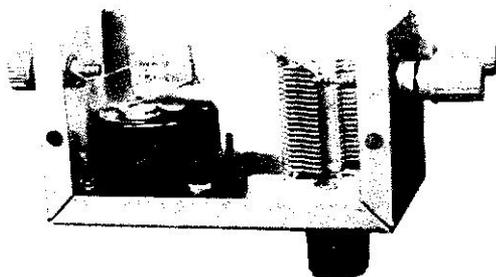Coils are easy to add to, or subtract from, if you use the Frequency-Finder first—try it.



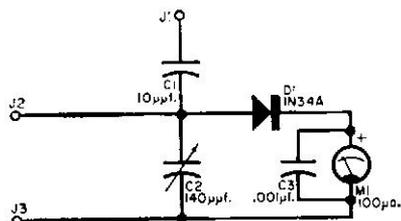Frequency-Finder is mounted in small Minibox; all wiring is done point-to-point to keep leads short.



## PARTS LIST


- $C1$  10  $\mu\text{p.f.}$  mica or ceramic capacitor
- $C2$  140  $\mu\text{p.f.}$  midget variable capacitor
- $C3$  100 p.f. ceramic disc capacitor
- $D1$  1N34A diode or equivalent
- $J1, J2, J3$  Insulated binding posts or jacks
- $M1$  50 or 100  $\mu\text{a. d.c.}$  microammeter
- 1-21," x 21," x 4" aluminum box
- 1 Knob with pointer

## INDUCTANCE MEASURING

How about an Inductance Measuring circuit? Say  $1\mu\text{H}$  to  $100\text{mH}$ .

G. C. Goode, Kelowna BC

*Here's how to measure inductance:*

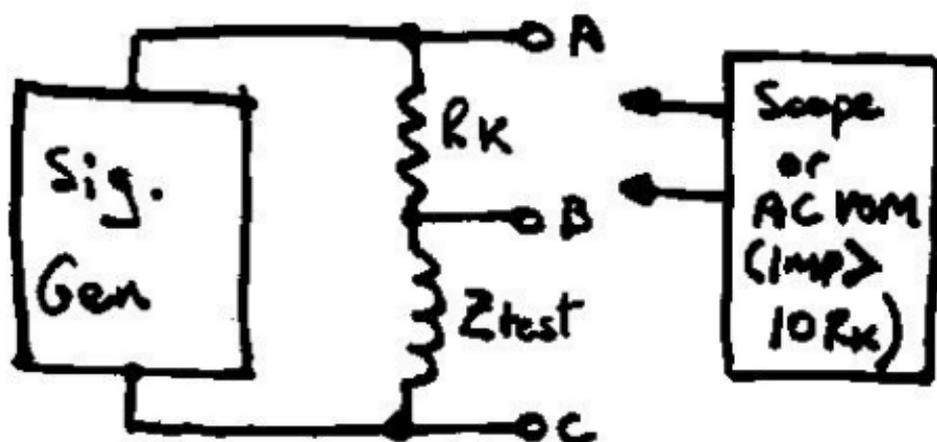

*Set the signal generator to some frequency, keep trying new values of  $R_k$  until voltage between B and C equals voltage between A and B. If R has to be very large, then reduce frequency, if it has to be very small then increase frequency.*

*Now with the two voltages equal,  $Z_{\text{test}} = R_k$  (at the set frequency). Since  $L = Z/6.28f$  and we know  $Z = R$  thus  $L = R/6.28f$ .*

*Eg. Sig. Gen.  $f = 10\text{ kHz}$  and  $R_k = 1\text{ k}$  to make the two voltages equal. Thus  $L = 1\text{ k}/(6.28 \times 10\text{ k}) = 16\text{ mH}$ .*