



BY LAWRENCE R. LAFLER

---

# A Low-Cost Emergency Broadcast System Monitor

---

Add-on circuit monitors the output of a broadcast receiver and sounds an alarm when an EBS warning signal is received

**T**HE National Weather Service and the Civil Defense Agency, in conjunction with local broadcasters and other authorities, maintain an emergency warning system to alert the public in case of impending natural disaster or national defense emergency. This system consists of a network of AM and FM radio stations that will interrupt their normal programs to broadcast an emergency bulletin immediately after an official severe weather or Civil Defense warning is issued. You have probably heard tests of this emergency broadcast system (EBS) on local radio stations. During such tests, and in the event of an actual alert, participating stations broadcast a special two-tone signal used to activate warning devices at other radio stations and at regional Civil Defense offices.

For less than \$25.00, you can build a circuit that will respond to the EBS alerting signal. This project receives signals from the earphone jack of a standard broadcast receiver and, in response

## emergency broadcast

to the special EBS tones, actuates a Son-alert or similar audible alarm or a relay. For around-the-clock protection, the EBS Monitor and the radio to which it is connected can be left activated continuously. If an emergency occurs, the alarm could save your life.

**How it Works.** The EBS alert signal consists of simultaneous tones at 853 Hz and 960 Hz broadcast for 22.5 seconds. This unlikely combination of frequencies and its long duration make it easy to distinguish the warning signal from speech and music. (Its waveform is shown in Fig. 1.)

Commercial EBS alerting devices employ a separate tone decoder for each of the two audio frequencies and a time-delay circuit that triggers an alarm only when the two frequencies are present for 15 seconds or more. This is an expensive approach requiring a large battery power source. To minimize cost and battery drain without sacrificing performance, this project employs a single CMOS phase-locked loop (PLL) to detect the presence of both frequencies. Three other CMOS integrated circuits perform most of the remaining functions. The circuit, which is shown schematically in


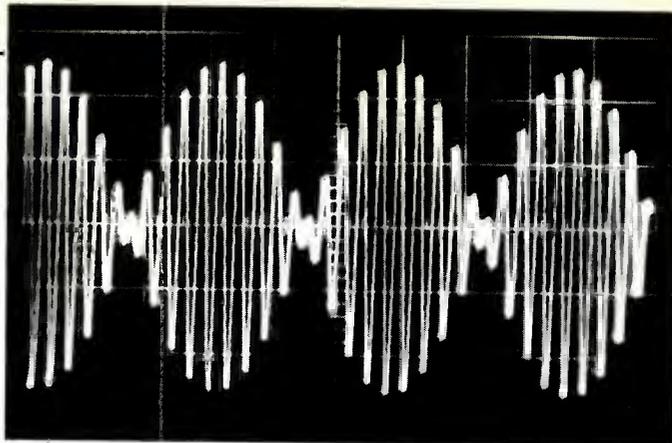


Fig. 1. Oscilloscope photo of the alert signal of the Emergency Broadcast System. It consists of two tones at 853 Hz and 960 Hz broadcast for 22.5 seconds.

Fig. 2, is such an energy miser that it will operate in its listening mode for more than one year on a single 9-volt transistor battery.

The one PLL is able to detect the two discrete audio tones by responding to the 107-Hz difference between their two frequencies. This 107-Hz difference tone can be separated from the rest of the alert signal by rectifying and filtering the signal. Diode *D3*, capacitors *C1* and *C2*, resistors *R2* and *R4*, and potentiometer *R20* perform this function.

Transistor *Q1* amplifies the 107-Hz difference signal and, with the help of inverter *IC3A*, converts it to a square wave that is then applied to the input (pin 14) of *IC4*, the phase-locked loop. The loop acts as a frequency-to-voltage converter that can be programmed to respond to a narrow band of frequencies called the *lock range*. Over this lock range, the output (pin 9) of the phase-locked loop will be a voltage that increases as the frequency of the input signal increases. For an input frequency

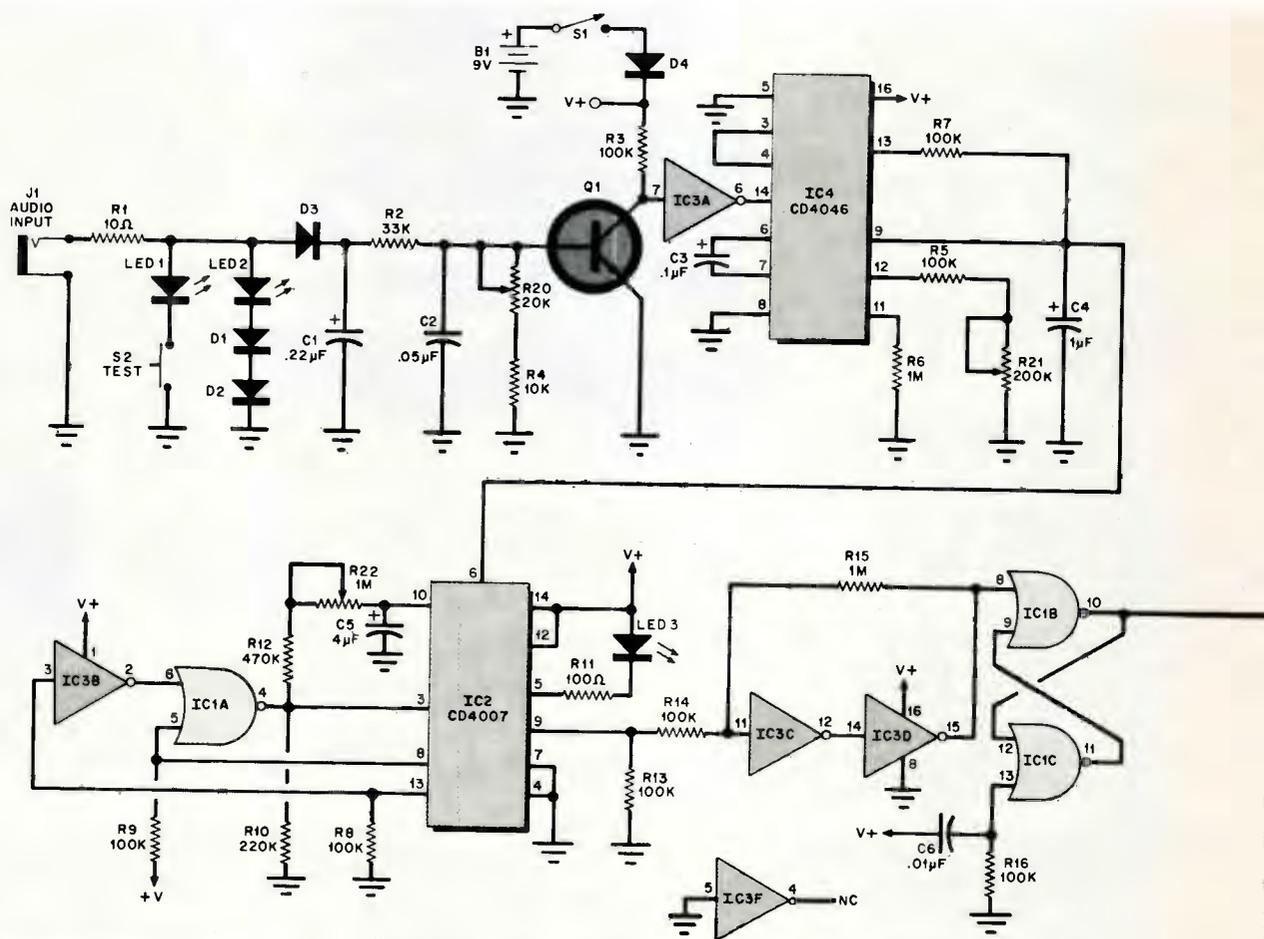




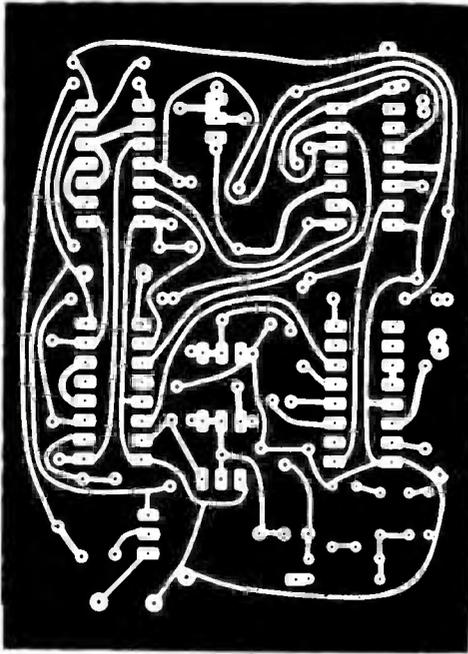


Fig. 3. Actual-size etching and drilling guide for a suitable printed circuit board.

Fig. 4. Component layout for the monitor's printed circuit board is shown below.

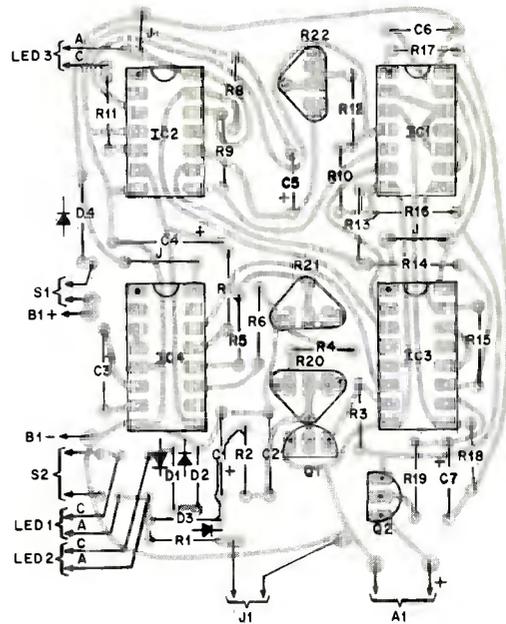

er than soldering them directly to the board. This makes replacement of defective ICs infinitely easier and eliminates the possibility of damaging them during soldering. Be sure to observe polarities and pin basings when you mount the diodes, transistors, LEDs, ICs, and electrolytic capacitors.

The LEDs should be mounted off the board so that they can project through the front panel of the enclosure that is employed to house the project. The switches should also be mounted on the front panel. Connect the LEDs and switches to the pc board using flexible hookup wire. Input jack *J1* should be mounted on the rear of the enclosure and connected to the board using two-conductor cable. Fasten a retaining clip for the 9-volt battery to the enclosure and connect suitably long leads from the appropriate foil pads to a 9-volt battery clip. Then install the battery and snap the connecting clip in place. Finally, prepare a two-conductor patch cord of convenient length terminated with miniature phone plugs at each end.

**Alignment.** There are only three adjustments that must be made before the EBS Monitor is ready for service. Potentiometer *R20* must be adjusted so that, when the audio output of the broadcast receiver is at the proper level and the EBS signal is present, a 107-Hz square wave will be applied to the input of the

PLL. Potentiometer *R21* must be adjusted so that the lock range of the PLL is centered around 107 Hz. Third, potentiometer *R22* needs to be set so that, once *LED3* begins to glow, there will be a 12- to 18-second delay before the alarm sounds. The easiest way to make these adjustments is to first make a recording of the EBS alert signal when a local radio station is conducting an EBS test. Use a high-quality cassette or open-reel tape recorder that has an earphone or line-level output jack. After you have recorded the two-tone signal, patch the output of the recorder to the project's input jack and proceed as follows.

First, connect a voltmeter between pin 14 of *IC4* and the circuit ground. Then close switch *S1* and play back the EBS alert signal. (Rewind and repeat this step as necessary so that the tone is present during all of the remaining steps.) Hold switch *S2* closed and adjust the recorder's output level until *LED1* glows but *LED2* remains dark. Vary potentiometer *R20* until the voltmeter reads 3 to 5 volts dc. Vary potentiometer *R21* until *LED3* glows most or all of the time that the tone is present. Vary potentiometer *R22* until the delay between the application of the tone and the activation of the audible alarm is between 12 and 18 seconds. The delay can be reduced by moving the wiper of *R22* toward capacitor *C5* as viewed from the top of the board.

**Use.** Your EBS monitor is ready for service. Apply power to both the project and the broadcast receiver with which it will be used. Tune in a local radio station that participates in the Emergency Broadcast Service, has a strong signal in your area, and broadcasts 24 hours a day. If possible, choose an FM station, because static interference during an electrical storm will be less severe and the operation of the Monitor will be more reliable.

Patch the output of the receiver to input jack *J1* and, if necessary, adjust the output level so that *LED1* flickers in step with the demodulated signal when *S2* is depressed but that *LED2* remains dark. When the project is operating in its listening mode, *LED3* should flicker on occasionally. As long as it flashes brightly, the battery is in good condition. As the battery becomes weaker and needs replacing, *LED3* will diminish in brightness.

Take advantage of the broadcaster's EBS tests to check the circuit periodically for proper operation. These tests are never conducted at night, so you will not be disturbed by false alarms if you leave the project in its listening mode while you sleep. When the alarm sounds, remove power from the project and disconnect the patch cord from the output jack of your broadcast receiver. You will then be able to hear the emergency message that follows. ♦