



## BY HOWARD JOHNSON, PhD

## Two-way street

uppose that I gave you a highway-traffic monitor that reports total traffic density on a section of roadway but does not provide separate figures for eastbound and westbound traffic. Obviously, this sensor reveals only part of the total traffic picture. Transmission lines, like streets, support traffic in two directions. A voltage probe connected to a transmission line acts much like a traffic-density sensor. It shows

an aggregate-voltage waveform but doesn't say which way the waveform is moving.

For example, Figure 1 shows the composite voltage (pink) at capacitor  $C_3$  (Reference 1). The waveform shows a 200-psec step followed by a negative bump at B. To decipher the cause of that bump, include in your schematic a virtual (nonphysical)  $0\Omega$  resistor,  $R_0$ . Set all the parasitics associated with that component to their minimum values

## Transmission lines, like streets, support traffic in two directions.

Export from your simulator both the voltage,  $v_o$ , at  $R_o$  and the current,  $i_o$ , flowing through  $R_o$ . Then, use the equations in **Figure 1** to compute both forward- and reverse-moving waveforms,  $v_F$  and  $v_R$ , respectively.

minimum values. 400 pSEC COMPOSITE VOLTAGE AT Ca 200 mV/DIV B  $v_{\rm F} = 1/2 (v_{\rm O} + Z_{\rm O} i_{\rm O})$  $v_{\rm R}=1/2(v_0-Z_0i_0)$ 200 pSEC/DIV HYPERLYNX V7.7  $OV_{cc}$ 188 pSEC  $\leq R_3$ Ro 100  $48.8\Omega$  $R_{\Delta}$  $\mathsf{R}_2$ BGA 903 pSEC ≤ 100 ROUTE 50 48.8Ω 0.5 pF\_

Figure 1 Voltage waveforms  $v_{\epsilon}$  and  $v_{\epsilon}$  propagate in opposite directions.


The composite waveform at  $C_3$  is the sum of these two waveforms. The forward waveform (blue) appears ideal. The negative bump appears only in the reverse waveform (purple). Therefore, the bump must be a reflection coming from something to the right of  $C_3$ .

Next, consider the shape and timing of the reflected bump. The bump duration is comparable with the signal rise time, so you may conjecture that it comes from one localized spot. The center of the bump occurs 400 psec after the midpoint of the initial rising edge. That 400-psec number is a round-trip reflection delay, so the imperfection you seek must be 200 psec downstream from R<sub>s</sub>. The only significant imperfection near that location is the receiver-load capacitance, C4. If you remove C4 from the circuit, the bump disappears, confirming C<sub>4</sub> as the source of the bump. A thorough examination of  $v_{\scriptscriptstyle 
m R}$  reveals a second negative bump, smaller than the first, coincident with the main signal edge. That reflection comes from the  $C_3$ .

If this technique seems new or unusual to you, think back to when you were a little kid. Didn't your mother tell you to look both ways?
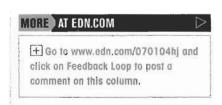
## REFERENCE

Johnson, Howard, PhD, "Eye of the probe," EDN, Dec 1, 2006, pg 30, www.edn.com/article/CA6395495.



Howard Johnson, PhD, of Signal Consulting, frequently conducts technical workshops for digital engineers at Oxford University and other sites worldwide. Visit his Web site at www.sigcon.com or e-mail him at howie03@sigcon.com.