

# **A Wireless Audio System for Remote Speakers**

*Now you can enjoy highquality  
remote sound without running  
wires around the house.*

**C**ONNECTING extension speakers to one's stereo system or rear speakers for a four-channel setup is a terrifying task for many people. It often means running speaker wires through walls and floors, hiding them under a carpet, or tacking them to baseboards. Presented here is a "wireless" system that eliminates this problem!


The new system uses existing ac power lines, operating in an FM mode. The result is good-quality audio (wide frequency response and low distortion) and a high order of noise immunity.

To overcome the old obstacles of the wireless medium (noise, narrow bandwidth, etc.), as in AM wireless intercoms, the Wireless Hi-Fi System employs an FM carrier, phase-locked-loop (PLL) and voltage-controlled-oscillator (vco) IC's. The result claimed by the author is a 30-to-17,000-Hz  $\pm 0.2$  dB frequency response, 2% total harmonic distortion (THD), and excellent noise immunity for a fine signal-to-noise (S/N) ratio of -50 dB unweighted, at 2 watts power output into an 8-ohm speaker. (How to achieve higher power output is discussed later in this article.) In addition, putting the signal on the ac line will generally assure good reception at all power outlets in your home—even if the transmitter and receiver are on *opposite* sides of the line.

---

# CONSTRUCTION

---

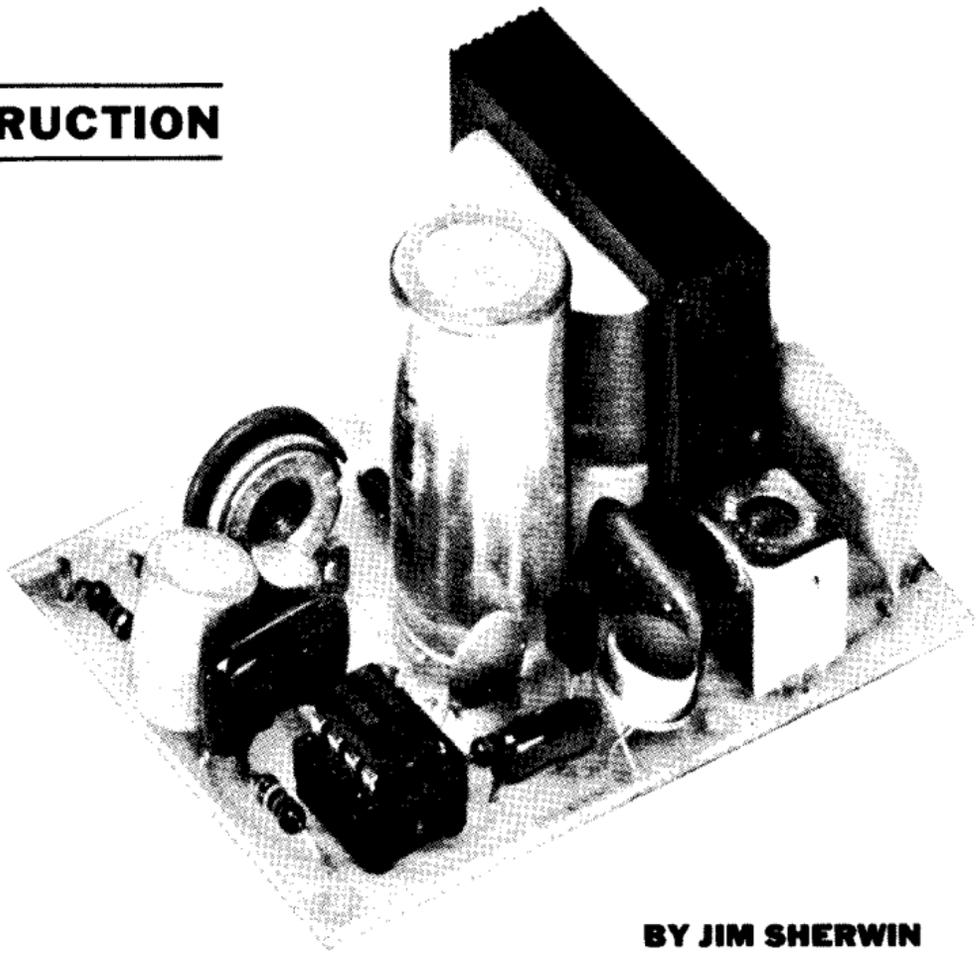


**BY JIM SHERWIN**

As structured, the system will accommodate a monophonic signal. To transmit stereo, two systems can be used, each tuned to a different carrier frequency. The drive signals can be taken from the tape monitor and tape output jacks of your amplifier. If your hi-fi system doesn't have these jacks, the signal can be taken from across the speaker terminals, but the advantage of a fixed level will be lost.


About the Circuit. The transmitter, shown schematically in Fig. 1, uses voltage-controlled oscillator IC1 to drive the Q1 amplifier. The dc power bus is regulated by IC2.

Two inputs are provided so that both left and right channels from a stereo system can be combined for transmission to a remote speaker system. For a monophonic source, resistors R7 and R8 can be eliminated and

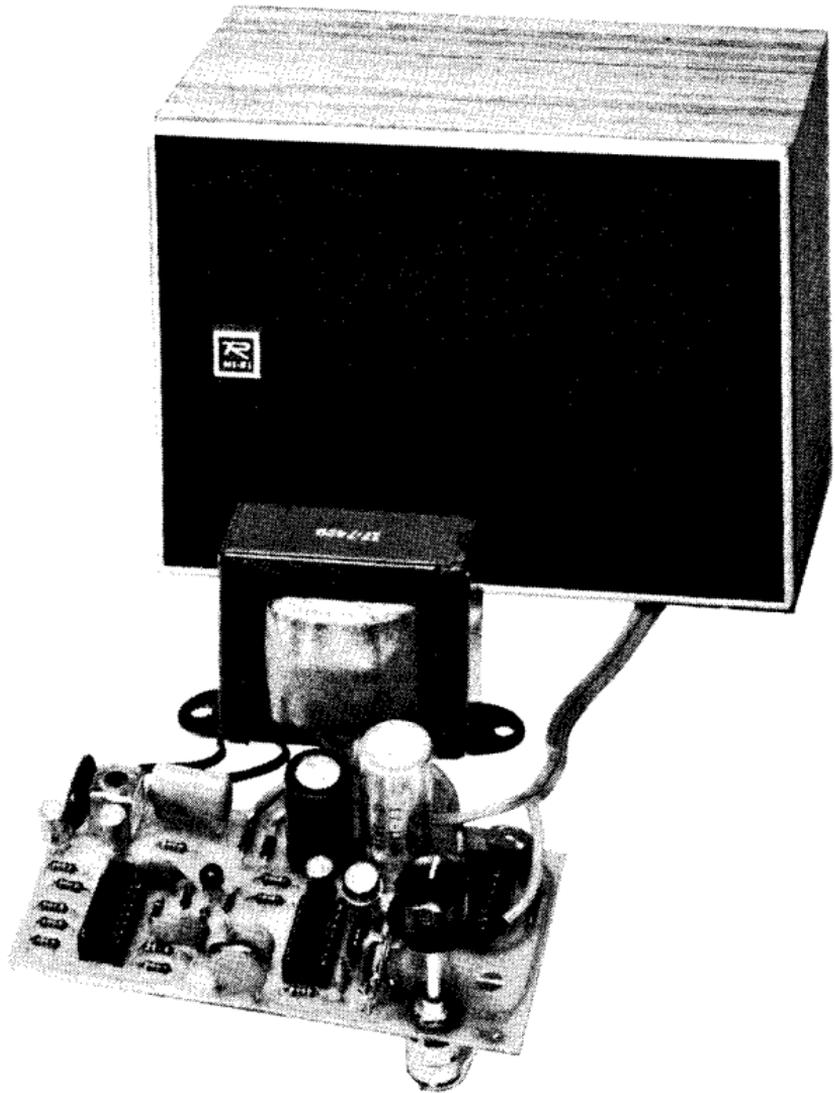

JANUARY 1976

Fig. 1. Two inputs are provided for the transmitter.  
 For a monophonic source, R7 and R8 can be eliminated.

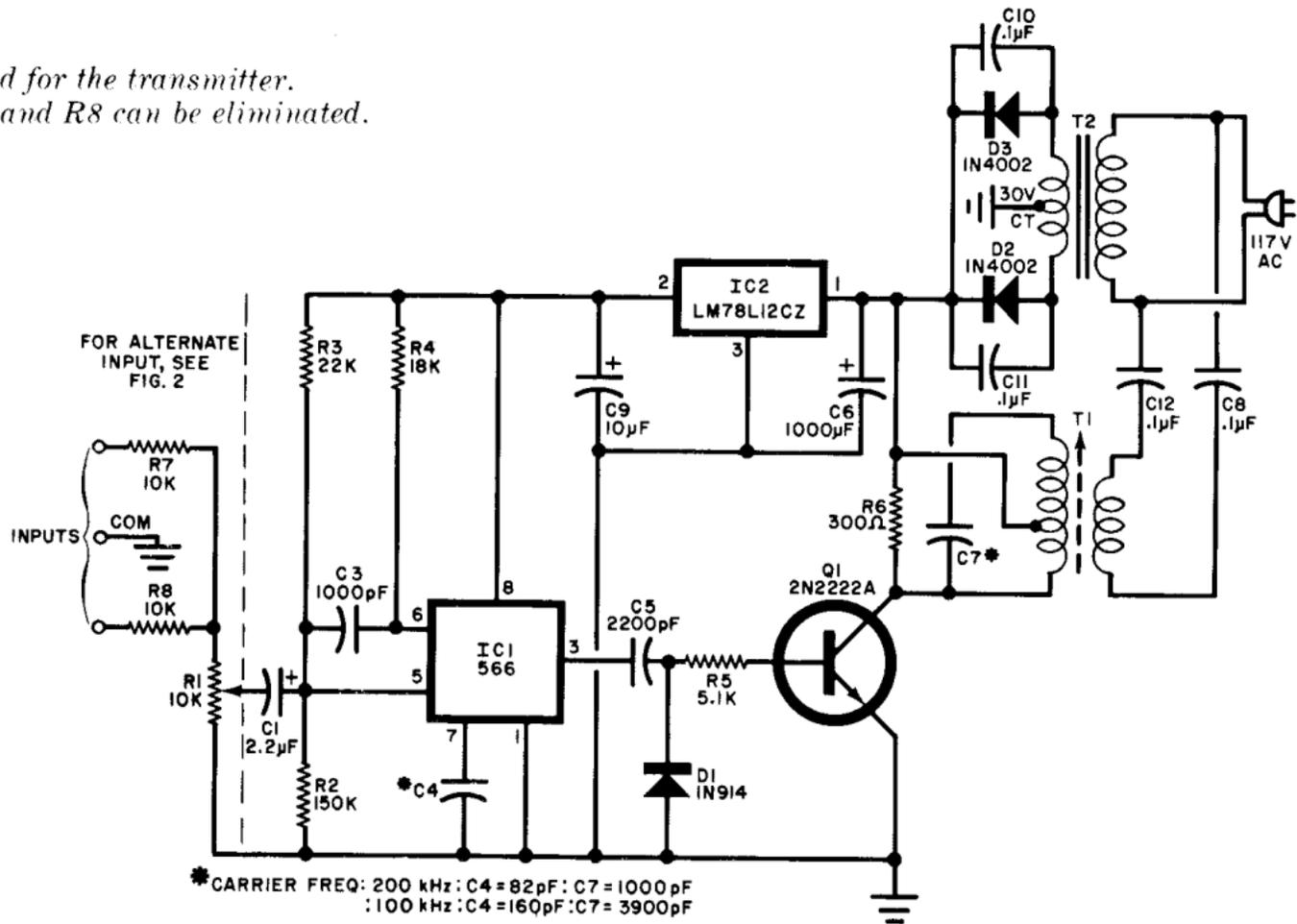


## TRANSMITTER PARTS LIST

C1,C13\*--2.2 $\mu$ F, 50-volt electrolytic capacitor  
C2\*--420-pF mica capacitor  
C3-1000-pF disc capacitor  
C4-See Fig. 1 for value  
C5-2200-pF disc capacitor  
C6-1000- $\mu$ F, 25-volt electrolytic capacitor  
C7-See Fig. 1 for value  
C8,C10,C11,C12-0.1- $\mu$ F, 200-volt film capacitor  
C9-10 $\mu$ F, 16-volt electrolytic capacitor  
D1-1N914 silicon diode  
D2,D3-1N4002 rectifier diode  
IC1--566C voltage-controlled oscillator integrated circuit  
IC2-78L12CZ-12-volt regulator integrated circuit  
IC3\*-741C operational amplifier integrated circuit.

Q1-2N2222A transistor  
R1-10,000-ohm pc-type potentiometer  
R11\*-1-megohm pc-type potentiometer  
The following resistors are 1/2 watt:  
R2--150,000 ohms, 10%  
R3-22,000 ohms, 10%  
R4,R12\*--18,000 ohms, 5%  
R5-5100 ohms, 10%  
R6-300 ohms, 5%  
R7,R8-10,000 ohms, 10%  
R9\*, R10\*--100,000 ohms, 10%  
T1--line-coupling transformer (see text)  
T2--Power transformer with 30-volt center-tapped, 50-mA secondary (Triad No. F133P or similar)  
Misc.-Printed circuit board; line cord; machine hardware; hookup wire; solder; etc.  
\*Optional pre-emphasis circuit components.  
Note--See Fig. 3 Parts List for availability of parts.

*Fig. 2. Use the circuit below to provide pre-emphasis for the transmitter in Fig. 1.*

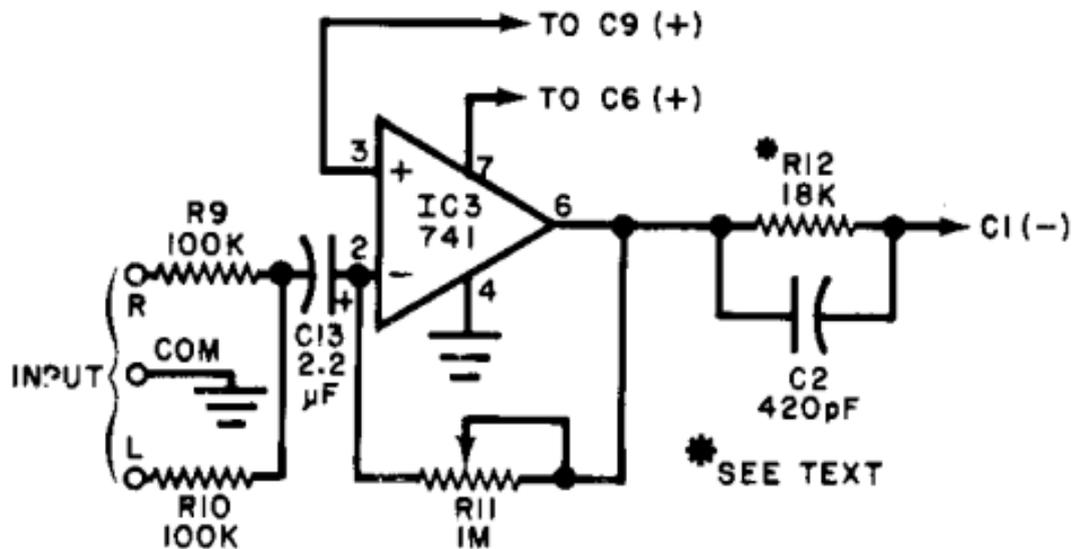

**P**OPULAR ELECTRONICS' *performance tests verified that the SIN ratio measured -65 dB, exceeding the author's claimed -50 dB. With "A" weighting it was -93 dB. At 0.9 W, distortion was 0.98%; at 2.5 W, it was 4.9%. Frequency response was 30 to 17,000 Hz ±0.5***dB-Ed.**

the input signal fed directly to the top of potentiometer R1. If you want to use the system to feed one channel from a stereo system to the other side of the room, for example, omit R8 and install a 470-pF capacitor across R7. This will improve the frequency response so that it goes out to about 20,000 Hz

The alternate input circuit shown in Fig. 2 should be used in either of two situations. First, if you are tapping the signal(s) from a high-impedance source, the 10,000-ohm resistor(s) could load down the driving signal in a mono circuit, or introduce unacceptable crosstalk between the two channels of a stereo system (as applied to the main power amplifier). If so, the circuit of Fig. 2 will provide the higher

degree of isolation required. The parallel combination R12-C2 will smooth out the frequency response of the system. To make up for losses in the RC combination, gain is provided (between unity and 10) by op amp IC1. Gain is controlled by feedback resistor R11.

Because the system's noise immunity is good, no preemphasis/de-emphasis is required. However, if you wish to experiment, the alternate input circuit should be used, with a higher RC time constant. For standard 75- $\mu$ s preemphasis, R12 should be changed to 180,000 ohms. Then, all program material above 2120 Hz will be emphasized before it enters the transmitter. As above, op amp IC1 provides gain (set by R11) to balance out losses in the preemphasis net-

work. Of course, if preemphasis is introduced in the transmitter, de-emphasis must then be incorporated into the receiver.

The free-running frequency,  $f_c$ , of voltage-controlled oscillator IC1 in Fig. 1 is determined by the values of R4 and C4. The sensitivity of the vco with the biasing shown and a  $V_c$  of +12 volts is about  $\pm 0.66 f_c/V$ . For minimum distortion, the deviation should be limited to  $\pm 10\%$ , which means that the maximum input signal level at pin 5 of IC1 should be 0.3 volt peak-to-peak. The output voltage from the tape monitor or tape output jack of an audio system may range from 0.4 to 1.5 volts rms; therefore, R1 is provided so that an appropriate modulation level can be set.

The frequency-modulated output at

pin **3** of **IC1** is roughly a 6-volt peak-to-peak square wave. This signal is used to modulate the Q1 r-f oscillator, which uses tuned transformer **T1** as its collector load. Because **T1** is tuned to  $f_c$  by adjusting its slug and C7, it serves as a high-impedance collector load, which eliminates the need for additional current limiting for Q1. Because the collector signal can have as much as a 50-volt peak-to-peak amplitude, Q1's breakdown point must be high. The transistor specified for Q1 in the Parts List has a 60-volt breakdown to provide a margin of safety. The modulated r-f output from the transmitter

is coupled to the power line via C8 and C12.

Note that Fig. 1 specifies values for C4 and C7 for either 100- or 200-kHz operation. Also note that capacitors C10 and C17 are connected across rectifier diodes D2 and D3. These capacitors reduce the small step transient that might be present across the silicon diodes whose upper harmonics fall within the frequency of interest.


The job of the receiver is to amplify, limit, and demodulate the received FM signal riding on the ac power line which can have high-amplitude noise

transients. In addition, the receiver must also provide an audio mute in the absence of a carrier.

The circuit shown in Fig. 3 picks up the incoming FM signal and tunes to the carrier frequency via the T1/C2 circuit. This signal is then applied to a two-stage limiting amplifier (composed of elements inside transistor array Q1), phase-locked loop IC1, audio amplifier IC2, and a mute circuit made up of Q1E and discrete transistor Q2.

The FM carrier is coupled to the primary of tuned transformer T1 through C1 and C27. The secondary of

Fig. 3. In the receiver, the value of C10 must be increased for de-emphasis, if preemphasis is used in transmitter.

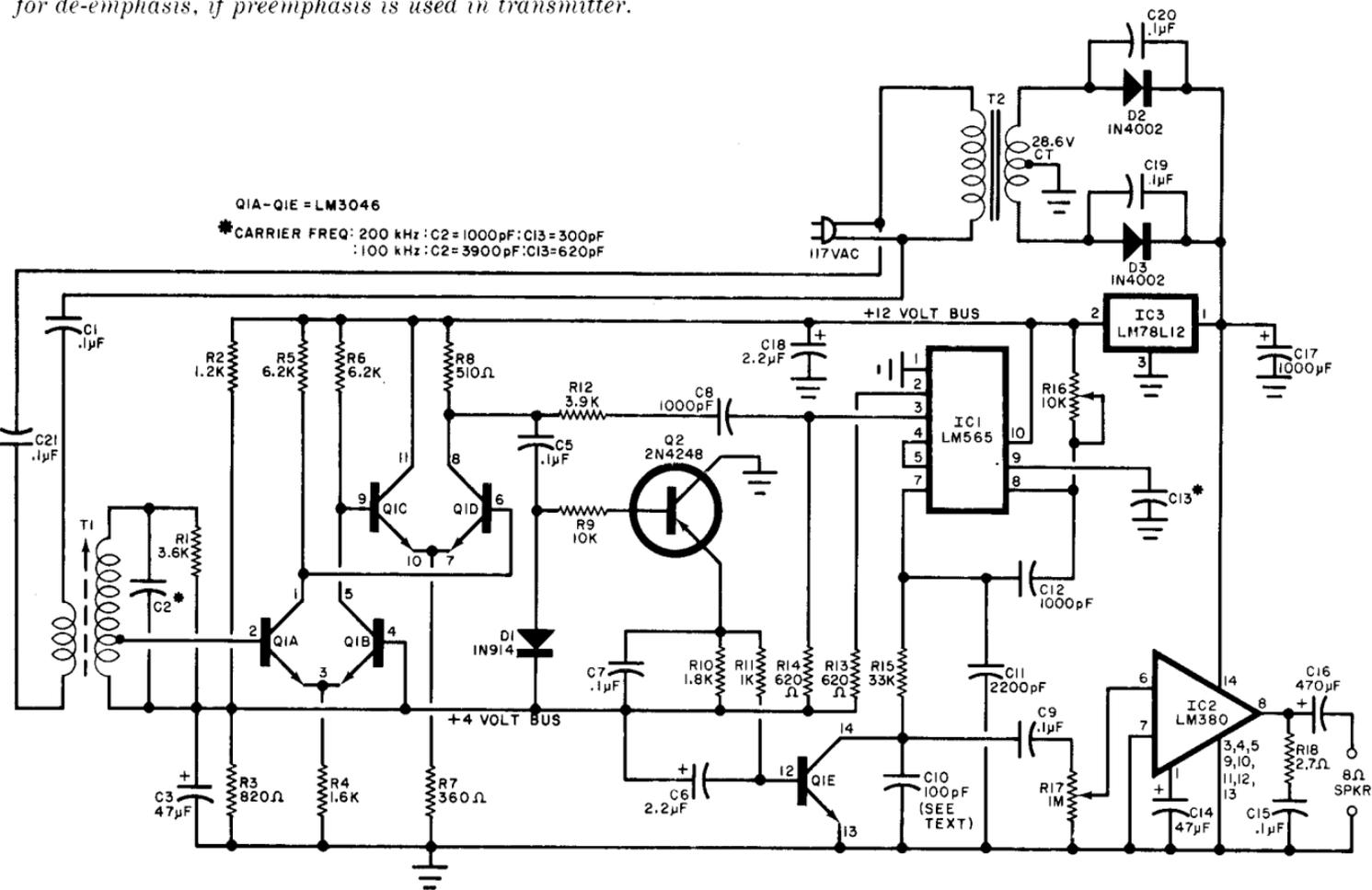

## RECEIVER PARTS LIST

**C1,C9,C19.C20,C21-O.1- $\mu$ F.** 200-volt film capacitor

**C2-See Fig. 3 for value**

**C3,C14-47 $\mu$ F,** 16-volt electrolytic capacitor

**C4-Not used**

**C5,C7,C15-0.1- $\mu$ F.** 25-volt disc capacitor

**C6,C 18-2.2- $\mu$ F,** 25-volt electrolytic capacitor

**C8, C12-1000-pF** disc capacitor

**C10-100-pF** disc capacitor (see text)

**C 11-2200-pF** disc capacitor

**C13-See Fig. 3 for value**

**C16-470 $\mu$ F.** 25-volt electrolytic capacitor

**C17-1000- $\mu$ F,** 25-volt electrolytic capacitor

**D1-1N914** silicon diode

**D2,D3-1N4002** rectifier diode

**IC 1-565C** phase-locked loop integrated circuit

**IC2-LM380** audio amplifier integrated circuit (National)

**IC3-78L 12CZ** 12-volt regulator integrated circuit

**Q1 (A to E jLM3046** transistor array (National)

**Q2-2N4248** transistor.

The following resistors are  $\frac{1}{2}$

**R2--1200** 5%

**R3-820** ohms. 5%

**R4-1600** ohms. 5%

**R5,R6--6200** Ohms. 5%

**R7-360** ohms, 5%

**R8-5 IO** ohms. 5%

**R9-10,000** ohms. 10%

**R10--1800** ohms. 5%

**R11--1000** ohm\ 5%

**R12-3900** ohms, 10%

**R13, RIG-620** ohms, 5%

**R15-33,000** ohms. 10%

**R18--2.7** ohms.10%

**R16--10,000-ohm** pc-type potentiometer


**RI7-1-megohm** potentiometer

**TI-Line-coupling** transformer (see text)

**T2-Power** transformer with 26.8-volt center-tapped, 1-ampere secondary (Triad No. F40X or similar)

**Misc.-Printed** circuit board: line cord; machine hardware: hookup wire; solder; etc.

**Note-**The following item\ are available from American Scientific Corp., 1957 Old Middlefield Rd.. Mountain View. CA 94043: etched and drilled transmitter pc board for \$3; etched and drilled receiver pc hoard for \$5.50; transmitter ICs and transistor\ and Toko line-coupling transformer for \$6.00; receiver IC's and transistors and Toko transformer for \$10.50: complete transmitter kit for \$18.95. plus \$1.00 shipping; complete electronics receiver kit for \$27.95. plus \$1.00 shipping. National Semiconductor IC's are available. singly or in quantity from OEMorsco, 2403 Charleston Rd.. Mountain View. CA 94043.

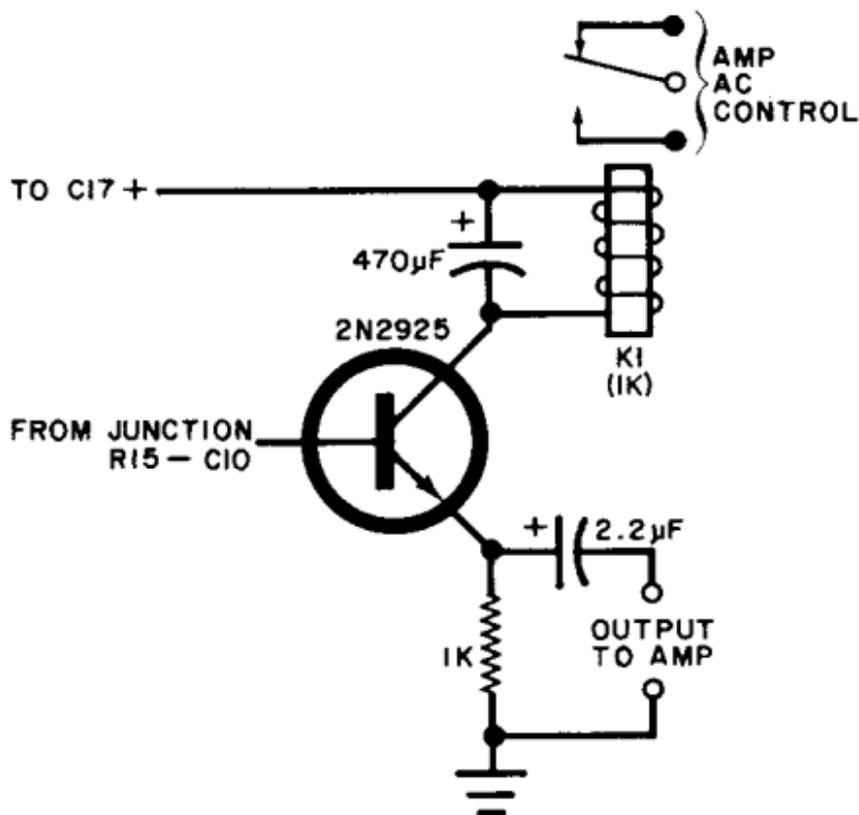

*Fig. 4. Use this circuit to change receiver output for more power.*

$T1$  is tuned by  $C2$ , while  $R1$  lowers the  $Q$  of the circuit to permit it to accept the  $\pm 10\%$  modulation and to prevent excessive ringing on noise spikes. Such ringing would cause the mute circuit to deactivate. The secondary of  $T1$  is tapped to match the input impedance of  $Q1A$ . The recovered carrier at the secondary of  $T1$  can have an amplitude of between 0.2 and 45 volts peak-to-peak. The 17:1 turns ratio from the full secondary to the tap reduces the amplitude of the recovered carrier so that the base of  $Q1A$  "sees" a signal that ranges from 12 mV to 2.6 volts peak-to-peak.

The two-stage limiter amplifier composed of  $Q1A$  through  $Q1D$  operates as a fairly fast comparator whose slew rate is about 70 volts/us and gain is about 3000. The output from this limiter is a roughly 7-volt peak-to-peak square wave that has rise and fall times of 100 ns. (Any fairly fast comparator that delivers more than 5 volts output could be used as the limiting amplifier. However, the transistor array specified is a low-cost item that has the advantage of containing an extra-high beta transistor,  $Q1E$ , which is used as the mute switch.) The 7-volt peak-to-peak output of the limiting

amplifier is applied directly to the mute detector, Q2, but is reduced to about 1 volt by the attenuator consisting of R12 and R14 before being applied to PLL IC1.

The PLL operates as a narrow-band filter that tracks the incoming FM signal and provides a low-distortion demodulated audio output whose signal-to-noise (S/N) ratio is high. The oscillator inside the PLL is set to free-run at a frequency near that of the car-

rier by the choice of value for C13 and setting of R16.

If 75-microsecond preemphasis is used, increase the value of C10 to 2200 pF. Increasing this capacitor's value will reduce the carrier level in the audio line at the expense of high-frequency audio response.


The mute circuit quiets the receiver when no carrier is present. Without this circuit, an excessive noise level would result as the PLL attempts to



*Fig. 5. Etching and drilling guide for the transmitter are shown above (A). Component placement for standard transmitter is at left (B). If pre-emphasis is used, the component placement at right is necessary (c).*

**B**

**C**

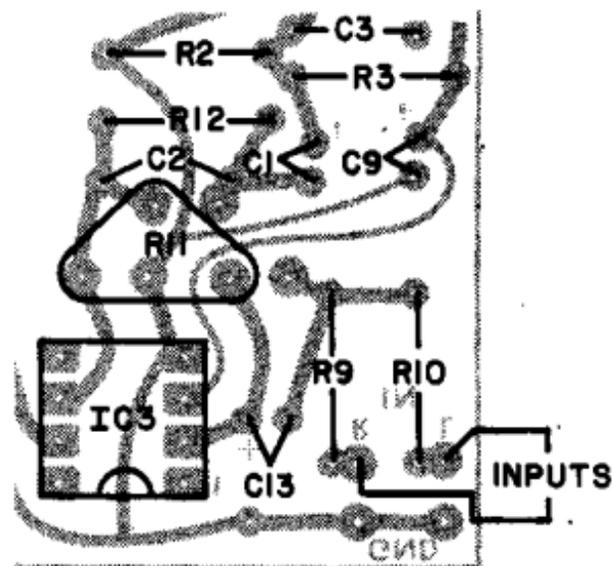


**POPULAR ELECTRONICS**

lock onto noise spikes when the transmitter is shut off. The mute detector is composed of C7, D1, and Q2. Note that an emitter-follower transistor stage is used in place of a diode to give the peak detector a high input and a low output impedance. This permits the peak detector to shunt 1 to 2 mA of bias away from Q1E, without loading the limiter amplifier.

With no carrier present, the +4-volt line biases Q1E into conduction via R10 and R11, shorting the audio signal to ground. When a carrier is present, the 7-volt square wave from the limiter amplifier is peak detected, producing a negative output that is integrated by R9 and C7, averaged by R10 across C7, and further integrated by C6 and R11. The resultant -4-volt output subtracts from the +4-volt bias to deprive Q1E of base current. This transistor cuts off and allows the demodulated audio signal to pass to the audio amplifier. Peak detector integration and averaging prevents random noise spikes from deactivating the mute when no carrier is present.


Audio amplifier IC2 supplies about 2 watts of audio power to an 8-ohm speaker connected across the output of the receiver. Although this amount of power is adequate for casual and background-music listening, if you want to drive relatively inefficient hi-fi speaker systems, you'll have to modify the output of the receiver to drive a hi-fi amplifier. The circuit shown in Fig. 4 does this. To use it, audio power amplifier IC2 is removed from the receiver circuit and the Fig. 4 circuit goes into the receiver as specified. This switching circuit operates from the mute signal so that when the transmitter is switched on, the relay will energize to apply power to the external power amplifier. In this manner, the power amplifier will automatically switch on when a signal is received. Standby power is less than 1 watt.

**Construction.** The transmitter is best assembled on a printed circuit board, the etching and drilling guide for which is shown actual size in Fig. 5A. In Fig. 5B is the component placement diagram for the board, while the detail in Fig. 5C shows the additions and changes to be made when preemphasis is used in the transmitter. When comparing Band C, note that R1 is eliminated from the former and R11 is installed in the latter, *displaced one pad space to the left* but oriented the same.

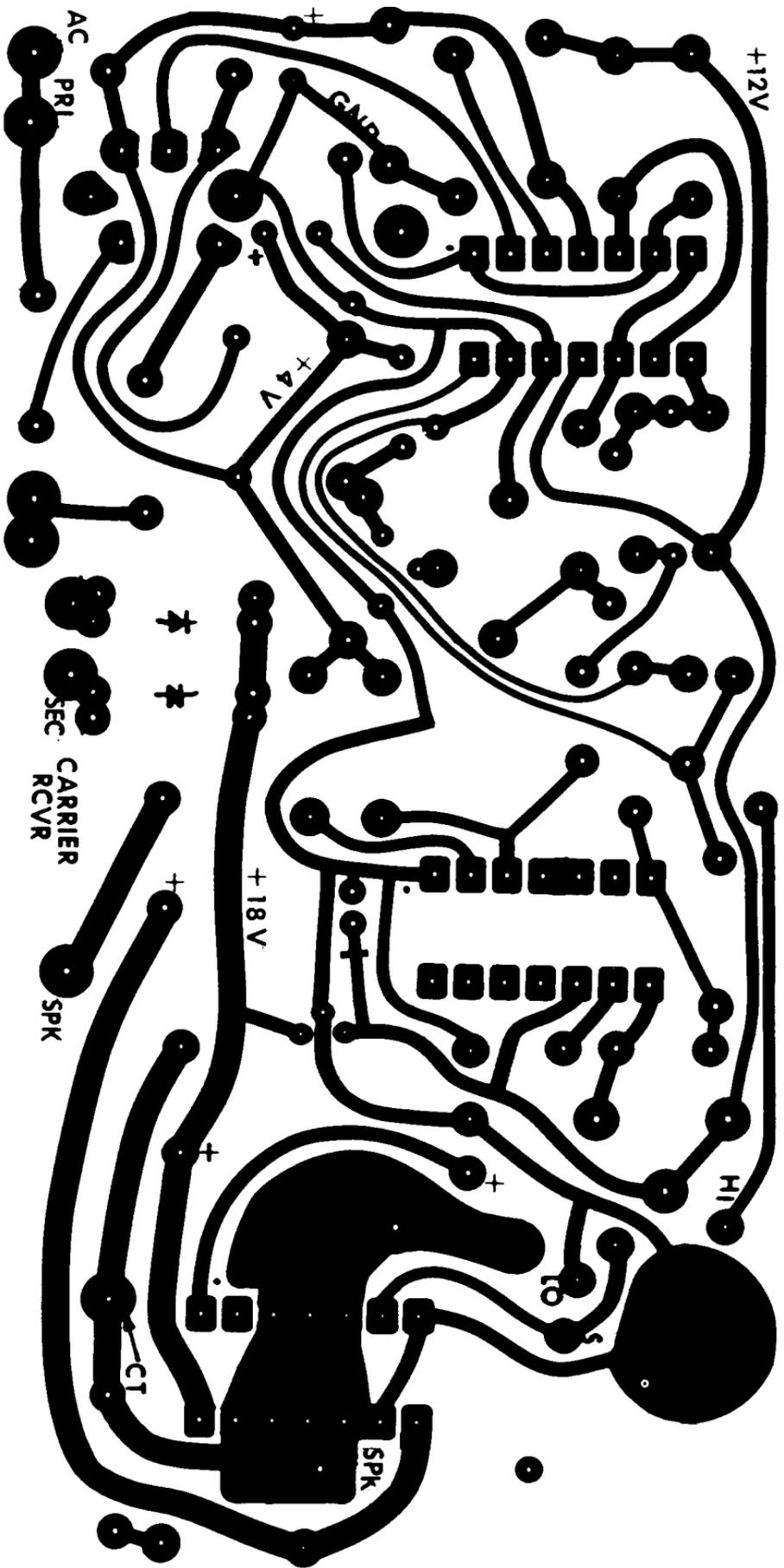

**A**

*Fig. 6A. Etching and drilling guide for the receiver is shown above. The component placement diagram (Fig. 6B) is on next page.*

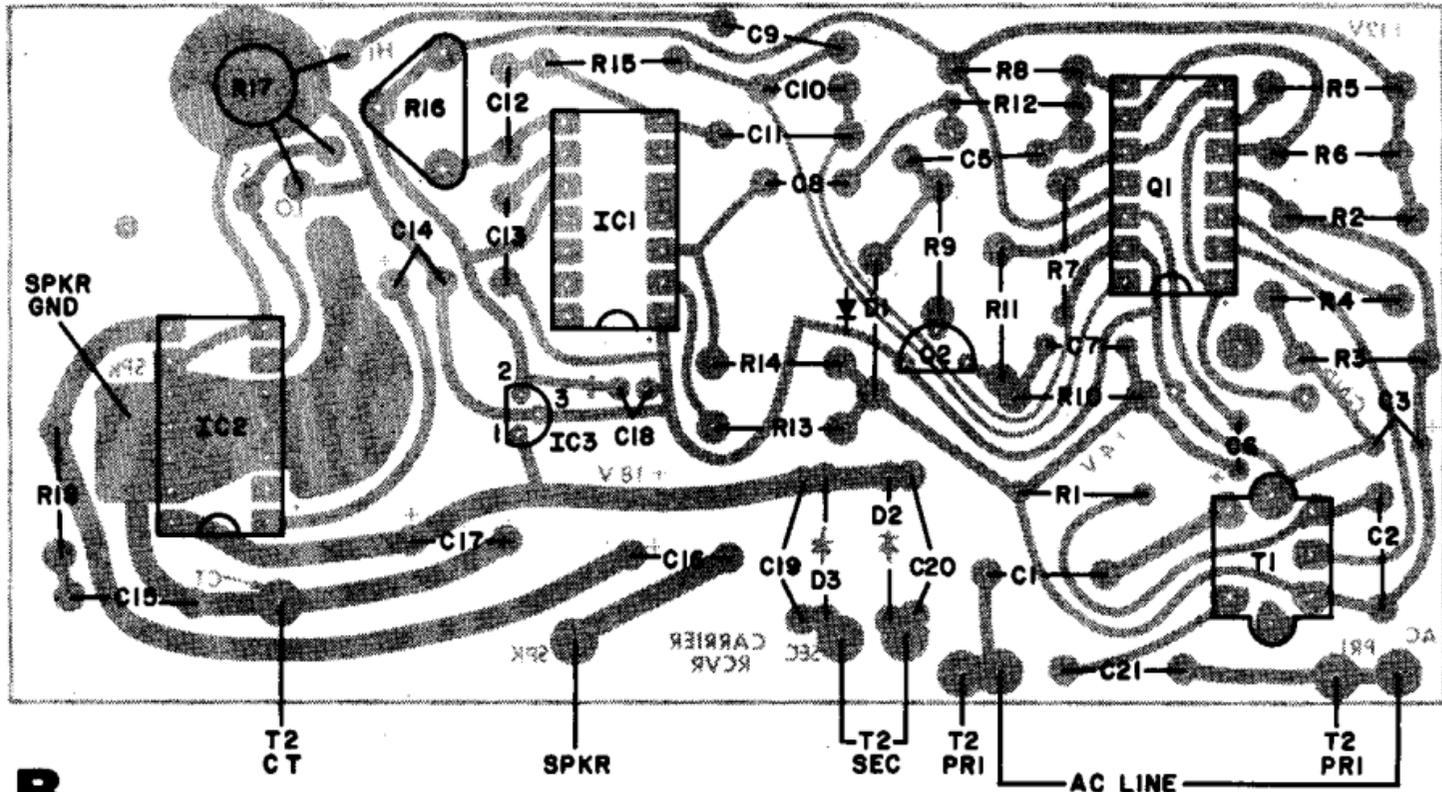

**B**

*Fig. 6B. Component placement diagram for the receiver is shown above. Foil pattern (Fig. 6A) is on previous page.*

Line-coupling transformer T1 can be made from a 455-kHz AM i-f transformer. In rewinding the turns, the secondary is made up of four turns, while 154 turns are used in the primary, tapped 29 turns from one end of the coil. You can use the wire originally wound on the transformer or 41 AWG enameled wire for the turns.

As with the transmitter, the receiver is best assembled on a printed circuit board. The etching and drilling guide and components placement diagram are shown in Fig. 6A & B.

Line-coupling transformer T1 is constructed in the same manner as described for T1 in the transmitter, except that primary is composed of 4 turns the secondary 154 turns, tapped 9 turns from one end.

**Adjustments.** Make sure that the transmitter and receiver are operating at the same frequency. (See Figs. 1 and 3 for values of frequency-determining components.) Plug the transmitter and receiver into ac outlets and use an oscilloscope or ac voltmeter to check the amplitude of the waveform across the secondary of T1 in the receiver. There is no need at this time to have the carrier modulated.

Adjust the slugs in the T1's in both the transmitter and the receiver for maximum signal amplitude across the secondary of T1 in the receiver. If the receiver is to be located some distance from the transmitter or on the opposite side of a 117/220-volt service line, T1 will have to be readjusted in the receiver to maximize rejection of ac line noise.

The free-running frequency of the PLL in the receiver is trimmed by adjusting R16, which should initially be

set near the center of its range. Rotate R16's wiper slowly in both directions until the PLL loses lock, indicated by a sharp increase in noise and a distorted output from the receiver. Note the two positions where drop-out occurs; center R16 between these two points. A finer adjustment may be required to obtain minimum noise if an SCR light dimmer is in operation.

The final adjustment is for modulation amplitude in the transmitter. Connect an audio signal source to the input of the transmitter and adjust R1 for a signal amplitude of about 0.1 volt rms maximum at the input (pin 5) of IC1. This can also be accomplished by carefully listening to the receiver while adjusting R1 in the transmitter until the sound just distorts and then backing off a little.

Because a single transmitter/receiver system will suffice for a monophonic sound system or for one channel of a stereo system, a second receiver and transmitter will be required for stereo sound over the wireless medium. In this case, one transmit/receive system would be tuned to 100 kHz and the other to 200 kHz. You can also use a pair of transmit/receive systems for the rear channels in a 4-channel system to avoid running cables all over your listening room. Again, you would use a different carrier frequency for the different channels.

One final note: Although we have mentioned using carrier frequencies of 100 kHz and 200 kHz for a two transmit/receive system, this spacing needn't be 100 kHz apart. For most purposes, a 40-kHz spacing will do, while still providing maximum frequency response from the system. ♦