

Program analyzes all-resistive dc circuits

by Mark Jong
Wichita State University, Wichita, Kansas

Networks that are strictly resistive can be analyzed easily and quickly for dc conditions with a brief but effective computer program written in Basic. The circuit to be analyzed can also contain active devices, provided those devices can be represented by only resistive elements and voltage-dependent sources.


The standard circuit branch allowed by the program is shown in Fig. 1, along with the program listing. Nodes may be numbered in any order with consecutive integers beginning with zero. (The program always assumes that node 0 is the reference node.) Branches may also be numbered in any order with consecutive integers, but this set of numbers must begin with the number one.

The program first asks to know the number of nodes minus one, and then it requests the number of branches.

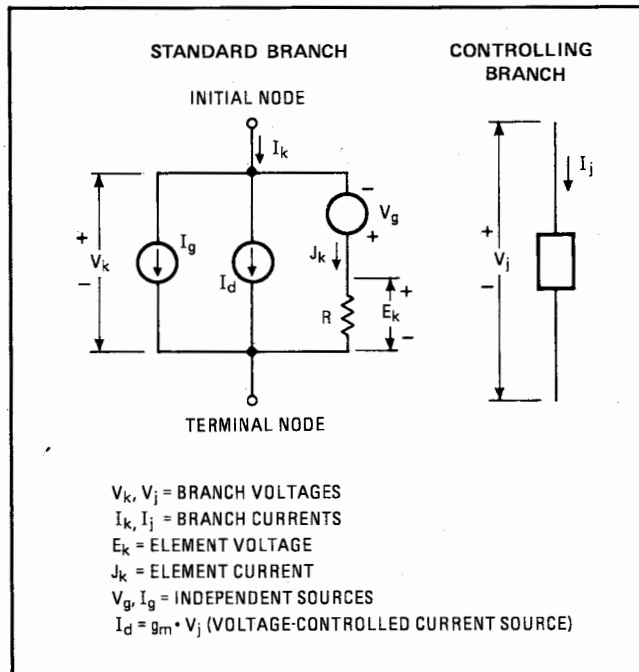1. Dc circuit analysis. Computer program, which is written in Basic, is useful for a speedy dc analysis of small resistive networks. The definitions for a standard circuit branch and the program listing itself are given here. Dependent sources must be voltage-controlled.

(A question mark is typed after each request.) The user responds by typing in the data requested each time, and pressing the RETURN key on his terminal.




After this preliminary input data is obtained, the program asks for the branch data by typing a question mark each time for each branch. In response, the user types in the data for each branch in a specific order and



```

100 DIM A(7,15),Y(15,15),E(15),I(15),
    J(15),V(15),S(15),W(15,7),U(15,7)
110 PRINT "NUMBER OF NODES - 1 = ";
111 INPUT N
120 PRINT "NUMBER OF BRANCHES = ";
121 INPUT B
130 MAT A=ZER(N,B)
140 MAT Y=ZER(B,B)
150 MAT E=ZER(B)
160 MAT I=ZER(B)
170 FOR K=1 TO B
180 INPUT B1,F1,T1,R,E(B1),I(B1),Y1,C1
190 IF F1=0 THEN 210
200 LET A(F1,B1)=1
210 IF T1=0 THEN 230
220 LET A(T1,B1)=-1
230 LET Y(B1,B1)=1/R
240 IF C1=0 THEN 260
250 LET Y(B1,C1)=Y1
260 NEXT K
270 MAT S=ZER(B)
275 MAT J=ZER(B)
280 FOR K=1 TO B
281 LET S(K)=Y(K,K)*E(K)
282 NEXT K
290 MAT S=I+S
295 MAT S=J-S
300 MAT W=ZER(B,N)
310 MAT W=TRN(A)
320 MAT U=ZER(B,N)
330 MAT U=Y*W
340 MAT W=ZER(N,N)
350 MAT W=A*U
360 MAT U=ZER(N,N)
370 MAT U=INV(W)
380 MAT V=ZER(N)
390 MAT V=A*S
400 MAT J=ZER(N)
410 MAT J=U*V
420 PRINT
430 PRINT "NODE"," VOLTAGE"
440 FOR K=1 TO N
450 PRINT K,J(K)
460 NEXT K
470 MAT V=ZER(B)
480 MAT W=ZER(B,N)
490 MAT W=TRN(A)
500 MAT V=W*J
510 MAT J=ZER(B)
520 MAT J=Y*V
530 MAT J=J-S
540 PRINT
550 PRINT "BRANCH"," VOLTAGE"," CURRENT"," POWER"
560 FOR K=1 TO B
570 PRINT K,V(K),J(K),V(K)*J(K)
580 NEXT K
590 MAT V=V+E
600 PRINT
610 PRINT "ELEMENT"," VOLTAGE"," CURRENT"," POWER"
620 FOR K=1 TO B
630 LET J(K)=Y(K,K)*V(K)
640 PRINT K,V(K),J(K),V(K)*J(K)
650 NEXT K
660 END

```

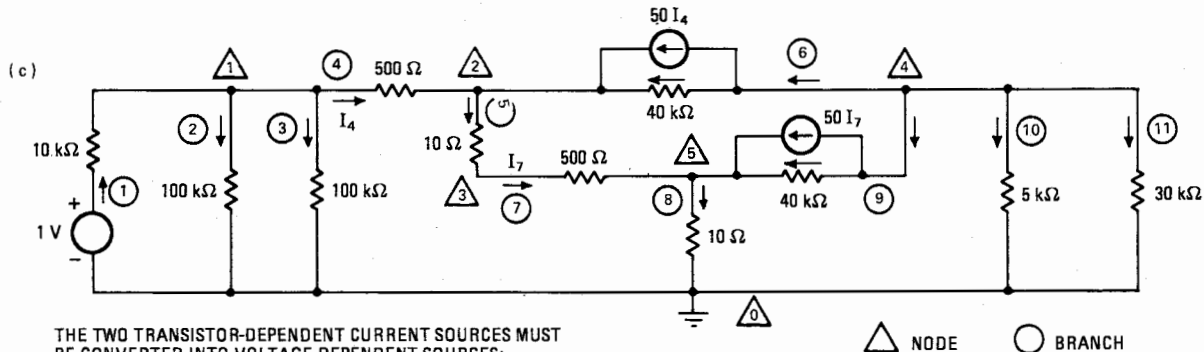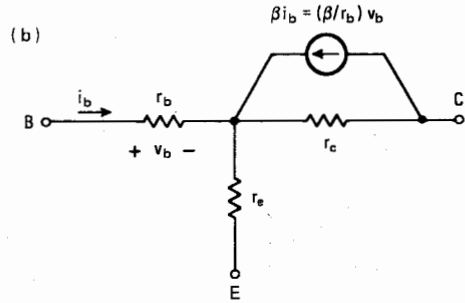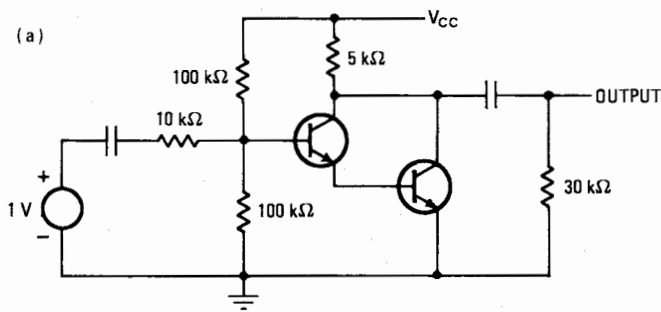

THE TWO TRANSISTOR DEPENDENT CURRENT SOURCES MUST BE CONVERTED INTO VOLTAGE-DEPENDENT SOURCES:
 $50 I_4 \rightarrow 50 (V_4/500) = 0.1 V_4$
 AND $50 I_7 \rightarrow 0.1 V_7$

(d)

```

READY
RUN
NUMBER OF NODES - 1 = 25
NUMBER OF BRANCHES = 11
?1, 1, 10000, 1, 0, 0, 0
?2, 1, 100000, 0, 0, 0, 0
?3, 1, 100000, 0, 0, 0, 0
?4, 1, 2, 500, 0, 0, 0, 0
?5, 2, 3, 10, 0, 0, 0, 0
?6, 4, 2, 40000, 0, 0, 0, 1, 4
?7, 3, 5, 500, 0, 0, 0, 0
?8, 5, 0, 10, 0, 0, 0, 0
?9, 4, 5, 40000, 0, 0, 0, 1, 7
?10, 4, 0, 5000, 0, 0, 0, 0
?11, 4, 0, 30000, 0, 0, 0, 0
  
```

NODE	VOLTAGE
1	.428572
2	.428286
3	.428121
4	-.222203
5	.191866

BRANCH	VOLTAGE	CURRENT	POWER
1	-.428572	5.71428E-05	-2.44898E-05
2	.428572	4.28572E-06	1.83674E-06
3	.428572	4.28572E-06	1.83674E-06
4	2.42857E-02	4.85713E-05	1.17959E-06
5	4.16505E-03	4.16505E-04	1.73477E-06
6	-.22.4246	3.67952E-04	-3.43283E-02
7	.228255	4.16509E-04	8.67399E-05
8	.191866	1.91866E-02	3.68127E-03
9	-.22.2122	1.87701E-02	-1.54314
10	-.22.2203	-1.64041E-02	1.34547
11	-.22.2203	-2.73401E-03	.224245

ELEMENT	VOLTAGE	CURRENT	POWER
1	.571428	5.71428E-05	3.26530E-05
2	.428572	4.28572E-06	1.83674E-06
3	.428572	4.28572E-06	1.83674E-06
4	2.42857E-02	4.85713E-05	1.17959E-06
5	4.16505E-03	4.16505E-04	1.73477E-06
6	-.22.4246	-2.06042E-03	-1.69845
7	.228255	4.16509E-04	8.67399E-05
8	.191866	1.91866E-02	3.68127E-03
9	-.22.2122	-2.05531E-03	-1.68971
10	-.22.2203	-1.64041E-02	1.34547
11	-.22.2203	-2.73401E-03	.224245

READY

2. Program at work. The transistor amplifier in (a) is analyzed for dc conditions. The T-model equivalent circuit (b) can be used for the transistors, provided that all dependent current sources are converted into voltage-dependent sources. In the complete amplifier equivalent circuit (c), all nodes and branches are numbered consecutively. The program printout is shown in (d).

on the same line. He gives the branch number, the initial node number, the terminal node number, the resistance value, the value of the independent voltage source, the value of the independent current source, the transconductance of the dependent current source, and the number of the branch that is controlling the dependent current source, finally pressing the RETURN key.

The polarity signs allotted to the voltage and current sources must agree with the sign conventions defined by the standard branch of Fig. 1. The various data inputs must be separated by commas.

Once the program has all of the input data, it will compute the circuit's output node voltages, as well as all the branch and element voltages, currents, and power. The element of a branch is the resistance of that branch. When there is no current source associated with a branch, the branch current is the same as the element current. And when a branch does not have a voltage source, branch and element voltages are the same.

Figure 2 shows an example analysis of a two-transistor amplifier (Fig. 2a). The simple T-model equivalent circuit (Fig. 2b) is used to represent each transistor. In the complete amplifier equivalent circuit (Fig. 2c), the node numbers are enclosed by triangles, and the branch numbers are encircled. The program printout (Fig. 2d) conveniently tabulates the input data, the output node voltages, the branch data, and then the element data.

On a 16-bit minicomputer with an 8,000-word memory, the program can handle a circuit having up to seven nodes and 15 branches. If a machine with more storage capacity is used, the dimensions of the arrays set up by statement 100 in the program listing can be increased to accommodate larger circuits. □

Engineer's notebook is a regular feature in Electronics. We invite readers to submit original design shortcuts, calculation aids, measurement and test techniques, and other ideas for saving engineering time or cost. We'll pay \$50 for each item published.