## Contact tester quantifies open-, short-circuit tendencies

by Steven Nirenburg and Wunnava V. Subbarao Florida International University, Mlami, Fla.

Many present-day electronic systems, being modular in nature, rely heavily on connector blocks to hook the various functional units together. As such, it is becoming increasingly important to detect any momentary opencircuit or short-circuit tendencies of the system at the connector—especially in high-vibration environments—both in production-line testing and during actual operation. This tester detects both, while indicating if either condition persists beyond a given time preset by the user.

Consider the detection of an open-circuit tendency of contact  $S_1$ , as shown in the figure. For the purposes of discussion, the open-circuit condition is arbitrarily chosen to be one in which the resistance across  $S_1$  is greater than 10 ohms for a period equal to or greater than 100 microseconds.


On system reset, the 74192 counters and 7476 flipflops are brought to logic 0. If  $S_1$  is closed, voltage  $V_1$ will be near zero and the outputs of comparators  $G_1$  and  $G_2$  will be high. Light-emitting diode  $D_0$  then glows, indicating the contact is closed. If  $S_1$  is momentarily opened or shows any contact deterioration,  $V_1$  rises slightly above ground potential, forcing  $G_1$  low and gating the output of the 1-megahertz clock through to the counters. Thus should the contact deterioration last for 100  $\mu$ s, 100 clock pulses will be counted and the resulting carry pulse generated from the second 74192 will set flip-flop  $F_1$ . And if the ohmic resistance across  $S_1$  goes above 10  $\Omega$ ,  $V_1$  will rise above 50 millivolts, forcing  $G_2$  low and flip-flop  $F_2$  high.

Thus  $D_1$  will glow if  $F_1$  is set and  $F_2$  is clear.  $D_2$  will glow if  $F_1$  is clear and  $F_2$  is set.  $D_3$  will light if both  $F_1$  and  $F_2$  are set, so that the predetermined open-circuit time and resistance of  $S_1$  may be readily recorded.


Short circuits are readily detected by connecting points A and B across the normally opened contact under test. When the contact is open,  $V_1$  is near zero and the system remains in the reset position, lighting up  $D_0$ . If shorted momentarily,  $S_1$  will cause either  $D_1$ ,  $D_2$  or  $D_3$  to light. For the values shown in the figure,  $D_1$  will glow if the short circuit exceeds 100  $\mu$ s or more;  $D_2$  indicates if  $S_1$ 's resistance is less than 1 M $\Omega$ ;  $D_3$  illuminates if both of the aforementioned conditions exist.

By changing the clock frequency or the counting limit, any time interval can be preset. Similarly, the impedance at which the circuit responds may be selected by adjusting the threshold voltage at  $G_2$ .

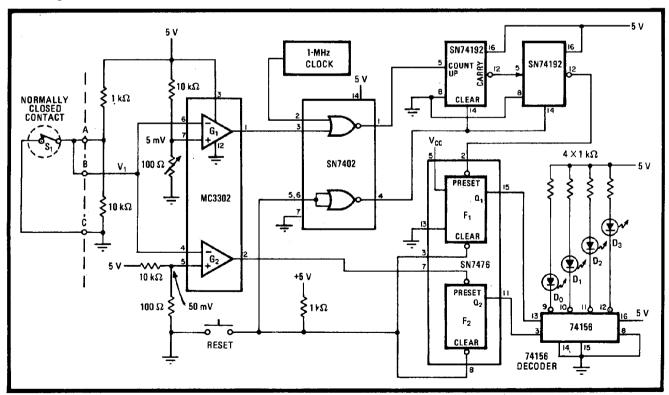Engineer's notebook is a regular feature in *Electronics*. We invite readers to submit original design shortcuts, calculation aids, measurement and test techniques, and other ideas for saving engineering time or cost. We'll pay \$50 for each item published.



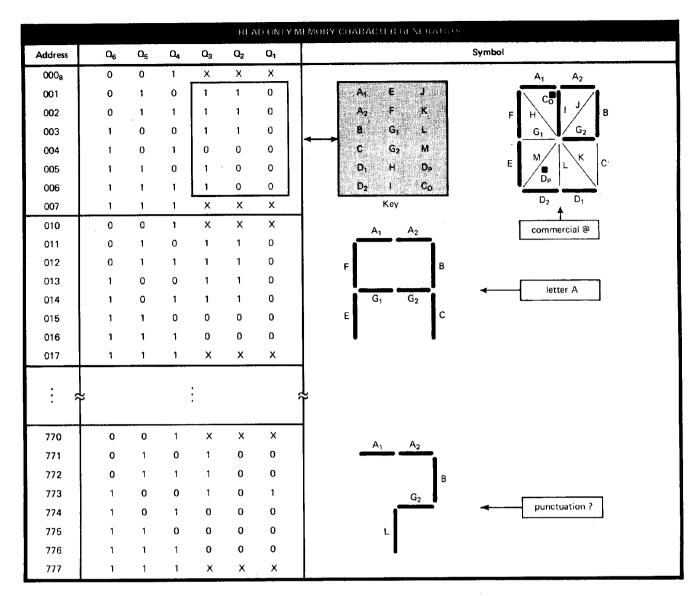**Connection.** Tester for block connectors, pc boards, and cable assemblies indicates if duration of open or short circuit in circuit pin or lead exceeds preset time and checks relative magnitude of resistance across switch or broken wire. Four LEDs indicate state of affairs.



requiring high voltage may be accommodated, also.

In general operation (see figure), the microprocessor coordinates character selection, strobe-timing, and overall control duties with the aid of the NE590 strobe drivers, the NE591 peripheral display drivers, and the 74LS175 quad latch. When suitably addressed, the 82S115 512-word-by-8-bit PROM, which stores all the ASCII characters, delivers a logic-state table corresponding to the character selected via the clocked 74LS175 and the NE591s.

The PROM functions both as a character-request lookup table and as a state machine, with the quad flip-flop holding the current machine state. Bit 7 of the processor initializes the state to zero at the beginning of a character-decode cycle.

Logic signals corresponding to the character desired are then applied to pins  $A_3$ - $A_8$  of the PROM, and the device is clocked through seven states (see table) so that the desired segments are excited. The display is then strobed and the character thus placed in any desired location via command from pins 0 to 6 of the processor via the strobe latches, each latch of which is enabled separately. This process is repeated for up to 64 charac-

ters, the maximum that may be placed on the display at any given instant. Thereafter, as in all multiplexed displays, only one character is enabled at any time. All characters will appear to be displayed continuously, however, because of the high scanning rate.

As seen in the table, during each clocked state the PROM generates 3 bits of segment information. Six such states define the character produced. Thus only three display segments switch during each NE591 latching period, substantially reducing load transients and large load-current variations, which tend to cause difficulty in circuits of this kind. Only six of each NE591's eight outputs are used, to reduce power dissipation. Note that each device handles 6 of the total of 18 display segments for each character.

As the circuit is digital, neither layout nor component values are critical. The clock frequency, typically less than 5 MHz, should have a minimum pulse width (t<sub>w</sub>) of 100 ns, however, in order to ensure proper display and strobe latching.