

Commercial-Quality Function Generator

How about this addition to the bench?

How many times have you needed a function generator to provide a source of sine or square waves to test your ham equipment or a new circuit idea? More than a couple, at least if you are anything like most experimenters. A good, high-quality, dual-tone sine wave generator is a really needed item also, if you need to check out your SSB transmitter and linear amplifier performance.

Well, here is such an instrument that does those jobs nicely, with the added fea-

ture of a frequency counter that is also a nice extra to have. So let us take a look at what is required.

First, we must understand what I was interested in when doing the design phase. The absolute number one

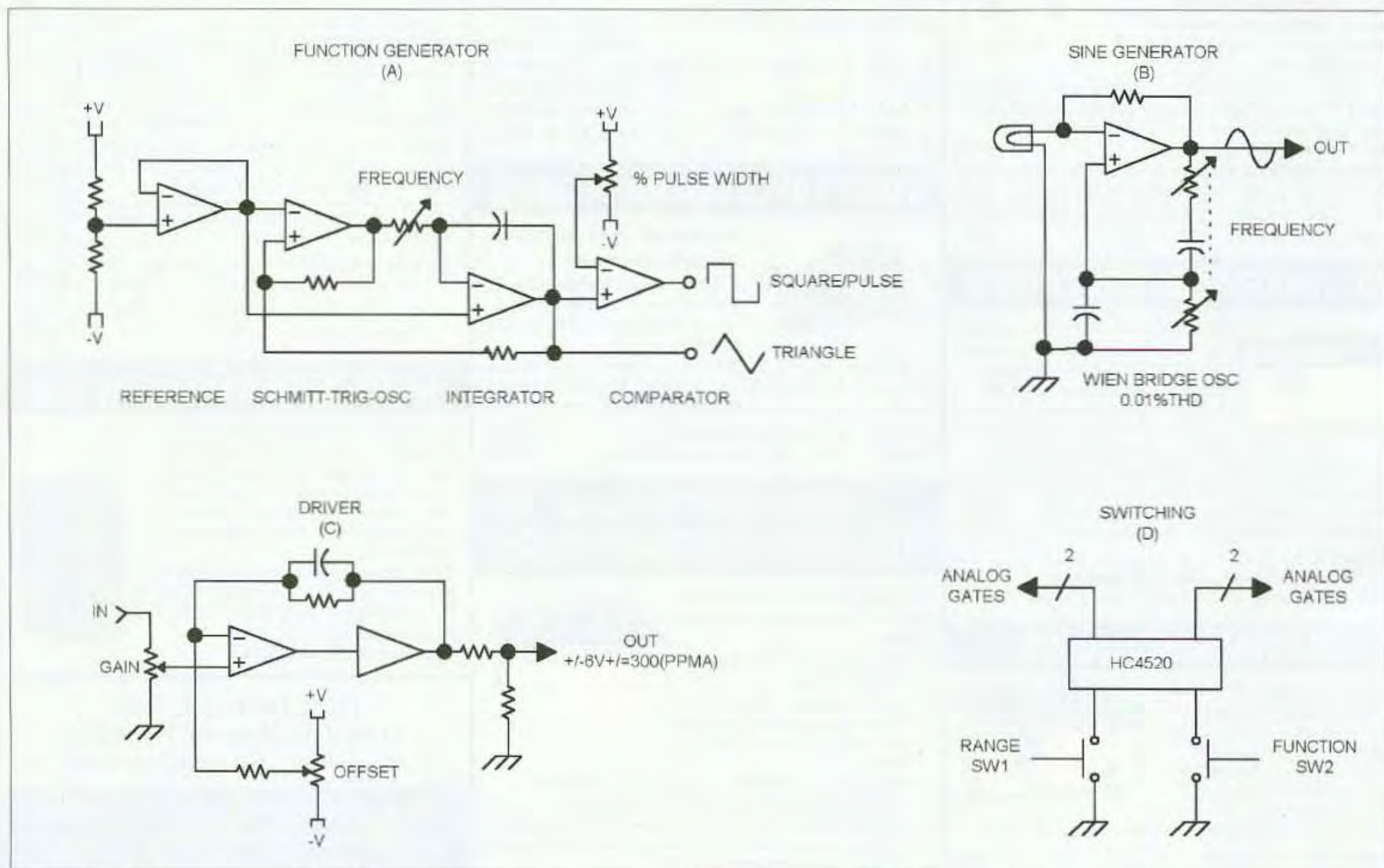


Fig. 1. Simplified schematics.

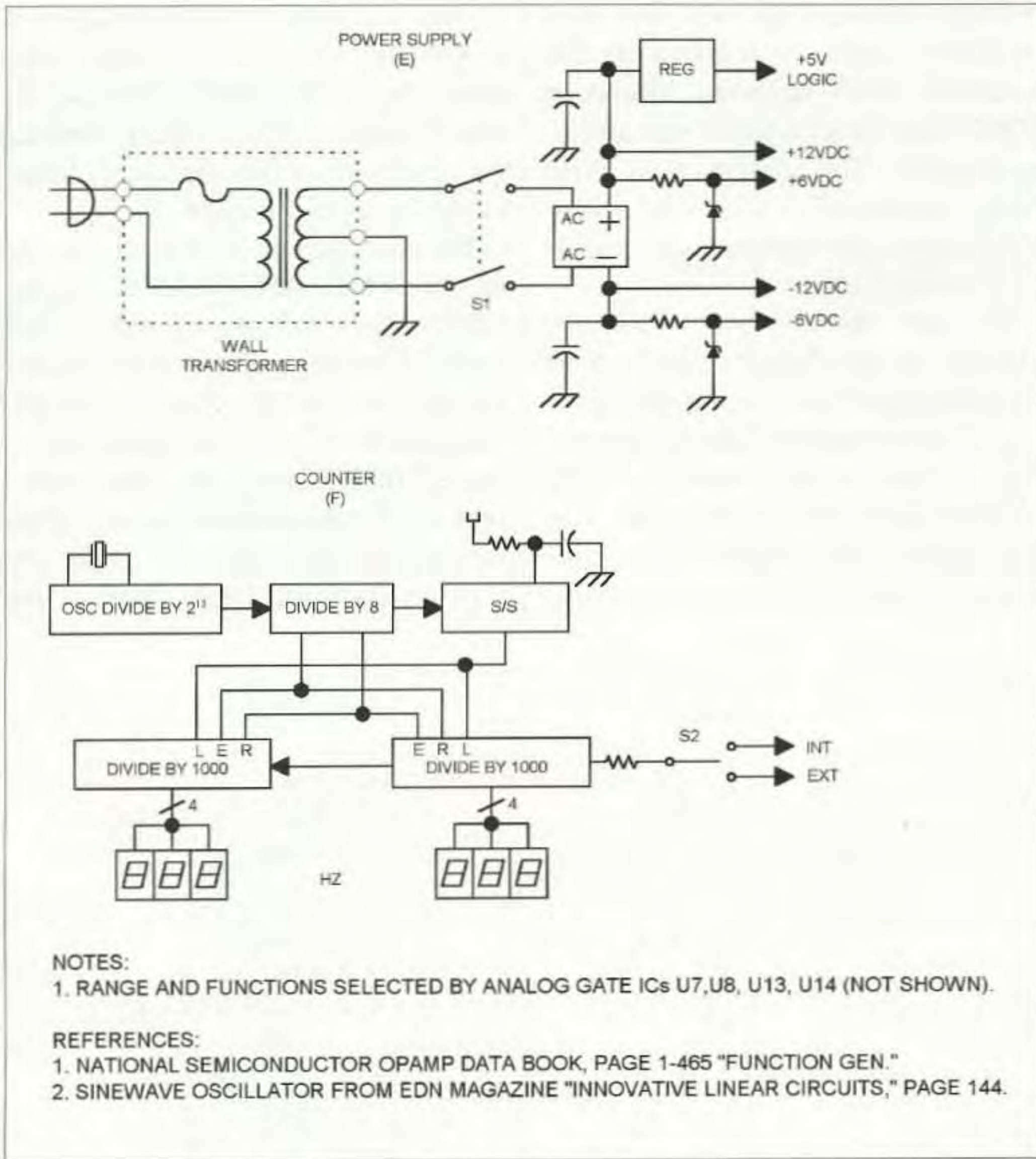


Fig. 1. Simplified schematics (continued).

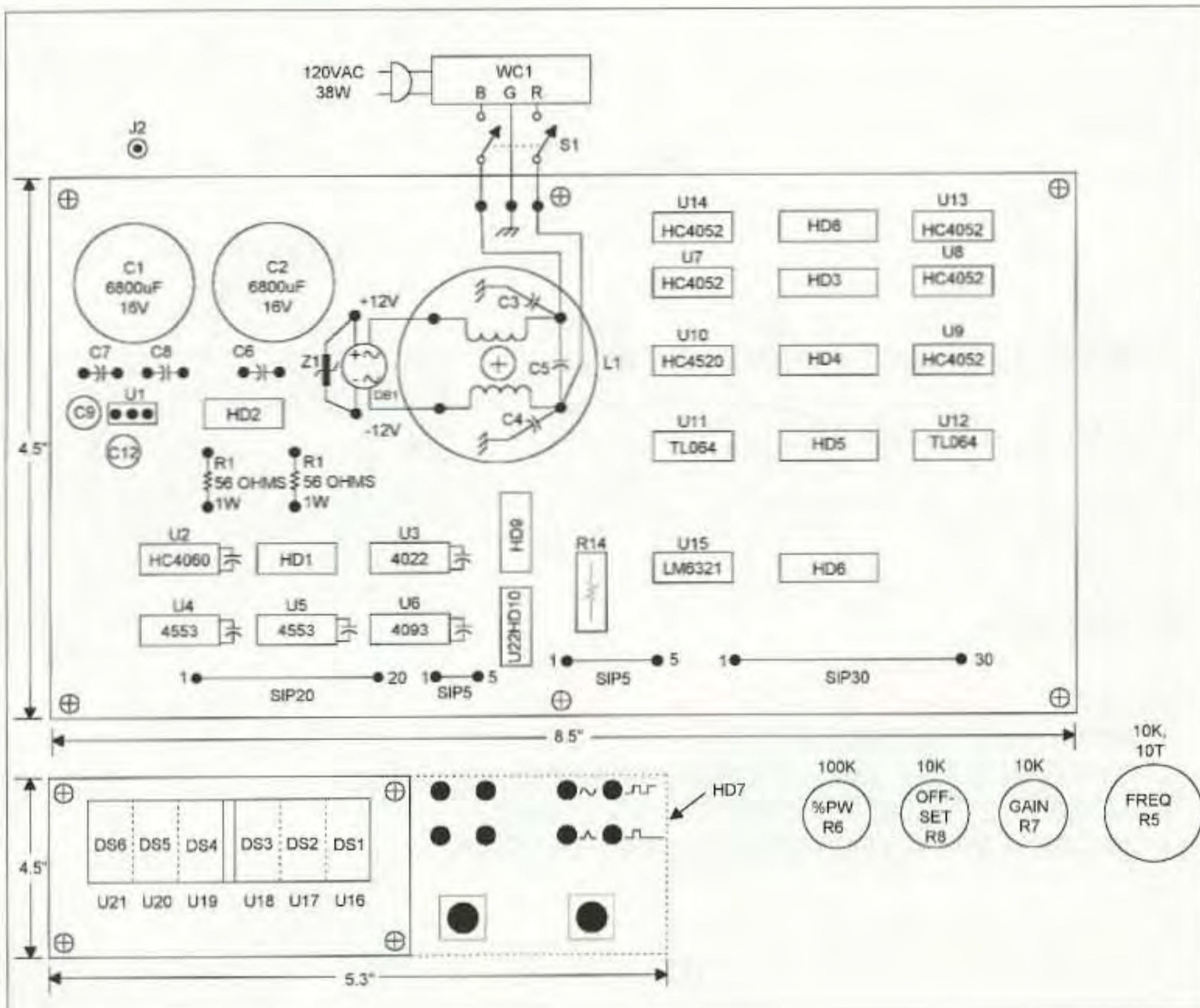



Fig. 2. Component locations.

priority was to get the best sine wave oscillator I could. My requirement was a 0.01% total harmonic distortion (THD) sine wave, which I was able to accomplish. This design is a Wien bridge arrangement with four selectable ranges with continuously variable overlapping bands.


The next absolute was to have an onboard digital counter circuit. It must be inexpensive and reasonably accurate, with an external input for measuring a test circuit frequency. The counter circuit is a watch crystal time base which is divided down to provide a one second window as a counting

period. The second one second period is used for the latch and reset functions. The 0.5 Hz is well within the tolerance required to accurately measure the one hertz to one megahertz range of the function generator.

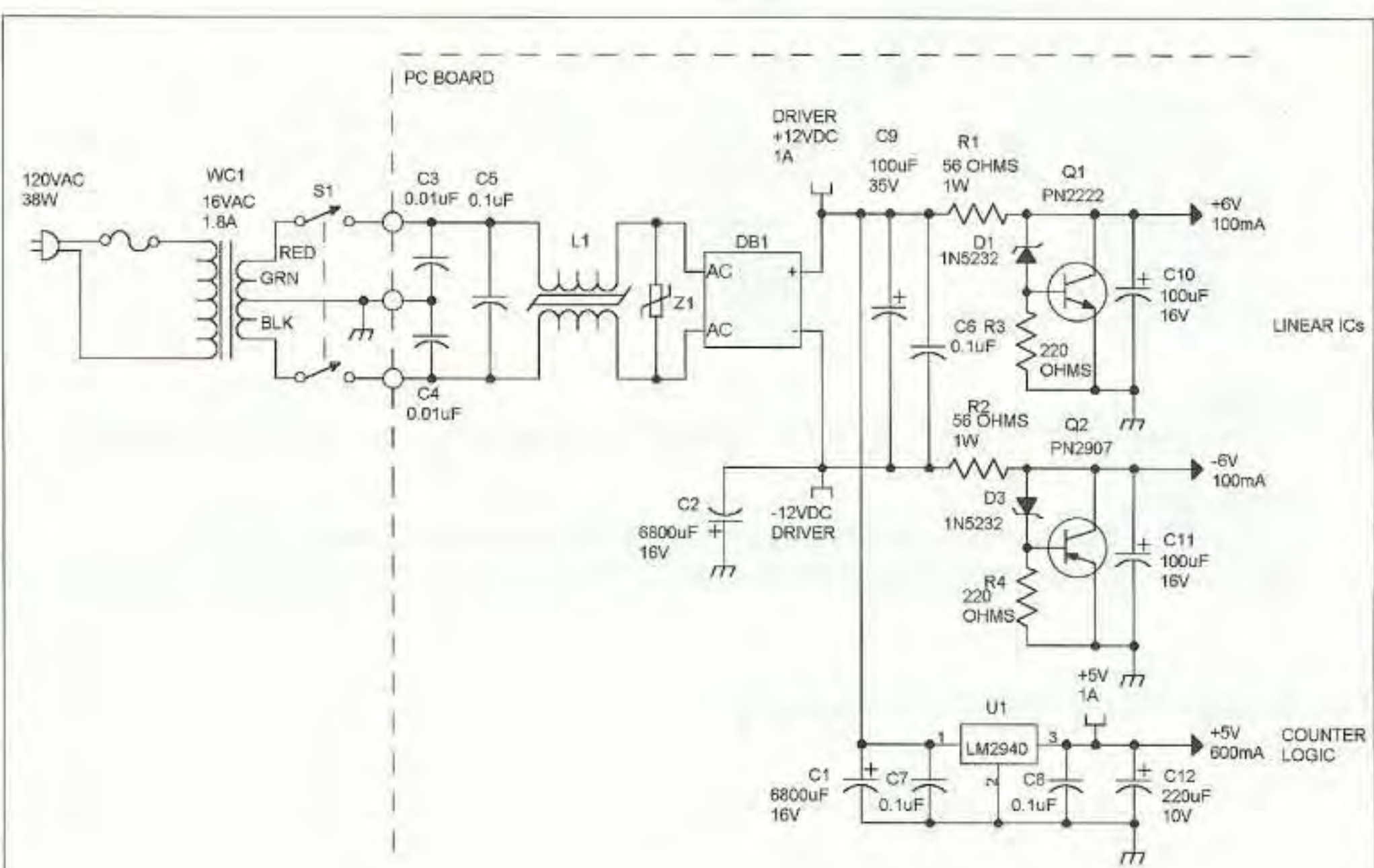The six stage counter circuit consists of two MC-14553 CMOS digital DIP16 ICs which provide the six decades of counting. The output is multiplexed so as to have a small, inexpensive IC package. These multiplexed BCD outputs are then loaded into the latching and decoding seven segment displays that are made by Hewlett Packard. These displays are



(A)

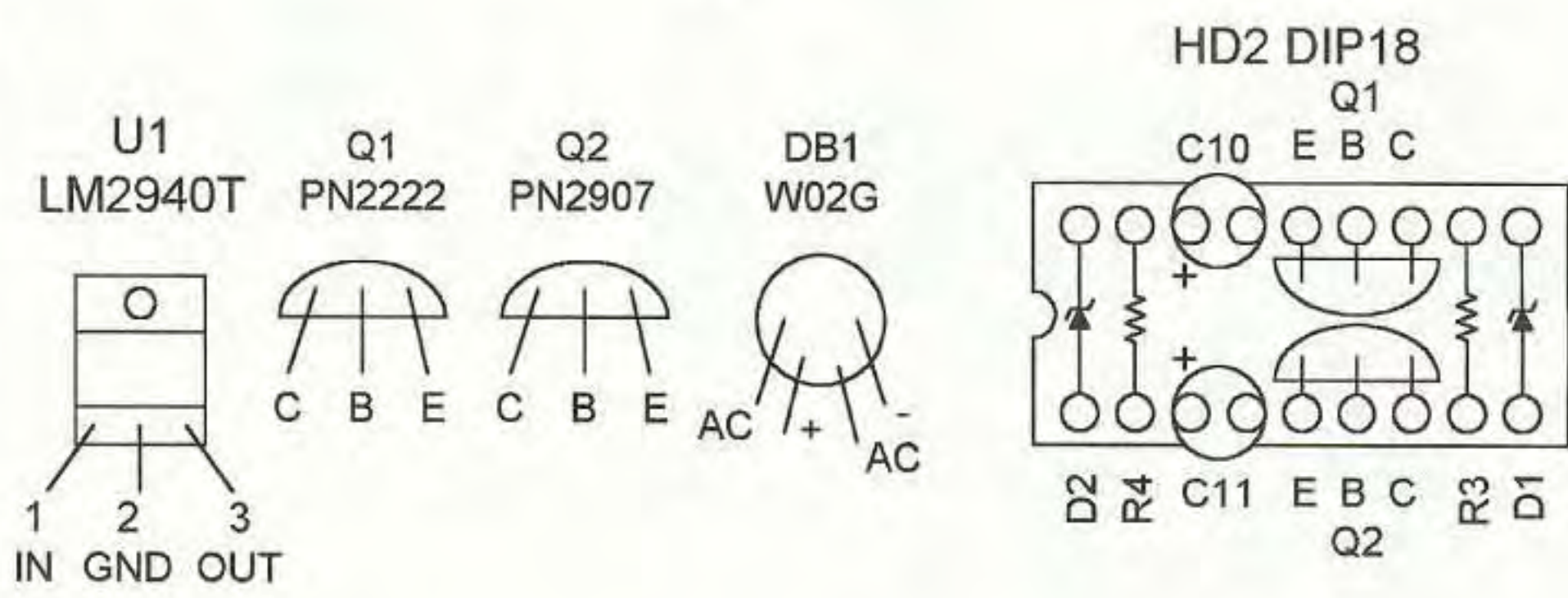

- NOTES:
1. WC1 = 16VCT @ 1.8A (UL/CSA).
 2. SHUNT REG OUT ON AUTHOR'S UNIT +6.25V AND -6.25V.
 3. C7, C8, C12 SOLDERED DIRECTLY TO U1 PINS.
 4. C3-C6, Z1, WC SOLDERED DIRECTLY TO L1 PINS.

(B)

Fig. 3. Schematic, power supply section.

1	ENC	Ten-Tec Enclosure	(TEN-TEC-JW10)	\$ 16.00
6	---	0,75" (#4) Stand-Off	(Hosfelt-28-146)	1.50
1	*WC	15VAC-1,8A (CT)Wall Xfmr	(Hosfelt 56-781)	2.95
1	U1	LM2940CT-5 5V-1A Reg IC	(Jameco-107182)	1.29
1	U2	HC4060 CMOS IC DIP	(Mouser-511-M74HC4060)	.64
1	U3	4022 CMOS IC DIP	(Mouser-511-4022)	.66
2	U4,U5	4553 CMOS IC DIP	(Jameco-13709)	5.90
1	U6	4093 CMOS IC DIP	(Jameco-14300)	.29
5	U7-9,13,14	HC4052 CMOS IC DIP	(Mouser-511-M74HC4052)	4.20
1	U10	HC4520 CMOS IC DIP	(Mouser-511-M74HC4520)	.62
3	U11,12,22	TL064ACN Quad OPamp IC	(Mouser511-TL064ACN)	3.00
1	U15	LM6321 Linear IC	(Digi-Key LM6321N)	5.28
6	U16-U21	HP-5082-7300 7Seg IC	(Jameco-173833)	29.70
1	BZ1	Bezel-- 3,5"--Black	(DigiKey-PRD250B)	2.00
1	BZ2	Bezel-- 3,5"--Red Lens	(DigiKey-PRD250R)	1.60
1	BZ3	Bezel-- 3,5"--Clear Lens	(DigiKey-PRD250W1)	1.60
3	J1,J3,J4	Jack SMA Bulkhead Fem Coax	(Jameco-153285)	7.50
1	J2	Jack (Test Point)	(Any)	.25
1	Q1	PN2222 NPN Tran	(Jameco-178511)	.16
1	Q2	PN2907 PNP Tran	(Jameco-178520)	.16
1	DB1	200V-1,5A Diode Bridge	(Mouser-625-W)2G)	.35
2	D1,D2	1N5232B Zener Diodes	(Jameco-179055)	.14
2	D3,D4	DELETE		---
4	D5-D8	T-1 (3mm) Green LED	(Jameco-34606)	.60
4	D9-D12	T-1 (3mm) Red LED	(Jameco-94529)	.76
8	BZ4-11	3mm LED Bezels (LH-100)	(Jameco-95513)	.96
1	PCB	Perf PC Board 4.5x17"	(Mouser-574-169P44)	10.59
3	B1,2,3	#1240 Lamp T1 Wire Leads	(Hosfelt-25-290)	1.05
1	X1	32768 HZ Watch Crystal TF2	(DigiKey X801)	.30
8	---	DIP16 WW (Mach Pin)Socket	(Hosfelt-21-174)	4.00
9	---	DIP18 WW (Mach Pin)Socket	(Hosfelt-21-180)	4.50
2	---	DIP24 (W) WW (MachP)Socket	(Hosfelt-21-184)	.70
8	---	DIP24 (S) WW (MachP)Socket	(Hosfelt-21-183)	2.80
2	SIP-1,2	SIP40 WW Header	(Jameco-160881)	.80
1	---	Decal Kit (Radio Shack)	(RS-270-201)	3.00
2	C1,C2	6800MF-16V-Elect-Cap(18x36)	(Jameco-31510)	2.18
4	C3,4,21,22	0,01MF-50V-Mono-Cap	(Mouser-21RX410)	.44
1	C9	100MF-35V Elect Cap (8X11)	(Jameco-93551)	.19
2	C10-C11	100MF-16V Elect Cap (6x5)	(Jameco-94431)	.18
1	C12	220MF-10V Elect Cap	(Digikey 140-MLRL10V220)	.17
6	C13-C17	0,1MF-50V Mono Cap	(Mouser-21RZ310)	.48
21	C5-C8	0,1MF-50V Mono Cap	(Mouser-21RZ310)	1.72
	C23-C37,C50,C52			
2	C19	100PF-50V-NPO-Mono Cap	(Mouser-21RD610)	.10
2	C20,C51	10PF-50V-NPO-Mono Cap	(Mouser-21RD710)	.20
4	C38-C41	0,002MF-50V-5%-Styrene Cap	(Mouser-23PW220)	.96
2	C42,C46	0,001MF-50V-5%-Styrene Cap	(Mouser-23PW210)	.22
1	C18	0,1MF-50V-Mono Cap (Axial)	(Hosfelt-15-407)	.08
2	C43,C47	0,01MF-50V-5%-Styrene Cap	(Mouser-23PW310)	.38
2	C44,C48	0,22MF-50V-Elect. Cap	(Mouser-140-L50V,22)	.09
2	C45,C49	4,7MF-16V-Elect Cap	(Mouser-140-L16V4,7)	.09
1	L1	Dual 8,2MH Choke(PE96180)	(Hosfelt-18-129)	.35
1	Z1	11VAC/18VAC Clamp MOV	(Jameco-190449)	.25
2	R1,R2	56-5%-1W-MOF-Resistors	(Mouser-281-56)	.38
2	R3,R4	220-5%-0,25W-CF-Res	(Jameco-30470)	.10
1	**R5A,R5B	10K-10T-Dual POT(Bourns#84A2DB28J15/J15)		---
	Alternate	10K-1T-Dual POT	(Mouser-31VW401)	2.10
	Optional	15:1 Mechanical Dial	(Mouser-5940-16111)	12.00
1	R6	100K-1T-POT	(Mouser-31CN501)	1.02
2	R7,R8	10K-1T-POT	(Mouser-31CN401)	2.04
2	R9,R27	22K-5%-0,25W-CF-Res	(Jameco-30453)	.10
1	R14	10K-15T-T-POT (Bourns-3006)	(Hosfelt-380135)	.85
1	R10	15M-20%-0,25W-CF-Res	(Mouser-291-15M)	.10
3	R15,R16	1K-5%-0,25W-CF-Res	(Jameco-29663)	.15
	R20,R22			
2	R18,R19	47K-5%-0,25W-CF-Res	(Jameco-31149)	.10
1	R12	2200-5%-0,25W-CF-Res	(Jameco-30314)	.05
3	R13,32,33	150-5%-0,25W-CF-Res	(Jameco-30162)	.15
3	R17,24,25	330-5%-0,25W-CF-Res	(Jameco-30867)	.15
1	R21	33-5%-1W-MOF-Res	(DigiKey-P33W-2BK)	.30
3	R22,23,26	10K-5%-0,25W-CF-Res	(Jameco-29911)	.15
2	R28,R31	56K-5%-0,25W-CF-Res	(Mouser-291-56K)	.10
3	R11,29,30	100K-5%-0,25W-CF-Res	(Jameco-29997)	.15
2	R35,R36	1200-5%-0,25W-CF-Res	(Jameco-29735)	.10
1	R35	1800-5%-0,25W-CF-Res	(Jameco-Bulk)	.05
1	R37	560-5%-0,25W-CF-Res	(Jameco-31376)	.05
0	R38	DELETE		
8	R39-R46	CAL Res 5%-0,25W,CF-Res	(Any)	.40
1	---	Knob-0,25"-Black (Large)	(Jameco-138481)	1.25
3	---	Knob-0,25"-Black (Small)	(Jameco-162499)	3.75
1	RN*	100Kx8-2%-DIP16-RNET	(Jameco-108644)	.60
2	SW1,2	PB Switches (KRS-1273-B)	(Jameco-155379)	.80
2	SW1,2	PB Caps (KRS-CAP-B)	(Jameco-155408)	.30
1	S1	DPDT (2-Pos)SubMini Toggle	(Jameco-75977)	1.29
1	S2	SPDT (2-Pos)SubMini Toggle	(Jameco-75969)	1.15
1	S3	SPDT (3-POS)SubMini Toggle	(Jameco-72557)	1.15
1	---	0,25" Rubber Gromet	(Any)	.10
8	---	0,25" Nylon Standoffs #4 screws	(Hosfelt)	

APPROX. TOTAL: \$ 132.00

NOTE:

- (1) ACE Hardware #1003979 Almond Spray Paint (15oz) \$3.00
- (2) Minwax Polyurethane #33050 Clear Gloss Spray (11oz) \$4.00
- (3) * WC is GroupWest #57A-15-1800CT (38W) Wall Transformer.
- (4)** Author used Bourns 10turn pot because it was available
Tests show Mouser part is O.K.(Optional) 15:1 Dial.
- (5) Out/In=6FT Coax with male SMA's (Jameco-159450) \$5.75.

Table 1. Bill of materials.

high-quality, dot matrix hybrid types which are very compact and high-contrast. They are small enough that three digits can be handled by a standard DIP24 socket. I use the least significant digit's decimal point to show the

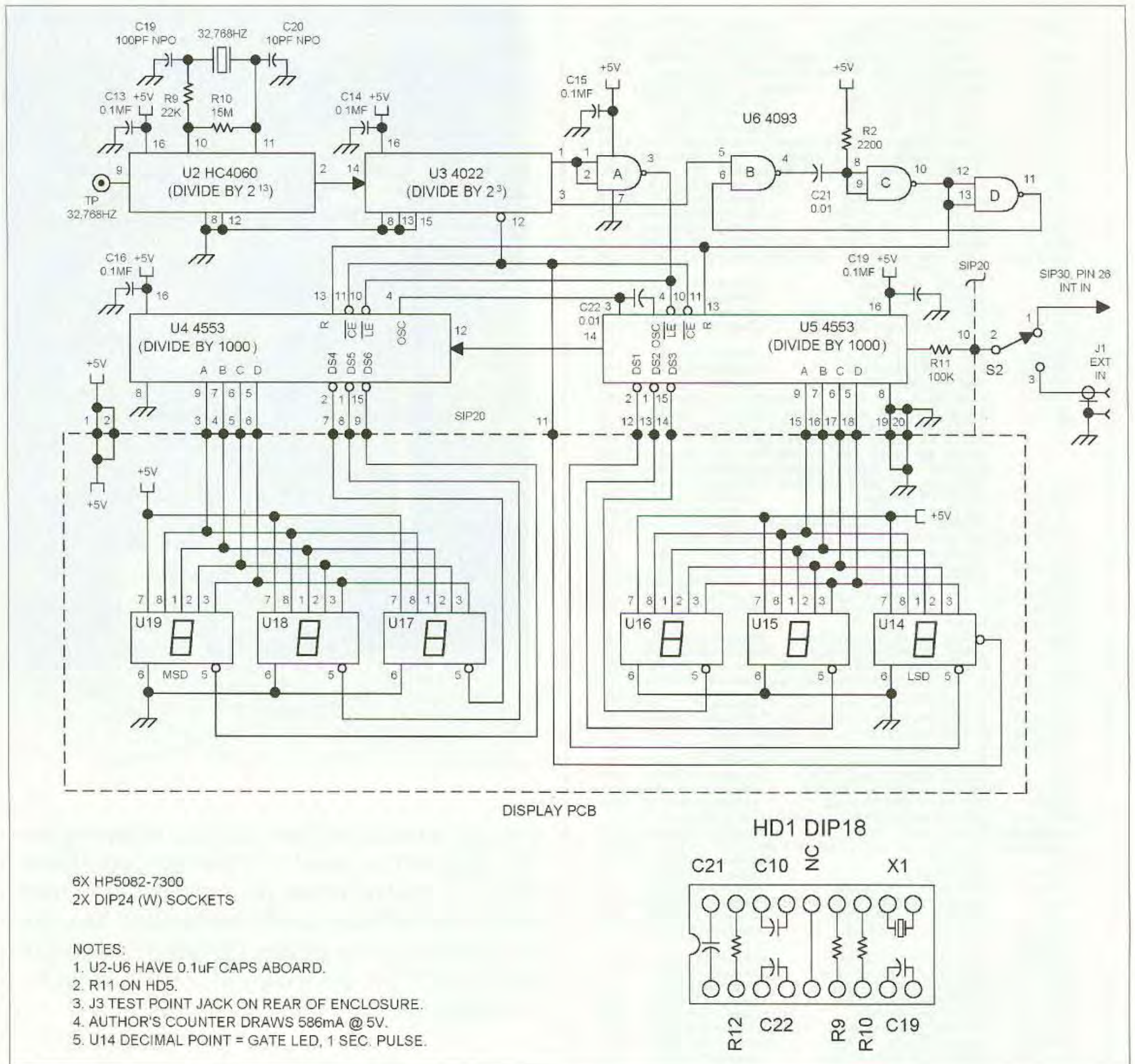


Fig. 4. Schematic, counter section.



Photo A. The completed function generator with wall converter.

count gate action. Since upon power-up we do not know what the oscillator time base chain has in it, a couple of seconds is sometimes required to clear and get the first one second count period. The flashing decimal point indicates that everything is working correctly.

The next section of the generator is the triangle, square, and pulse generator. Since we do not normally need an extremely low THD for these functions, a simple quad op amp IC was used to perform these functions. An IC such as the 8038 could have been used but again, something a little better than

the 1% specified (THD) was desired. So a voltage reference, Schmitt trigger, integrator, and comparator circuit was designed using a quad JFET op amp IC, TL064A. The circuit also uses a couple of analog gate ICs to do the resistor and capacitor selections. The timing resistor and capacitors are the same ones that are used in the Wien bridge sine wave oscillator. Two additional analog gate ICs were also used to select the LED indicators for range and function. These gates are selected digitally with push-button switches to a dual binary counter IC, U-10.

The multiwave output is then sent out to the gain and offset controls so that amplitude and position relative to ground can be adjusted by the user. The frequency is controlled by the ten-turn dual 10k-ohm pot, R5. The output of the generator is run through a special current mode driver IC. This IC provides 200 mA of continuous drive and is short-circuit and thermal protected. Quite a bargain at under six dollars and in a DIP-8 package!

The power supply circuit was my next concern. The use of a wall converter is most desired so as to keep the high voltage AC out of the enclosure. These wall converters or transformers are UL and CSA approved for safety and are very inexpensive. Ours brings a 15 volt centertapped winding to the PC board and is rated at 1.8 amps. This AC voltage is put through a bridge rectifier to get our POS and NEG 12 VDC at over 1 amp. Note that at 1.8A the voltage would be about 8 VCT, but since we have a maximum of 12 VDC @ 200 mA requirement, we do not level. The two shunt regulator circuits draw another 200 mA to achieve the POS and NEG 6 VDC power for the

Continued on page 16

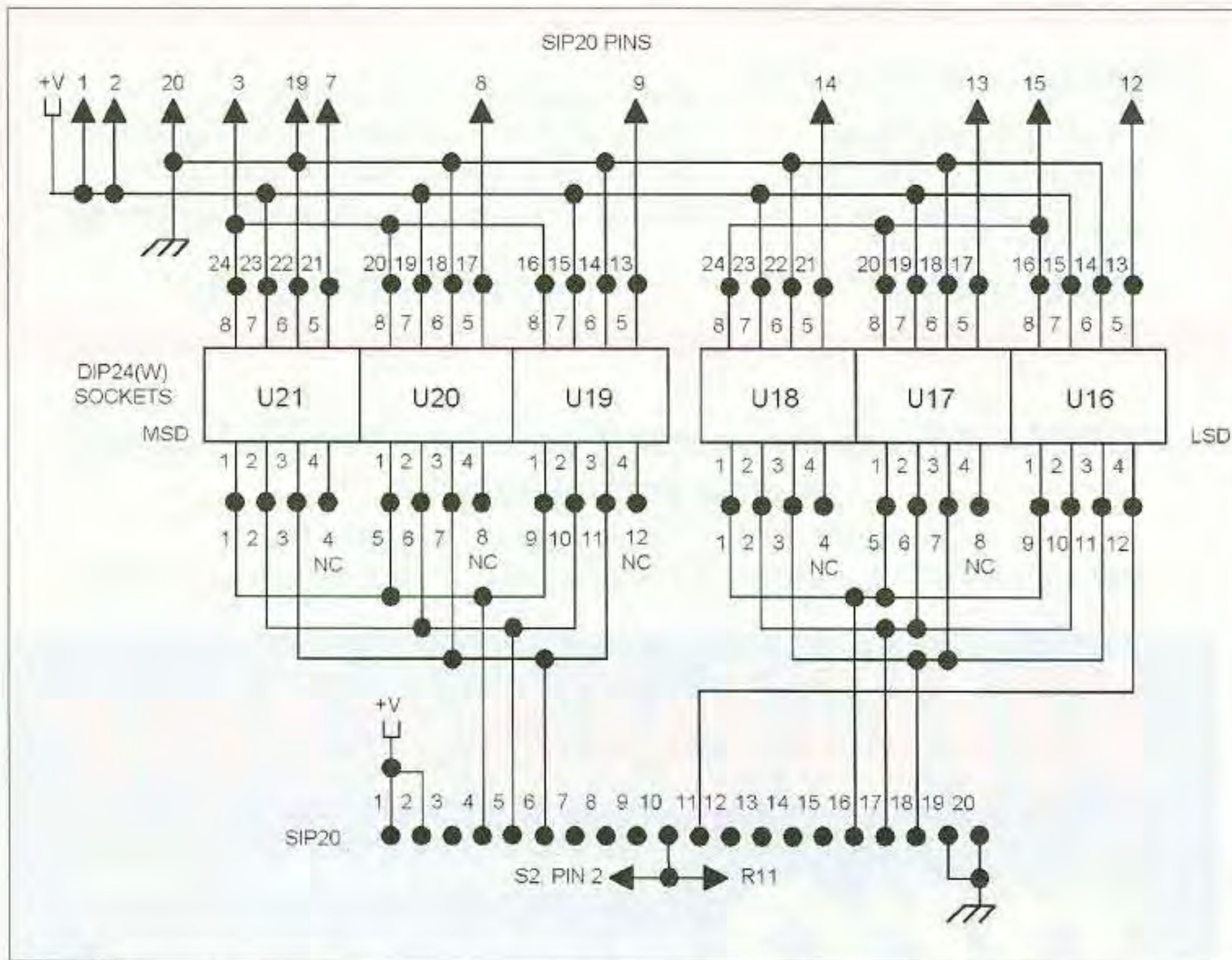


Fig. 5. Schematic, counter display section.

Commercial-Quality Function Generator

continued from page 15

op amps and CMOS logic components.

Now, the digital logic TTL display hybrids which draw about 100 mA each will need that high-current 5V source. I took the +12VDC line and put the U-1 series voltage regulator IC on it for the 5VDC 600 mA requirement. The regulator IC LM-2940-5 is a low dropout type which can work down to the one half volt differential point, so no problems in our application. The 5 VDC 600 mA display requirement does

not throw our bridge rectifier circuit out of balance. The regulator is rated for 1 amp, so 600 mA does not exceed its specification, but do expect a little heat on the TO-220 package running at about four watts. No heat sink is required!

Some folks might ask why the shunt 6V regulators instead of the series ICs? Well, we find that transients, noise and such, will not get through as sometimes happens with series regulators. The use of a dual 8 mH choke L-1 is to eliminate the common mode parts of that power line stuff!

Now, we look at how to put it together. No etched and drilled PC board

is available to my knowledge. There does not seem to be an interest in that for this project. I chose to use wire-wrap technology, as always, with this project. The use of machine pin-type wire-wrap sockets to accommodate both ICs and passive components works very well. I also use SIP (single-in-line) wire-wrap binding posts for the termination of wires. These wires go between boards, controls, switches, and the like.

I chose my usual Ten-Tec enclosure and PMI plastic display bezel so that we can get a good professional looking instrument. All of the connectors, switches, and test lines are the sub-mini types. They look and work good, and the cost is very reasonable.

I added an additional two Wien bridge oscillators to provide an SSB test circuit. This is a 700 and 1900 Hz dual tone source. When you put the signals into the microphone jack of an SSB transmitter, you will have the required envelope test to check the rig and linear amplifier for linear operation.

I provided simplified schematic functions in Fig. 1. All of the component placements are also shown in Fig. 2. All of the header details are in Fig. 3. I provided a bill of materials (Table 1), the approximate cost, and the sources I found for them. A template is also provided as a guideline for the metalwork necessary on the JW-10 Ten-Tec enclosure. I recommend that a nice coat of enamel spray paint be used after the metal work. The decals make things

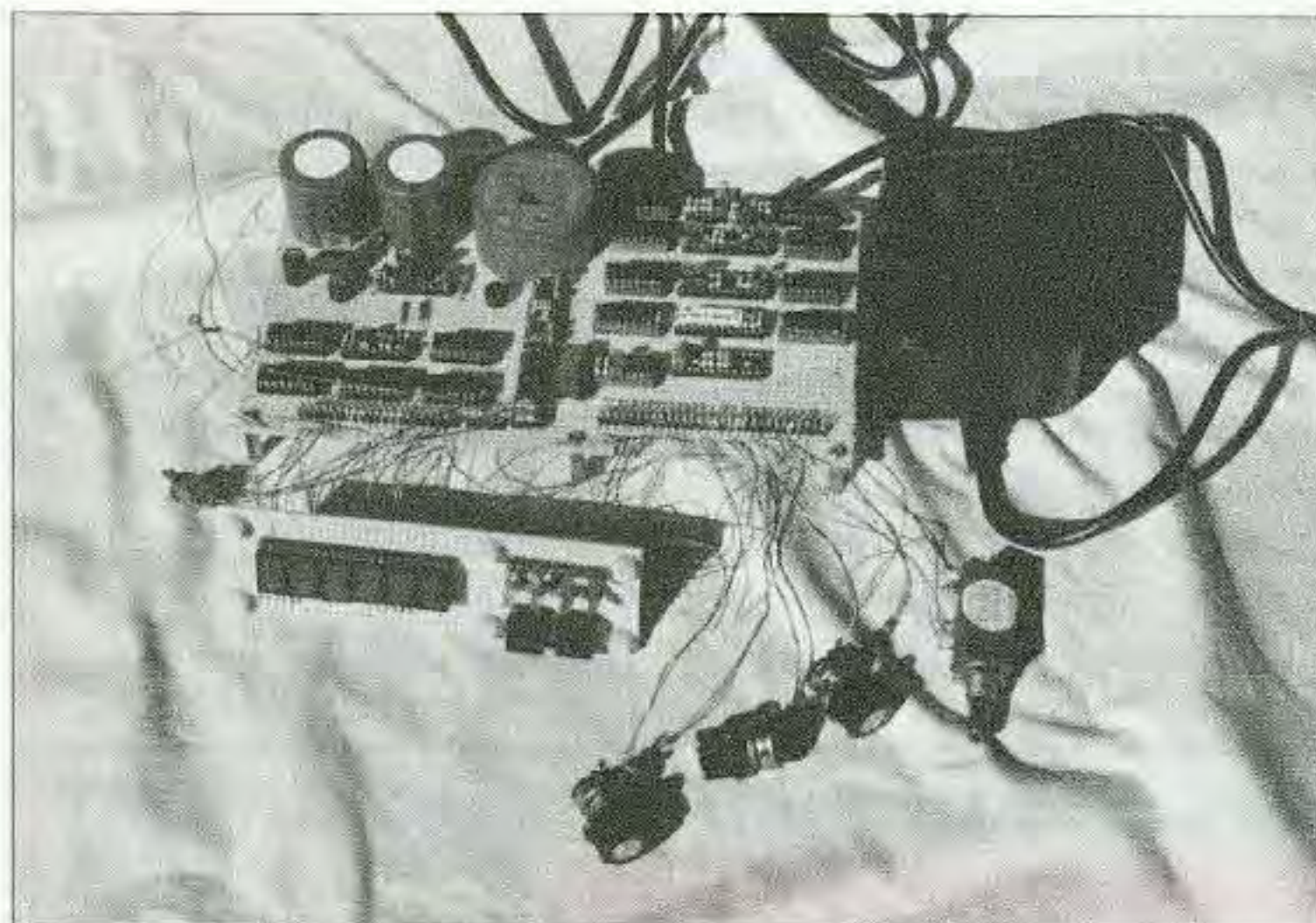


Photo B. Photo of components on PC board using wire-wrap technology.

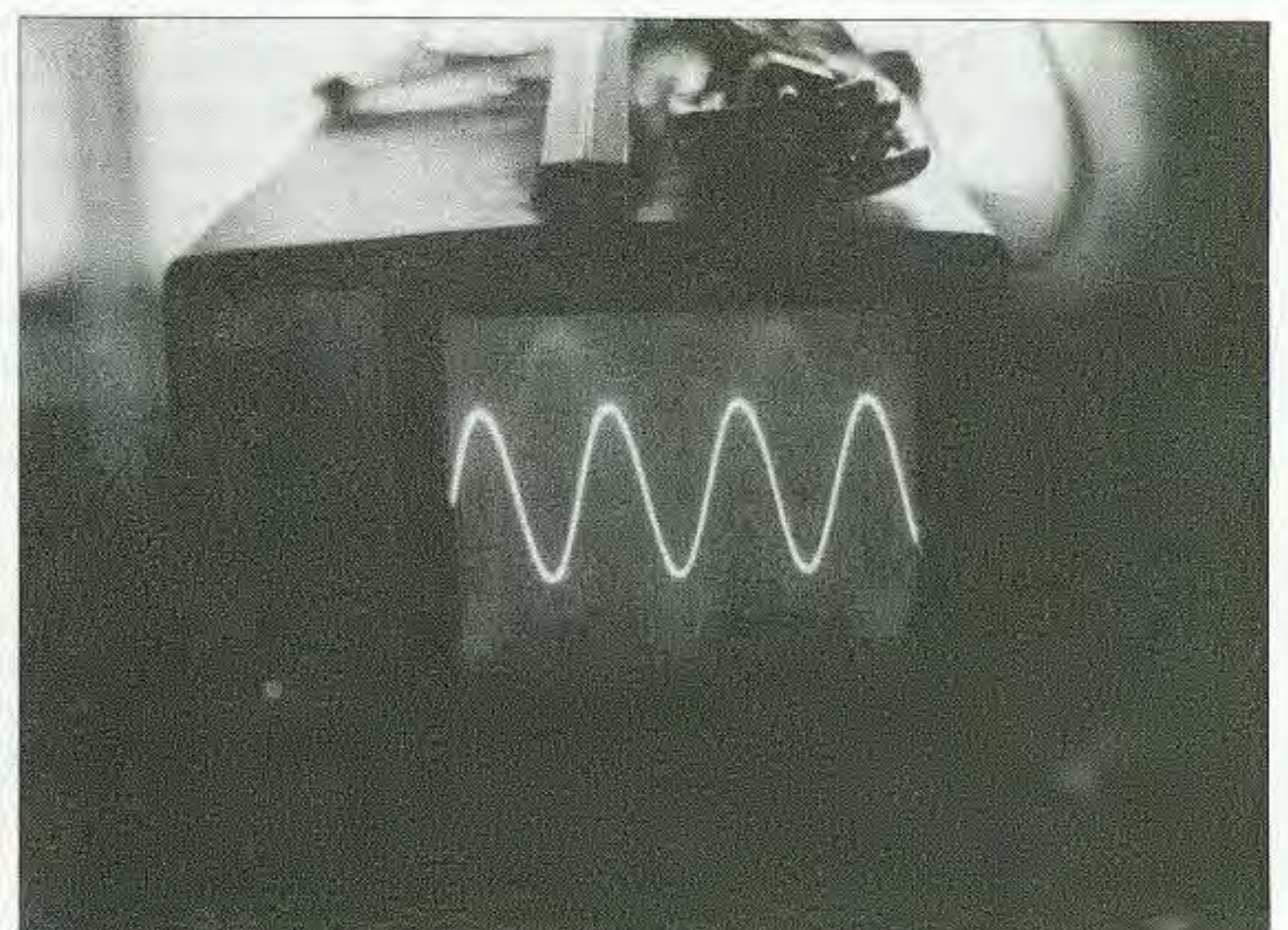


Photo C. Sine wave.

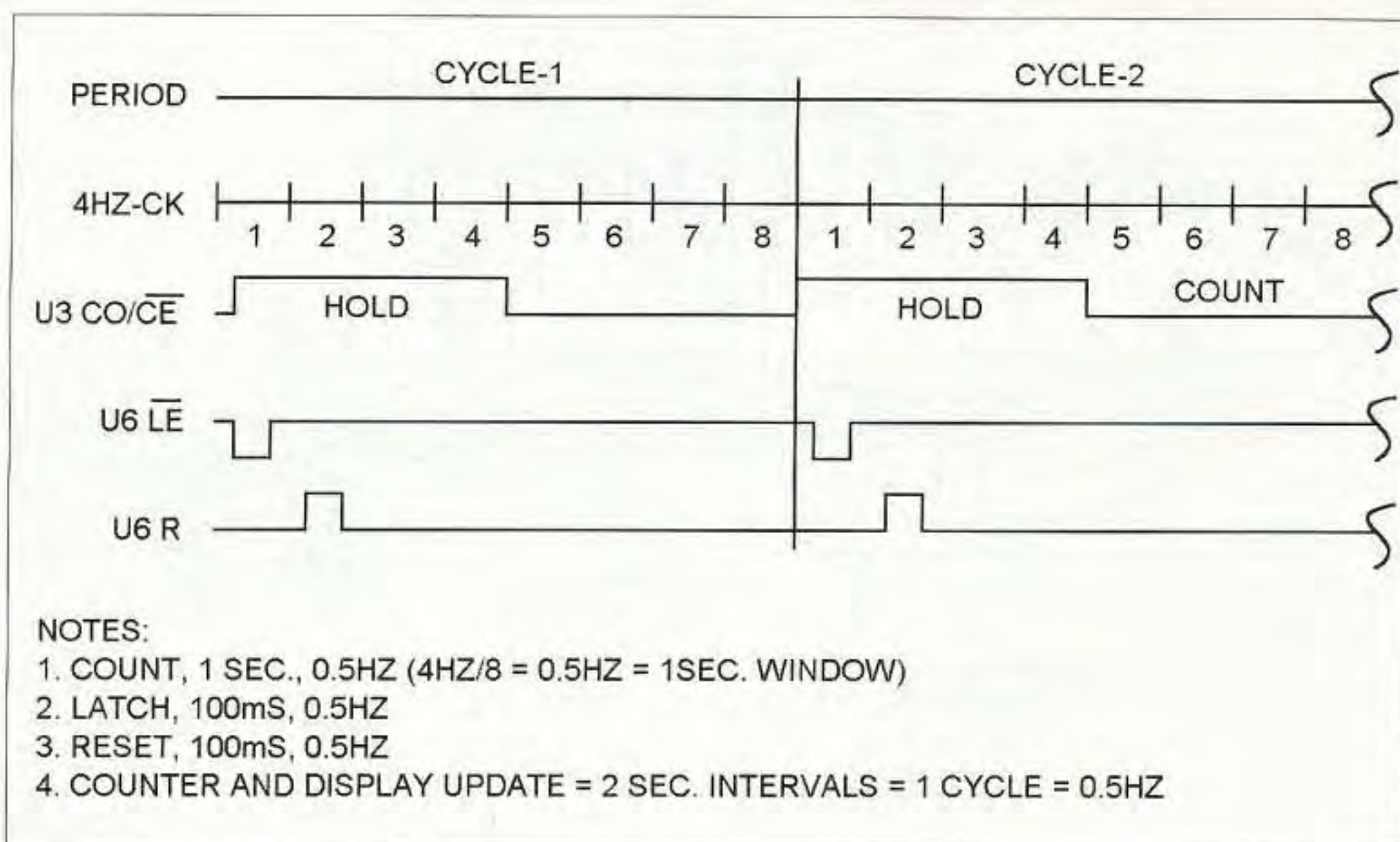


Fig. 6. Timing diagram counter section.

look very professional and can be found at your local Radio Shack or office supply stores. A couple of very

light coats of polyurethane gloss will

Continued on page 18

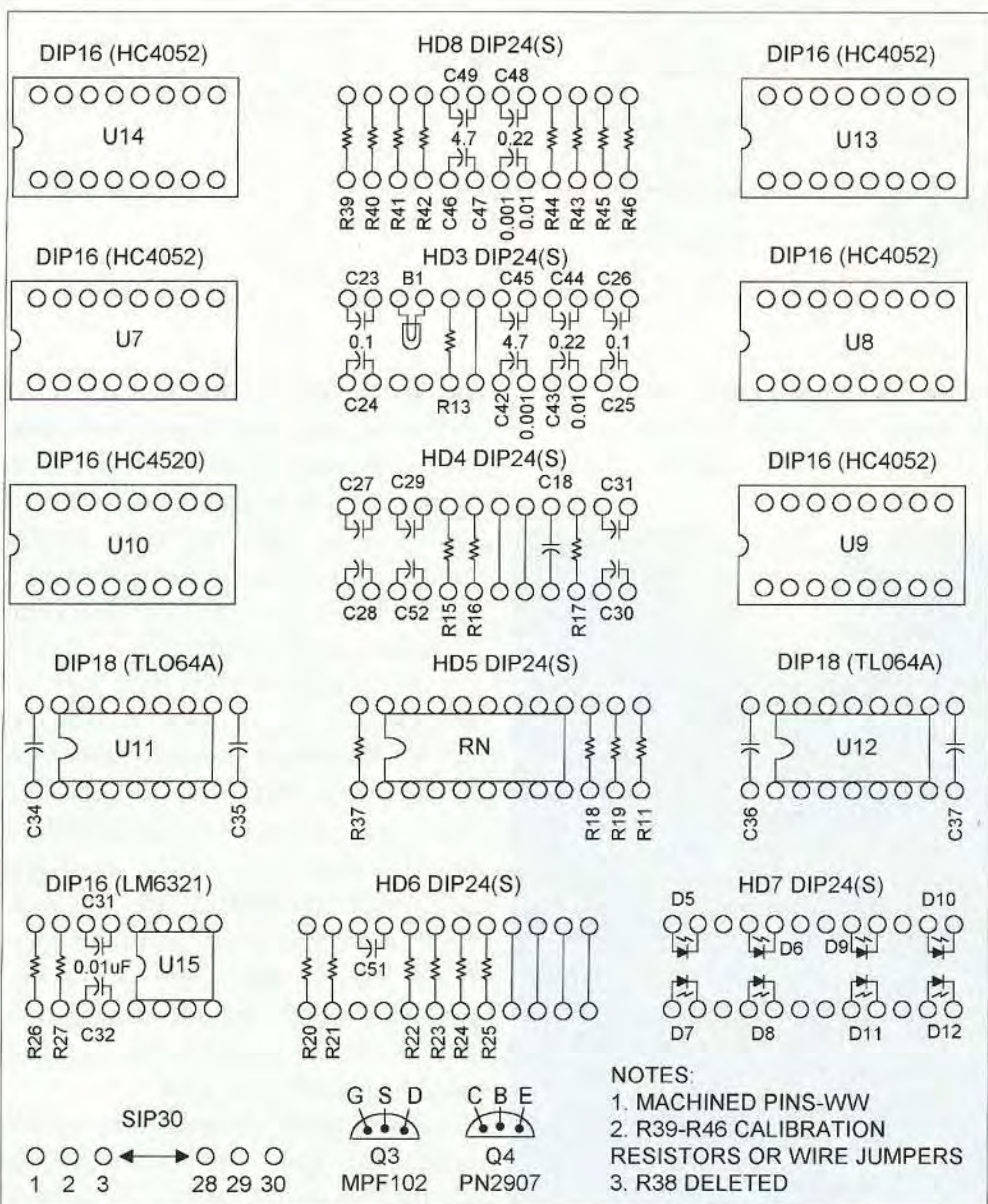


Fig. 7. Header component outline.

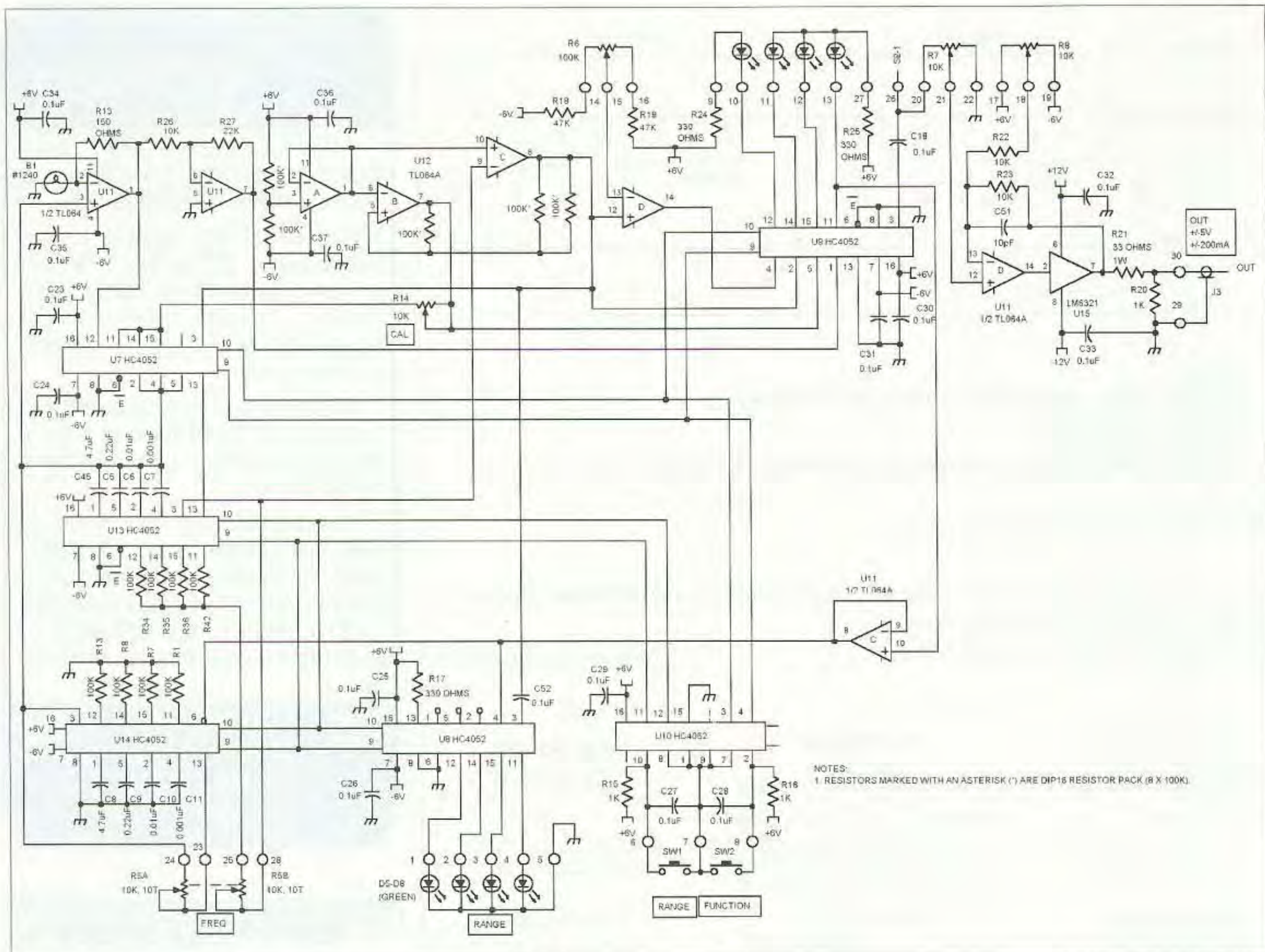


Fig. 8. Schematic, function generator section.

Commercial-Quality
Function Generator
continued from page 17

make it pretty and quite durable, and is definitely well worth the effort.

I have included a couple of photo-

graphs to show the extremely low distortion of the wave forms. Note that the fourth range position is for the sine wave only. The triangle (sweep wave), square, and pulse are not usually needed above about 20 kHz. The range can be used, but will have distortion especially on the triangle wave. A note of caution regarding the B1,2,3 #1240 incandescent lamps is that they should not be substituted with any other type if the 0.01% THD is to be expected. This type is the best I found to produce low distortion Wien bridge oscillator sine waves. This 0.01% THD was verified on a laboratory distortion analyzer. Only the zero crossover produced a slight distortion, but still it was below the 0.01% if the TL064A quad op amp IC was used.

I also included an optional time base crystal oscillator output via a jack on the back of the enclosure. The counter probe, in the external position, can be



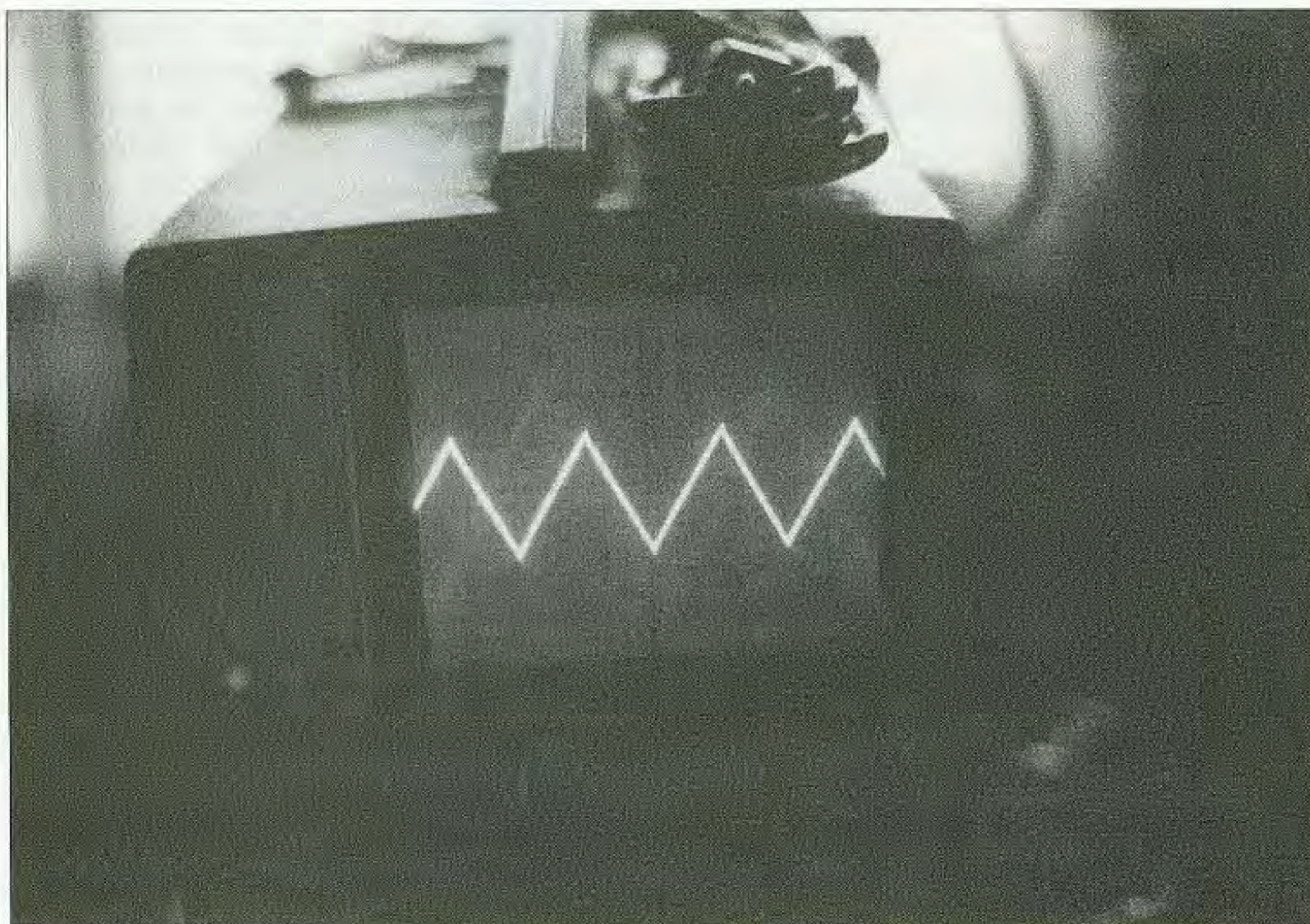


Photo D. Triangle wave.

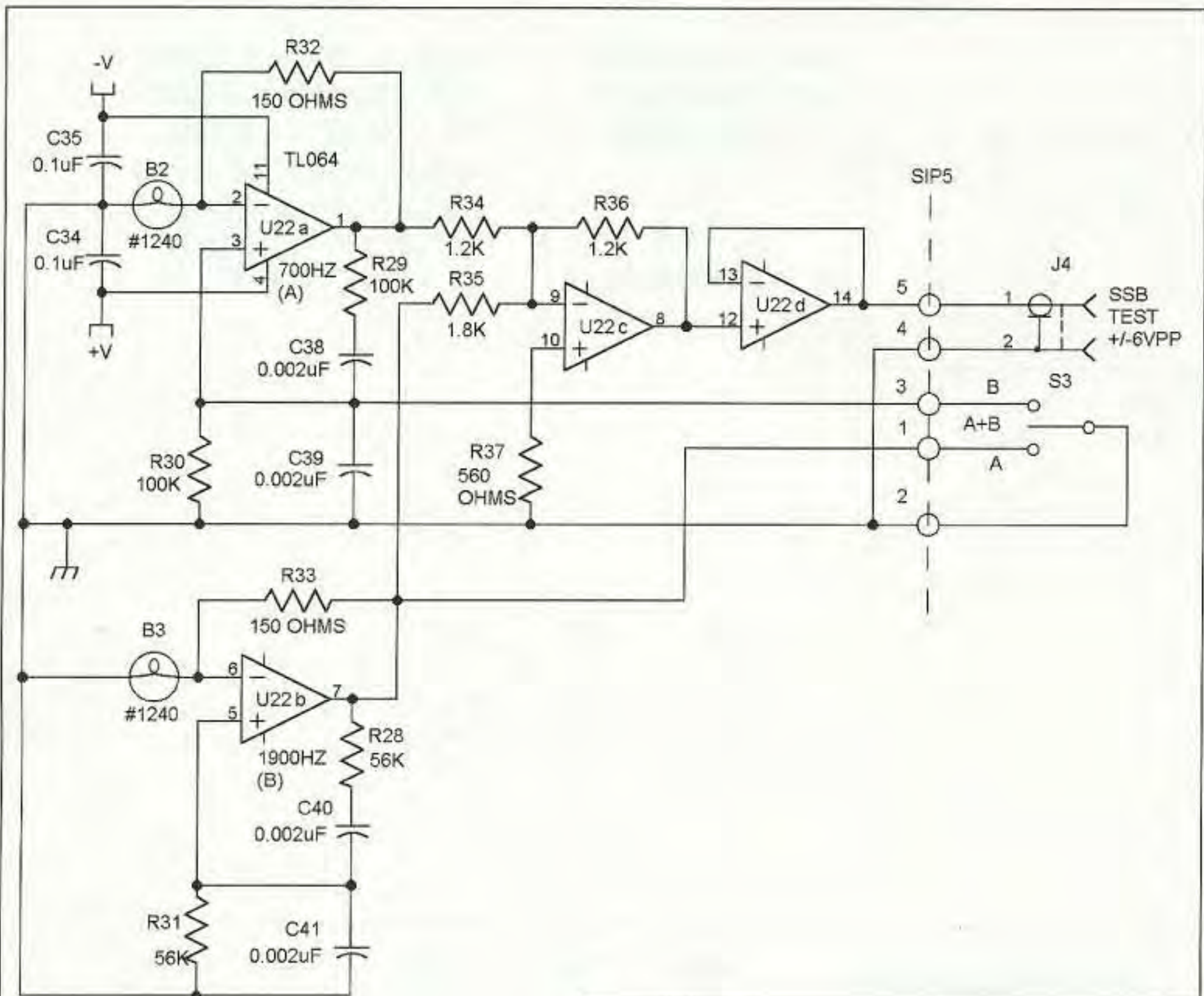

(A)

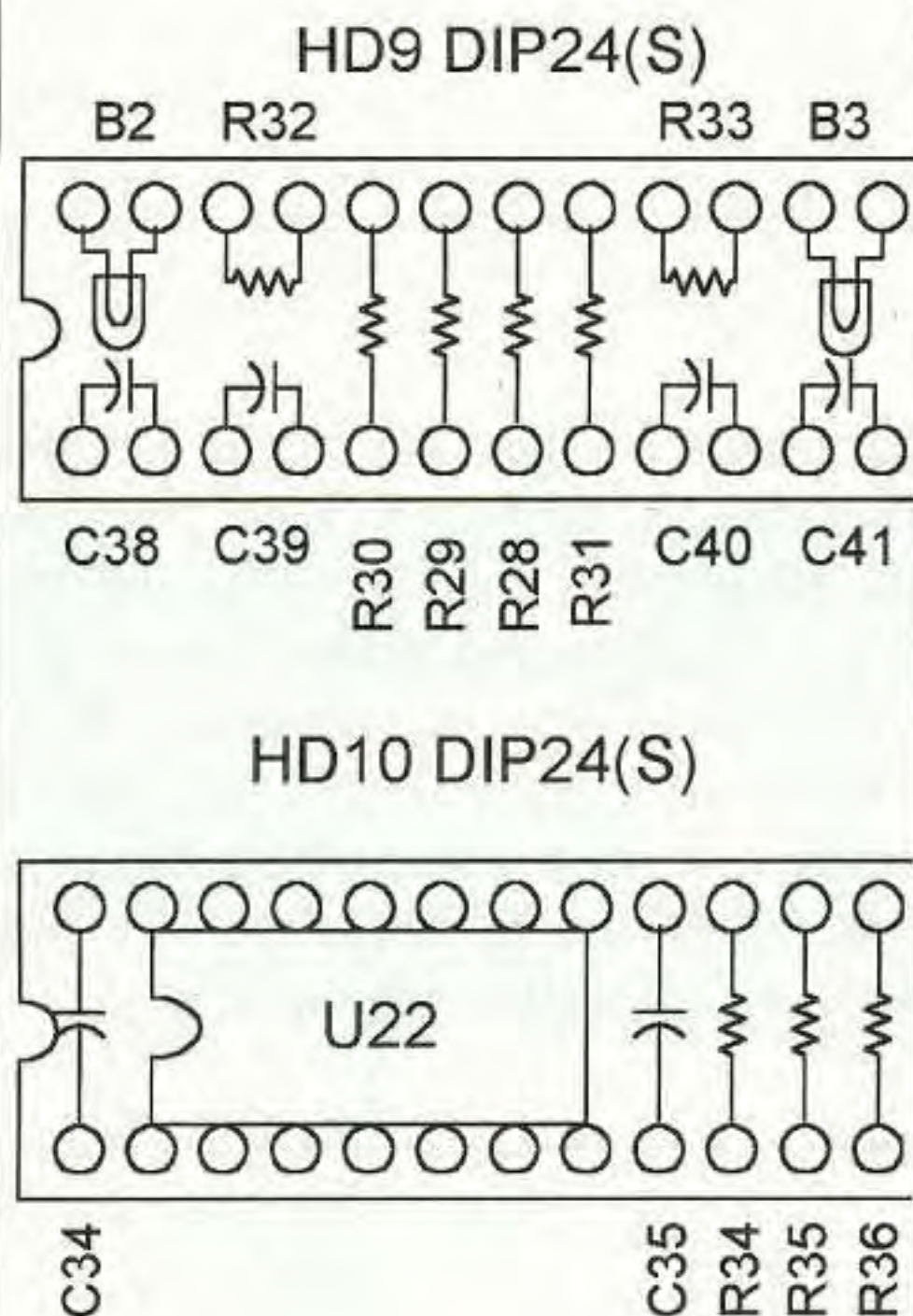

REF: 1986 ARRL HANDBOOK SECTION 25-27, FIG. 50.

(B)

Fig. 9. Schematic, SSB tone test (optional).

placed on the jack to read the time base frequency of 32768 Hz (± 1 Hz). I need to make mention of resistors R28 through R36, which are used to

FAIR RADIO SALES

ELECTRONIC MILITARY SURPLUS

40 Foot Mast Kit

AB-155 Mast Kit, includes eight self-stacking 66" long x 1.6" diameter aluminum MS-44 mast sections to make 40 foot mast. Also 4 each guy ropes MX-381 (40'), MX-382 (31'), MX-383 (50'), one MX-516 rope, 5 each MX-378 guy rings, AB-154 swivel base, six GP-101 15" stakes, and HM-1 hammer; 70 lbs sh. Used, \$225.00 plus shipping.

Electron Tubes, unused originalboxed.

4D32 Raytheon,	\$28.00	5998A Sylvania,	\$16.00
6AJ5 Tung-sol,	\$3.50	6336B Cetron,	\$45.00
24A or 27,	\$9.50	6922 ECG,	\$6.95
30,	\$16.50	7308 Amperex,	\$14.00
955 Hytron,	\$3.50	7360 ECG,	\$29.95

Allow money for shipping on merchandise.

WEBSITE: fairradio.com
 E-MAIL: fairradio@wcoil.com
 PHONE: 419-227-6573 - FAX: 419-227-1313
 2395 St Johns RD - Box 1105 Lima, OH 45802
 VISA, MASTERCARD, DISCOVER accepted
 Write for latest Catalog - Address Dept. 73

73 Ad Sales
 Call
1-800-677-8838

Amplifiers, ATU Down Converters & Hard to Find Parts

LINEAR AMPLIFIERS

HF Amplifiers
PC board and complete parts list for HF amplifiers described in the Motorola Application Notes and Engineering Bulletins:

AN779H (20W)	AN 758 (300W)
AN779L (20W)	AR313 (300W)
AN 762 (140W)	EB27A (300W)
EB63 (140W)	EB104 (600W)
AR305 (300W)	AR347 (1000W)

2 Meter Amplifiers (144-148 MHz)

(Kit or Wired and Tested)

35W - Model 335A,	\$79.95/\$109.95
75W - Model 875A,	\$119.95/\$159.95

HARD TO FIND PARTS

- RF Power Transistors
- Broadband HF Transformers
- Chip Caps - Kemet/ATC
- Metalclad Mica Caps - Unelco/Semco
- ARCO/SPRAGUE Trimmer Capacitors

We can get you virtually any RF transistor! Call us for "strange" hard to find parts!

DIGITAL FREQUENCY READOUT

For older analog transceivers

TK-1 (Wired and Tested)	\$149.95
-------------------------	----------

For detailed information and prices, call or write for our free catalog!

CCI Communication Concepts Inc.

508 Millstone Drive • Beavercreek, Ohio 45434-5840
 e-mail: cci.dayton@pobox.com
 www.communication-concepts.com

ADDITIONAL ITEMS

Heat Sink Material
 Model 99 Heat Sink (6.5" x 12" x 1.6"), \$24
 CHS-8 Copper Spreader (8" x 6" x 3/8"), \$24
 Low Pass Filters (up to 300W) for harmonics \$12.95
 Specify 10M, 15M, 20M, 40M, 80M or 160M
 HF Splitters and Combiners up to 2KW

ATU Down Converters

(Kit or Wired and Tested)

Model ATV-3 (420-450) (Ga AS - FET)	\$49.95/\$69.95
Model ATV-4 (902-926) (GaAS - FET)	\$59.95/\$79.95

- DIP switch programmable
- Miniature in size
- 37 EIA tones, 27 non-standard tones from 33.0 to 254.1 Hz included
- Reverse Burst built-in
- Easy 3 wire hookup

SS-64 CTCSS Encoder
.66" x 1.08" x .21"

SS-64 DIP Switch Programmable CTCSS Encoder \$28.95

TP-3200 Shared Repeater Tone Panel

TP-3200D Table Top Version	\$269.95 each
TP-3200RM-A Single Rack Mount version	\$279.95 each
TP-3200RM-B Triple Rack Mount version	\$279.95 each

*Holds up to three TP-3200s

- Fully enclosed CTCSS encoder
- All 32 EIA tones from 67.0 to 203.5 Hz included
- Perfect for mobile / base applications

TE-32
5.25" x 3.3" x 1.7"

TE-32 Multi-Tone CTCSS Encoder \$49.95

TP-3200 Shared Repeater Tone Panel

- 51 CTCSS Tones
- 106 DCS Codes
- Supports 157 Repeater Subscribers
- On-Line Computer Help
- Repeater CW ID
- Air Time Loading & Analysis Graphs
- Signalling Formats: CTCSS DCS & DTMF

ID-8 Automatic Morse Code Identifier
1.85" x 1.12" x .35"

ID-8 Automatic Morse Station Identifier \$69.95

Call or write to receive our full Product Catalog or visit our Web site for complete information at:
<http://www.com-spec.com>

COMMUNICATIONS SPECIALISTS, INC.

426 WEST TAFT AVENUE • ORANGE, CA 92665-4296
 (714) 998-3021 • FAX (714) 974-3420
 Entire U.S.A. (800) 854-0547 • FAX (800) 850-0547
<http://www.com-spec.com>

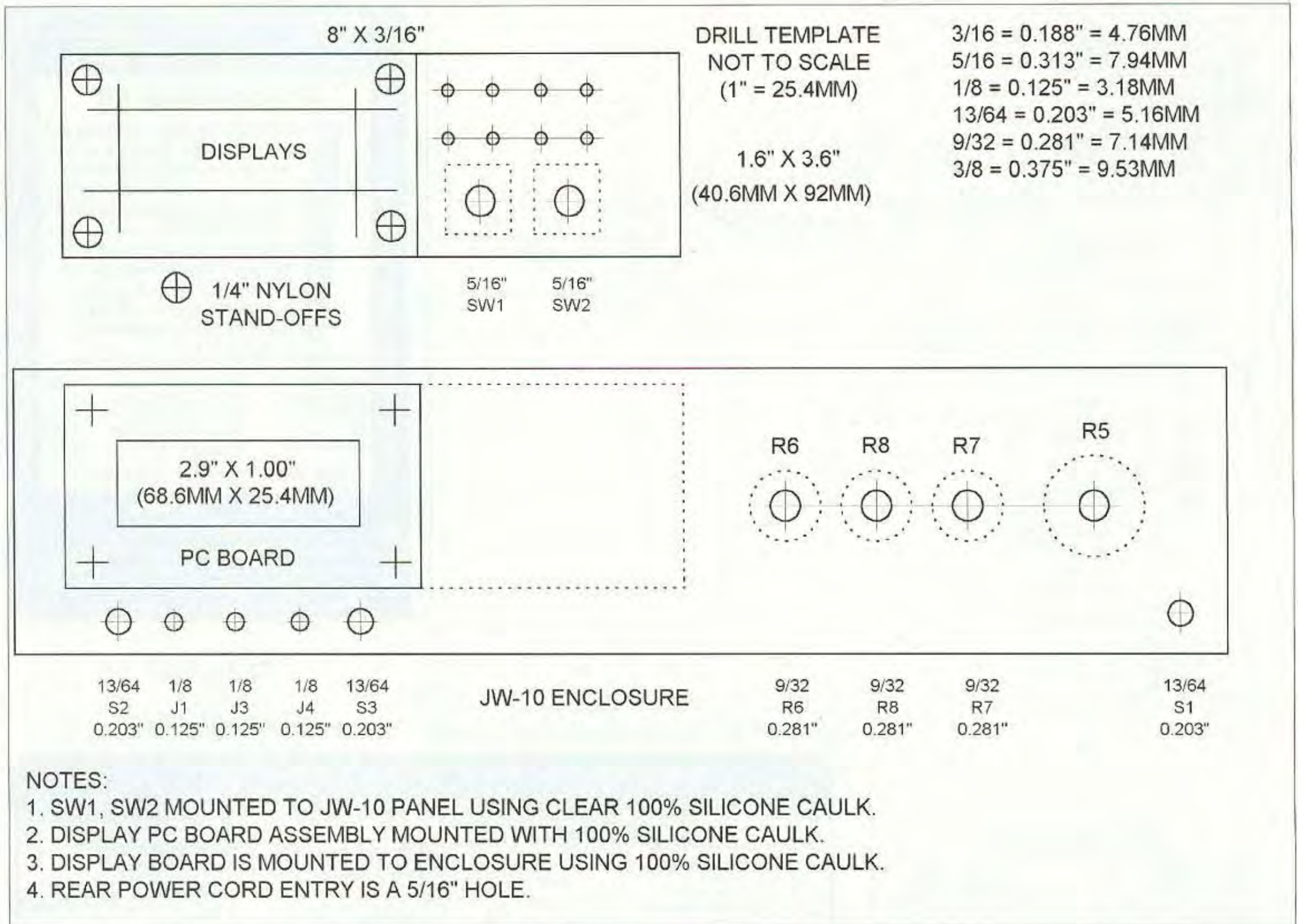


Fig. 10. Enclosure template.

calibrate the frequency ranges. We are using timing capacitors which have tolerances of 5 and 10 percent and do require a selected resistance value to set the bottom end frequency of each of the four ranges. If you do not care about the exact setting, these resistors can be omitted. Use jumper wires in their place. The triangle, square, and

pulse frequency goes from 1 Hz to about 15 kHz in the four ranges. The sine wave goes from 1 Hz to about 50 kHz in four ranges. The frequency counter measures the exact frequency in all bands, which is a marked improvement over a calibrated dial knob. The calibration is complete when you adjust the triangle wave to the same

frequency as the sine wave. Set the sine wave in the second band and read the frequency. Then move to the triangle function and calibrate it to the same frequency by adjusting R14. That is all there is to it! Well, that is about it for this project! It took quite a little bit of time to design this one, but I feel it was well worth the trouble.

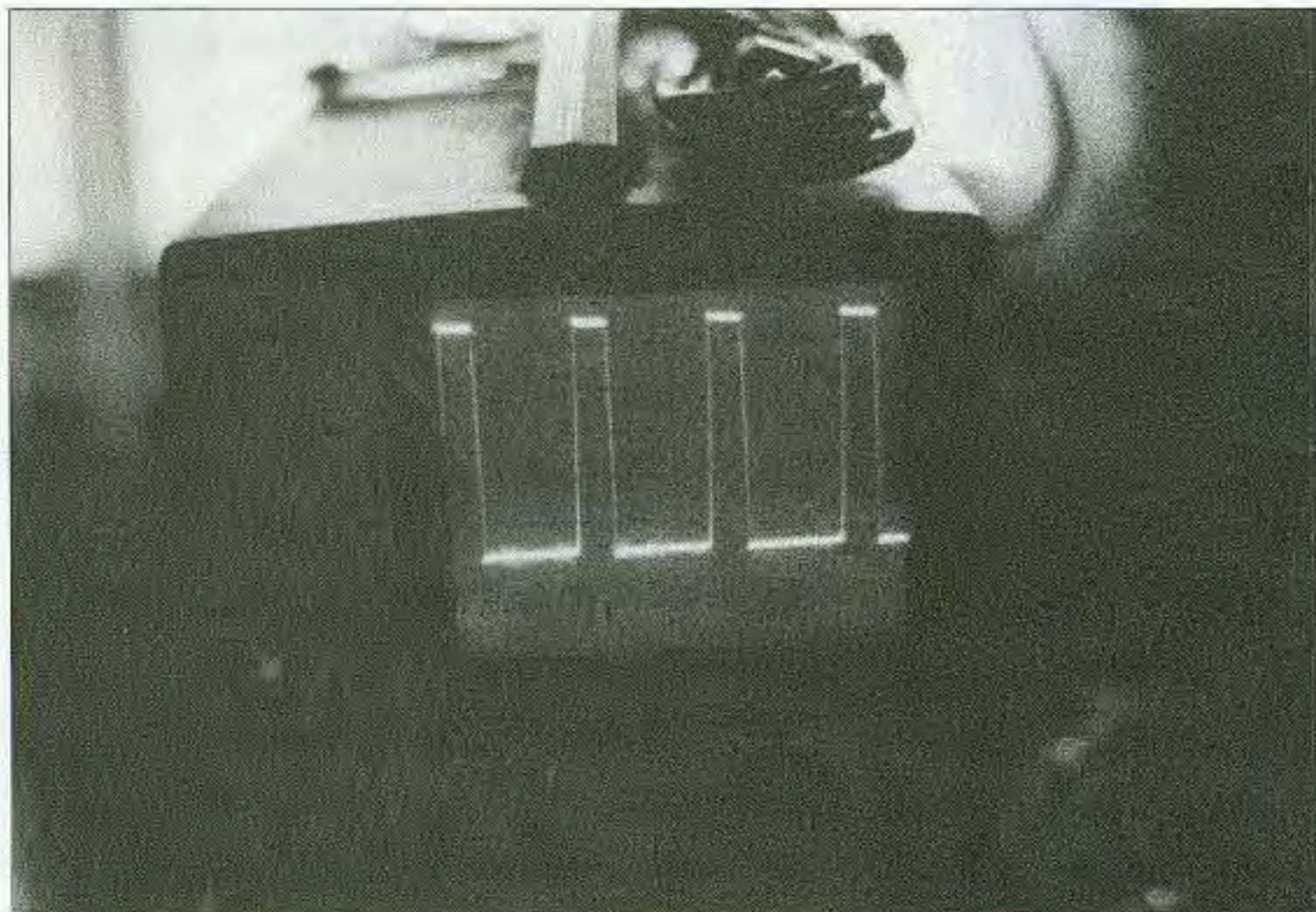


Photo E. Pulse wave.

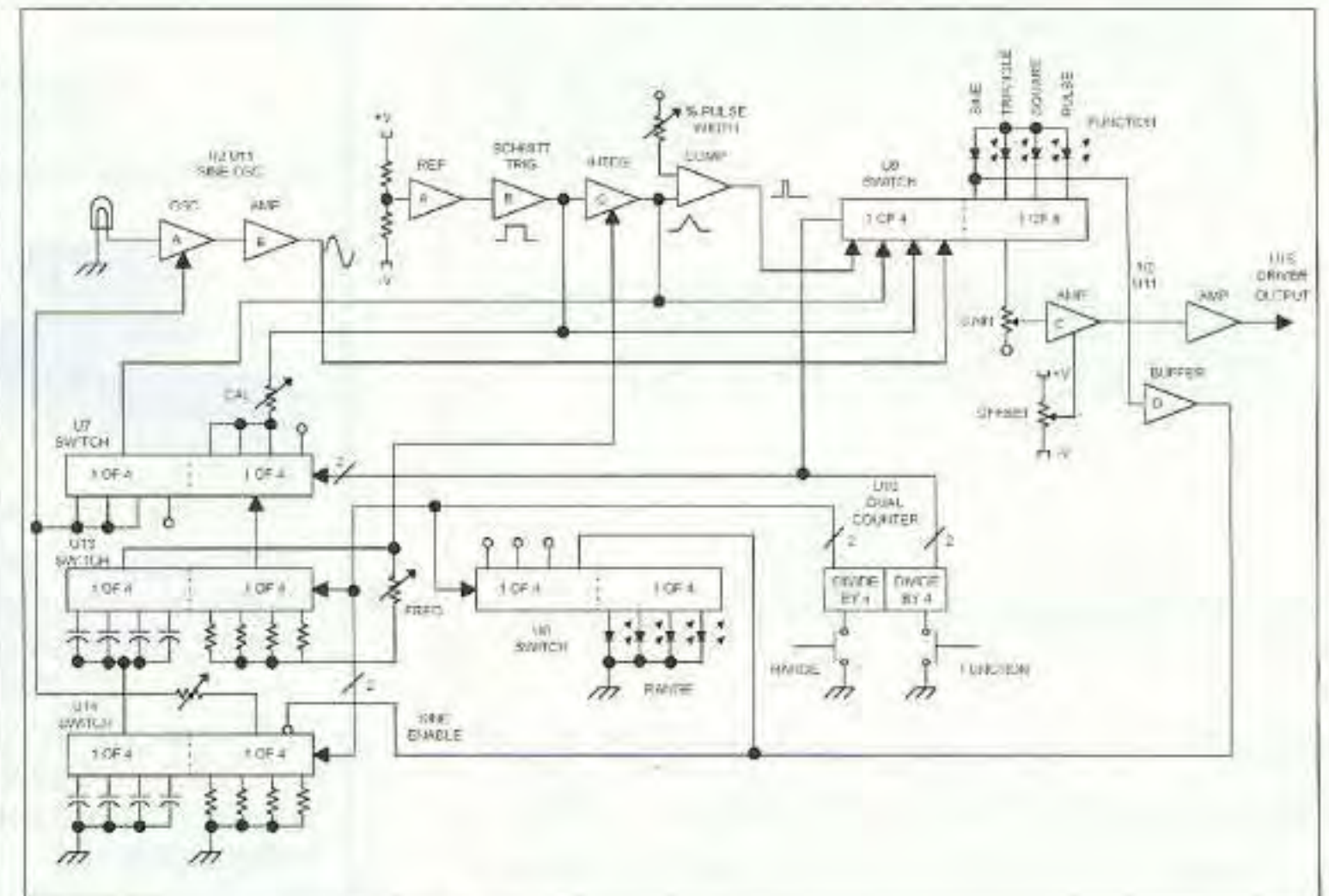


Fig. 11. Overall block diagram.

HEADER	ITEM	PINS					
HD-1	R9	22K RES	6,13	HD-8	R41	--- CAL RES	3,22
HD-1	R10	15M RES	7,12	HD-8	R42	--- CAL RES	4,21
HD-1	R11	10K RES	5,14	HD-8	R43	--- CAL RES	9,16
HD-1	R12	2200 RES	2,17	HD-8	R44	--- CAL RES	10,15
NOTE:	C13--C17	0,1MF CAP	Part of IC's	HD-8	R45	--- CAL RES	11,14
HD-1	C19	100PF-NPO CAP	8,9	HD-8	R46	--- CAL RES	12,13
HD-1	C20	10PF-NPO-CAP	15,16	U-15	R26	10K RES	1,16
HD-1	C21	0,01MF CAP	1,18	U-15	R27	22K RES	2,15
HD-1	C22	0,01MF CAP	3,4	U-15	C32	0,1MF CAP	3,4
				U-15	C33	0,1MF CAP	13,14
HD-2	R3	220 RES	8,11	U-11	C34	0,1MF CAP	1,18
HD-2	R4	220 RES	2,17	U-11	C35	0,1MF CAP	9,10
HD-2	C10	100MF CAP	15,16	U-12	C36	0,1MF CAP	1,18
HD-2	C11	100MF CAP	3,4	U-12	C37	0,1MF CAP	9,10
HD-2	D1	1N5232 DIODE	9,10	HD-9	R28	56K RES	5,20
HD-2	D2	1N5232 DIODE	1,18	HD-9	R29	100K RES	6,19
HD-2	Q1	PN2222 TRAN	12,13,14	HD-9	R30	100K RES	7,18
HD-2	Q2	PN2907 TRAN	5,6,7	HD-9	R31	56K RES	8,17
HD-3	R13	150 RES	5,20	HD-9	R32	150 RES	21,22
HD-3	C23	0,1MF CAP	23,24	HD-9	R33	150 RES	15,16
HD-3	C24	0,1MF CAP	1,2	HD-9	C38	0,002MF CAP	1,2
HD-3	C25	0,1MF CAP	11,12	HD-9	C39	0,002MF CAP	3,4
HD-3	C26	0,1MF CAP	13,14	HD-9	C40	0,002MF CAP	9,10
HD-3	C42	0,001MF CAP	7,8	HD-9	C41	0,002MF CAP	11,12
HD-3	C43	0,01MF CAP	9,10	HD-9	B3	#1240 Bulb (3mm) T-1	23,23
HD-3	C44	0,22MF CAP	15,16	HD-9	B4	#1240 Bulb (3mm) T-1	13,14
HD-3	C45	4,7MF CAP	17,18	HD-10	R34	1200 RES	10,15
HD-3	B1	#1240 Bulb (3mm)	21,22	HD-10	R35	1800 RES	11,14
HD-4	R15	1K RES	5,20	HD-10	R36	1200 RES	12,13
HD-4	R16	1K RES	6,19	HD-10	C34	0,1MF CAP	1,24
HD-4	R17	330 RES	10,15	HD-10	C35	0,1MF CAP	9,16
HD-4	C27	0,1MF CAP	24,23	HD-10	U22	TL064A IC	2-7,17-23
HD-4	C28	0,1MF CAP	1,2	PC Board	R1,R2	56-1W RES	-----
HD-4	C29	0,1MF CAP	21,22	PC Board	C1,C2	6800 MF CAP	-----
HD-4	C30	0,1MF CAP	11,12	PC Board	C3-C4	0,01MF CAP	-----
HD-4	C31	0,1MF CAP	13,14	PC Board	C5-C8	0,1MF CAP	-----
HD-4	C52	0,1MF CAP	3,4	PC Board	C9	100MF CAP	-----
HD-4	C18	0,1MF Cap (Axial)	9,16	PC Board	C12	220MF CAP	-----
HD-5	R18	1K RES	10,15	PC Board	DB1	Diode Bridge	-----
HD-5	R19	1K RES	11,14	PC Board	L-1	Choke	-----
HD-5	R37	560 RES	1,24	PC Board	U-1	LM-2940CT	-----
HD-5	R11	100K RES	12,13	PC Board	Z-1	MOV	-----
HD-6	R20	1K RES	1,24	PC Board	SIP	SIP's	-----
HD-6	R21	33-1W RES	2,23	PC Board	R14	10K-10T-Trim POT	-----
HD-6	R22	10K RES	5,20	JW10	Front R5A,R5B	10K-10T POT	-----
HD-6	R23	10K RES	6,19	JW10	Front R6	100K-1T-POT	-----
HD-6	R24	330 RES	7,18	JW10	Front R7,R8	10K-1T-POT	-----
HD-6	R25	330 RES	8,17	SO1,2,3,4	U2-U5	DIP18	
HD-6	C51	10PF-NPO CAP	21,22	SO5	U6	DIP16	
HD-7	D5-D12	LED's	-----	SO6,7,8	HD1,2,8	DIP18	
HD-8	C46	0,001MF CAP	5,6	SO9,10	U12,U13	DIP18	
HD-8	C47	0,01MF CAP	7,8	SO11-SO17	U7-U10,U13-15	DIP16	
HD-8	C48	0,22MF CAP	17,18	SO18-SO25	HD3-HD10	DIP24 (S)	
HD-8	C49	4,7MF CAP	19,20	SO26,27	U16-U21	DIP24 (W)	
HD-8	R39	--- CAL RES	1,24	END	NOTE: SO1-SO5 Sockets Author used sockets with on board 0,1MF capacitors...vice DIP18.		
HD-8	R40	--- CAL RES	2,23				

Table 2. Header component pinout locator.

Good luck on yours! I can answer reasonable questions if I receive an SASE with the request. For those folks who would like more research information, I have included some references.

References

1. *Ham Radio Magazine*, Sept., 1979; Aug. 1980; June 1982; April 1988.
2. *Electronic Design Magazine*, July 1993.
3. *National Semiconductor Op Amp Data Book*.

Parts sources

1. Hosfelt Electronics, catalog 1-800-524-6464.

2. Jameco Electronics, catalog 1-800-831-4242.

3. Mouser Electronics, catalog 1-800-346-6873.

4. Digi-Key Electronics, catalog 1-800-344-4539.

5. Ten-Tec, Inc., catalog 1-800-231-8842. 73

Subscriptions to 73 Magazine

Only \$24.97 — 1 year
\$44.97 — 2 years
\$65.00 — 3 years*


*best buy (54% off cover price!)

Call 800-274-7373

The New Pools!

Examination Test Questions & Answers

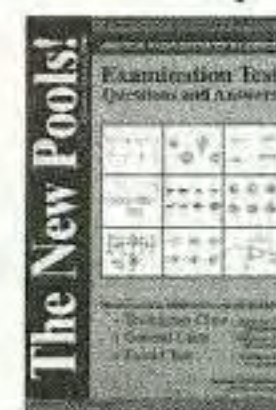The exact questions, multiple choices and answers for the Technician Class, General Class, and Extra Class operator's license.



Only \$9.95 Plus \$3.50 S&H

Omega Sales
P.O. Box 376
Jaffrey, NH 03452
800-467-7237

