

Single i.c. function generator

The c.m.o.s. nand gate CD4011 can be used as an operational amplifier with an open loop gain of ≈ 100 . The generator consists of an integrator G_1 with a variable delay-time, Schmitt trigger G_2 , G_3 , and a triangle to sinewave converter G_4 . The sine-wave approximation depends on the transfer function of G_4 and is calibrated by R_3 and R_4 . Sawtooth and pulse waveforms are obtained by choosing different values for R_1 and R_2 . Values of R_1 and R_2 may be varied between $10k\Omega$ and $10M\Omega$ while C can be between $100pF$ and $2.2\mu F$ (reversible). Typical oscillator frequency f is $\alpha/(R_1 + R_2)$. C hertz where α is the setting of R_5 . At the ends of the frequency range, however, waveform distortion and frequency deviation become significant.

J. W. Richter,
Backnang,
Western Germany.

