

# Simple continuity tester fits into shirt pocket

Tom Wason, Phoenixville, PA

This Design Idea describes a handy continuity tester with two modes of operation: It may sound if it detects continuity between its two probes, or it may sound when it detects no continuity. The second option permits testing for intermittent cable breaks. Response must be sufficiently fast to permit swiping a probe across perhaps 100 pins to instantly find a connected pin. The tester may also identify microfarad or larger capacitance between two conductors.

To properly test for continuity, the tester's voltage and current are limited so that low-power semiconductors do not suffer overstress or appear as a connection between two conductors. The tester must protect itself if you accidentally connect it across an energized circuit or a charged capacitor. Power consumption must be low so that if you accidentally leave the tester on overnight, it will not discharge the battery. The tester must operate even with low battery voltage.

Continuity requires a threshold of less than 200Ω. Depending on battery voltage, that threshold may even

be 80Ω. The tester's open-circuit voltage is less than 0.5V. Its short-circuit current is approximately 1 mA. Values are low so that the tester doesn't mistake a Schottky-barrier rectifier for continuity. When the tester is silent, it draws slightly more than 1 mA of current from a 9V battery. You can connect the probes for a few seconds across any voltage from -50 to +200V without damage.

A feedback circuit comprising Q<sub>1</sub> PNP and Q<sub>2</sub> NPN transistors maintains voltage on the gate of IGFET Q<sub>3</sub> (insulated-gate field-effect transistor) at less than 1.4V despite a 680-kΩ pullup resistor, R<sub>4</sub>, and current from D<sub>2</sub> (Figure 1). When you short the probes, you divert more Q<sub>1</sub> base current to the probes, and less current flows through D<sub>2</sub>. Eventually, Q<sub>2</sub> can no longer maintain a low Q<sub>3</sub> gate voltage. As the gate voltage exceeds 1.8V, Q<sub>3</sub>'s drain-to-source current causes Q<sub>4</sub> to become nonconductive. A 1-MΩ pullup resistor, R<sub>6</sub>, then applies 9V to Q<sub>5</sub>'s gate, causing the tester to sound, announcing continuity.

Without a conducting Q<sub>2</sub> collector,

Q<sub>3</sub>'s gate voltage approaches 9V. Current would then leak through Q<sub>1</sub>'s collector-to-base path. Diode D<sub>2</sub> blocks Q<sub>3</sub>'s gate voltage from leaking to the shorted probes.

The tester detects instantaneous continuity even when you quickly swipe a probe across 100 pins. Capacitor C<sub>1</sub> and pullup resistor R<sub>5</sub> extend Q<sub>5</sub>'s low gate-voltage response by 20 msec. Thus, the tester sounds slightly longer to indicate that it has established connectivity and does not miss a conductive pin during a fast swipe.

Probe current charging a capacitor may also create a short beep. The 20-msec extended beep means that the tester detects even 10-μF or smaller capacitors. With practice, you can estimate capacitance within decades from the beep's period.

Diodes D<sub>3</sub> through D<sub>5</sub> block destructive currents if probes touch an energized circuit. Resistor R<sub>3</sub> must be at least ½W to withstand current from an energized circuit for a few seconds without damage.

To test for cable continuity, the tester sounds only during a broken connection. In this case, firmly connect the probes to both ends of the cable. Switching S<sub>2</sub> changes the tester's function so that Q<sub>4</sub> drives the buzzer during a cable break.

You can modify the circuit to be a better cable tester by reducing the value of resistor R<sub>1</sub> to 4.7 kΩ and omitting capacitor C<sub>1</sub>. With these modifications, detecting loss of continuity occurs at a threshold resistance of less than 100Ω.

Unfortunately, a continuity tester may create noise currents that feed back into the sensitive Q<sub>1</sub>/Q<sub>2</sub> detector. Three circuit features minimize that noise. First, capacitor C<sub>2</sub> connects across the buzzer. Second, IGFET Q<sub>3</sub> acts as a buffer. Last, diode D<sub>5</sub> grounds Q<sub>4</sub> and Q<sub>5</sub> separately from ground for Q<sub>2</sub> and Q<sub>3</sub>.

The circuit performs even when a battery voltage is less than 6.5V. However, lower battery voltage means that the tester detects continuity at a higher threshold resistance. You may install the entire tester in a plastic case smaller than a pack of cigarettes. EDN

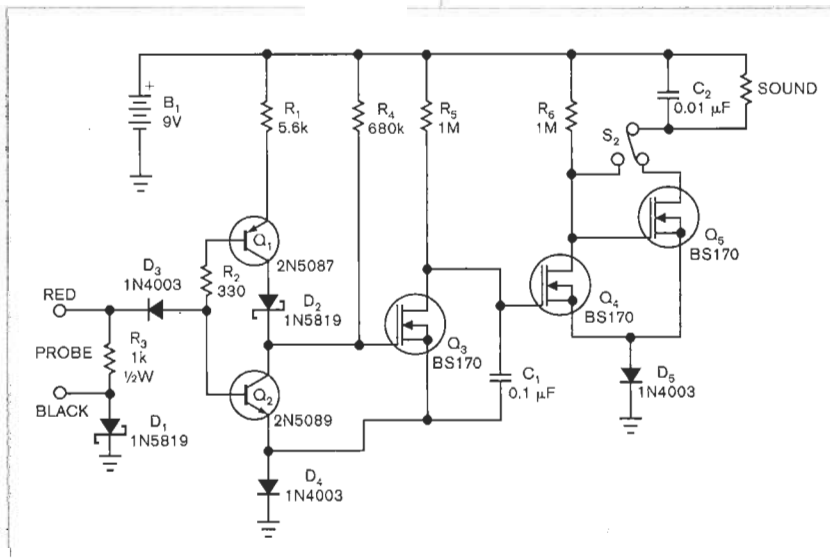


Figure 1 This simple continuity tester is switch-selectable to sound on either shorts or opens. It prevents a user from accidentally connecting it across live circuits.