

Circuit checks "swamp-cooler" water level

Daniel Krones, Precision Design Services, Sky Forest, CA

asimple, inexpensive backup

alarm signal if the water level exceeds the preset height. The circuit uses a single Schmitt-trigger IC to detect the water level, using the conductivity of the water to drop the input level of IC $_{\rm 1A}$. A 1- to 10- ${\rm M}\Omega$ resistor is suitable for ${\rm R}_{\rm l}$. You might

Detect water level in a swamp-cooler reservoir with this simple circuit.

have to experiment to determine a suitable value, depending on the conductivity of the water supply.

The highest practical vale of R_1 provides the widest range. The NAND gates IC_{1B} and IC_{1D} implement gated oscillators

to create a pulsed tone to drive the piezoelectric-bell audible alarm. Current consumption in the off state is lower than 10 μ A, thus allowing the use of a simple battery to drive the circuit. A button-cell lithium watch battery is sufficient. The small physical size and wiring simplicity of the circuit allow you to simply glue the unit to

the side of the cooler. Use a short piece of twin-lead, 300Ω transmission line for the electrodes.

Is this the best Design Idea in this issue? Select at www.edn.com.



Enter 3 at www.ednmag.com/info