

# Transistor Beta Tester With Linear Scale

SERGIO BERNSTEIN\*

Tube testers are accepted as necessary units of test equipment. Increased use of transistors makes some means for testing them almost imperative, and this design gives a direct reading with a minimum of manipulation.

**T**HIS SIMPLE AND LOW-COST instrument has a linear, direct-reading dial and two "beta" ranges. The accuracy can be made as high as one per cent depending on the components used, while the cost of the instrument is relatively low.

Basically, the circuit<sup>1</sup> is that of an oscillator. The point at which oscillation starts is determined by the  $\beta$  of the transistor and by a potentiometer  $R_1$  in Fig. 1. The frequency of oscillation which lies in the audio range, depends mostly on the transformer characteristics.

## Theory

To understand the operation of the circuit, let us examine the conditions which prevail when the circuit just begins to oscillate: (see Fig. 1)

let  $N$  = Transformer turns ratio

$I_c$  = a.c. collector current

$I_b$  = a.c. base current

$\beta$  = the base-to-collector current gain

We have:

$$I_1 + I_2 = I_c; \text{ and } I_b = \frac{I}{N} (I_1)$$

Also:

$$I_2 = \frac{R_1}{R_o} (I_1)$$

Then:

$$I_c = I_1 \left( 1 + \frac{R_1}{R_o} \right); I_1 = \frac{I_c}{1 + \frac{R_1}{R_o}}$$

Therefore:

$$I_b = -\frac{I_c}{N} \left( \frac{1}{1 + \frac{R_1}{R_o}} \right)$$

since

$$\beta = -\frac{I_c}{I_b}$$

we see that

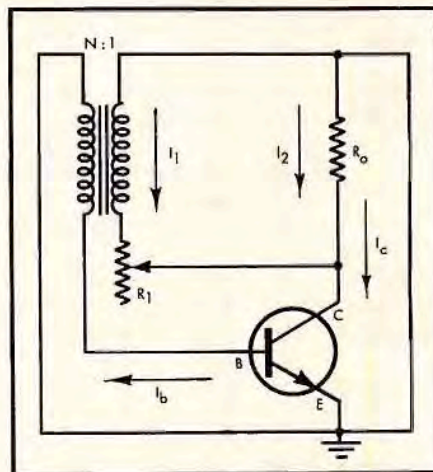


Fig. 1. Simplified schematic of basic arrangement for testing transistors.

$$\beta = N \left( 1 + \frac{R_1}{R_o} \right) \quad (1)$$

Therefore, for a given transformer ratio and a given transistor  $\beta$ , the circuit will start oscillating only when  $R_1$  is above a certain critical value, given by the relationship of Eq. (1). Thus the potentiometer  $R_1$  can be calibrated to read  $\beta$  directly.

Let us investigate the circuit further to see what other useful relationships we can determine, and how we can make a linear, direct-reading, dial scale. Suppose we make the resistor  $R_1$  a 10-turn potentiometer, and we use a 15-turn dial such as a Beckman type "RB" (or other similar device) to read out our  $\beta$  values directly. This dial has 100 major divisions per turn, and a total of 15 turns or 1500 divisions. If we determine the minimum  $\beta$  value we wish to read, we automatically set the maximum value of  $\beta$  we can read on one range. This is true since our resistor  $R_1$  in Fig. 1 goes from a minimum value of zero ohms to its maximum value when rotated the full 10-turns, and  $\beta$  varies with  $R_1$  according to Eq. (1).

Let us call our minimum value of  $\beta$  by the term  $\beta_{min}$ . Then our maximum value,  $\beta_{max}$ , will be  $\beta_{min} + 100.0$  since, after 10 turns, the dial will read 100.0 divisions more than at its initial position.

Let us call  $R_{min}$  the total circuit resistance, including the transformer primary resistance, when  $R_1$  equals zero. Let us call  $R_p$  the total resistance of the potentiometer.

Then using Eq. (1) we can write the following:

$$\beta_{min} = N \left( 1 + \frac{R_{min}}{R_o} \right) \quad (2)$$

$$\beta_{max} = 100.0 + \beta_{min} = N \left( 1 + \frac{R_{min} + R_p}{R_o} \right) \quad (3)$$

Combining (2) and (3):

$$100.0 + N \left( 1 + \frac{R_{min}}{R_o} \right) = N \left( 1 + \frac{R_{min} + R_p}{R_o} \right)$$

Therefore:

$$100.0 = N \left( \frac{R_p}{R_o} \right)$$

and

$$\frac{R_o}{N} = \frac{R_p}{100} \quad (4)$$

This equation gives the relationship necessary to get the correct dial reading for  $\beta_{min}$  and  $\beta_{max}$  for a given  $N$ ,  $R_o$ , and  $R_p$ . Note that this relationship is independent of  $R_{min}$ .

If we substitute Eq. (4) back into Eq. (2) we get:

$$\beta_{min} = N + \frac{R_{min} \times 100}{R_p} \quad (5)$$

This equation tells us what the minimum value of  $\beta$  is we can read, with a given turns ratio  $N$ ,  $R_{min}$ , and  $R_p$ .

From Eqs. (2) and (3) we note an important property of this circuit, namely: we can change the range of  $\beta$  readings

\* 205 South Broadway, Tarrytown, N.Y.  
<sup>1</sup> G. F. Montgomery, "Transistor beta tester." *Electronics*, May, 1957, pg. 198.

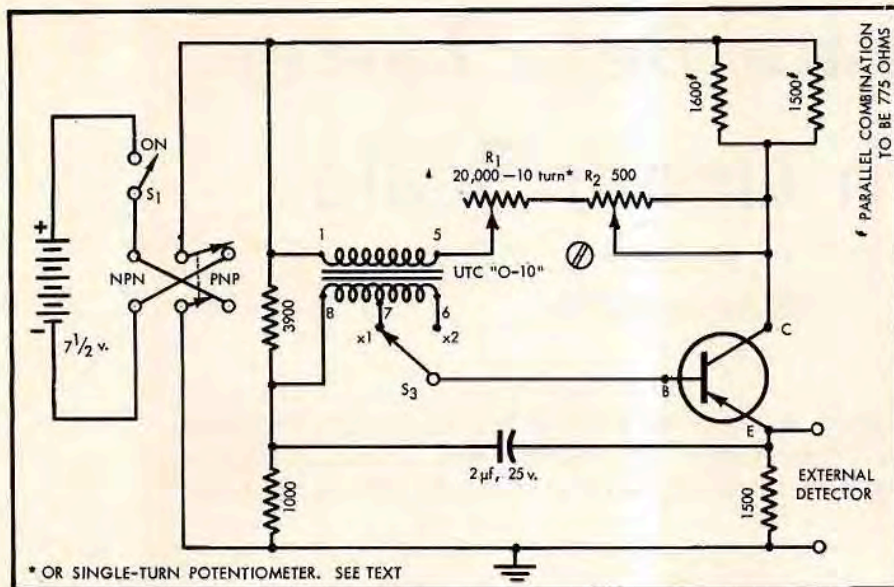


Fig. 2. Complete schematic of transistor tester.  $R_1$  may be a special 10-turn potentiometer, used with a 15-turn dial, although a single-turn four-watt type of pot may be used instead.

directly by changing only the transformer ratio  $N$ . Thus, if we use a multi-tap winding in the base circuit, having transformation ratios of  $N$  and  $KN$ , we can have two ranges of  $\beta$  namely: from  $\beta_{min}$  to  $(100 + \beta_{min})$  and from  $K \times (\beta_{min})$  and from  $K \times (\beta_{min})$  to  $K \times (100.0 + \beta_{min})$ . All we have to do is multiply our dial reading by the factor  $K$ .

Having established the relationships which govern the operation of this circuit, a practical form of it can be designed as in Fig. 2.

To keep the cost at a minimum, the surplus market was scanned, and it was found that 10-turn, 20,000-ohm, potentiometers were available.  $R_p$  then is 20,000 ohms.

Next  $T_1$  was chosen so as to get two  $\beta$  ranges. A UTC type 0-10 was selected.

For this transformer,  $N = 3.875$  using  $1/2$  primary to full secondary, or  $N = 7.75$ , using full primary to full secondary.

Using  $N = 3.875$  we find  $R_o$  from Eq.

$$(4) : R_o = N \times \frac{20,000}{100} = 775 \text{ ohms.}$$

$R_o$  should be measured accurately on a bridge. This will eliminate the necessity of using a variable adjustment for  $R_o$ .

$\beta_{min}$  can now be chosen. A value of  $\beta_{min} = 5.0$  seemed reasonable after looking over the characteristics of transistors presently available. Then:

$$5.0 = \beta_{min} = N \left( 1 + \frac{R_{min}}{R_o} \right) = (3.875) \times \left( 1 + \frac{R_{min}}{775} \right)$$

Thus,  $R_{min} = 225$  ohms.

A 500-ohm potentiometer ( $R_2$  in Fig. 2), is used to adjust  $R_{min}$  to its exact value.

The rest of the circuit is designed so that any transistor inserted in the test instrument will operate at approximately 6 volts collector voltage and approximately 1 ma emitter current. Switch  $S_2$  is included so that either PNP or NPN units can be tested, and switch  $S_3$  changes the dial reading from "times 1" to "times 2." One word of caution: check to see that the transformer is wired with the same phasing shown in Fig. 2—otherwise the circuit will not oscillate. To keep the instrument as simple and inexpensive as possible, no detector or meter was incorporated in the circuit. Any detector, such as earphones, VTVM, or oscilloscope can be used to detect when oscillation just starts.

When taking a reading, start from a high dial setting towards the low one. A reading should be taken when the oscillations just start, *not* when they stop, as indicated when going from a low reading to a high one.

#### Calibration

To calibrate the  $\beta$  tester, an oscillator, a VTVM (such as a Ballantine Model 300) and two precision resistors are required, one of 0.1 megohms and one of 1000 ohms, as in Fig. 3. The audio oscillator is set for 1000 cps, and its output at about 10 volts. The battery leads are shorted and are the "ground point." The 0.1-meg. resistor is wired between the collector terminal and the oscillator. The 1000-ohm resistor is wired between the base and emitter terminals.  $S_3$  should be in the "X1" position.

By comparing Fig. 3 to Fig. 1 it will be noted that:

$$\beta = \frac{I_c}{I_b} = \frac{V_{in}}{100,000} \div \frac{V_{out}}{1000} = \frac{V_{in}}{V_{out} \times 100}$$

The dial should now be set so that when the 10-turn potentiometer is at zero resistance, it reads  $\beta_{min}$ , i.e. 5.0. Rotate the dial ten full turns to check if it reads 105.0 i.e.:  $\beta_{min} + 100.0$ . (To avoid turning the potentiometer ten turns every time, leave it at its maximum resistance setting and use a short clip lead to short it out when zero resistance is required during calibration measurements). With  $R_1$  at zero ohms (using clip lead) adjust  $R_2$  to get:

$$\frac{V_{in}}{100 \times V_{out}} = \beta_{min}$$

With  $R_1$  at maximum resistance see if:

$$\frac{V_{in}}{100 \times V_{out}} = 100 + \beta_{min}$$

If  $R_o$  is the proper value then the measurements should check. If not,  $R_o$  has to be trimmed slightly, leaving  $R_2$  set, until

(Continued on page 53)

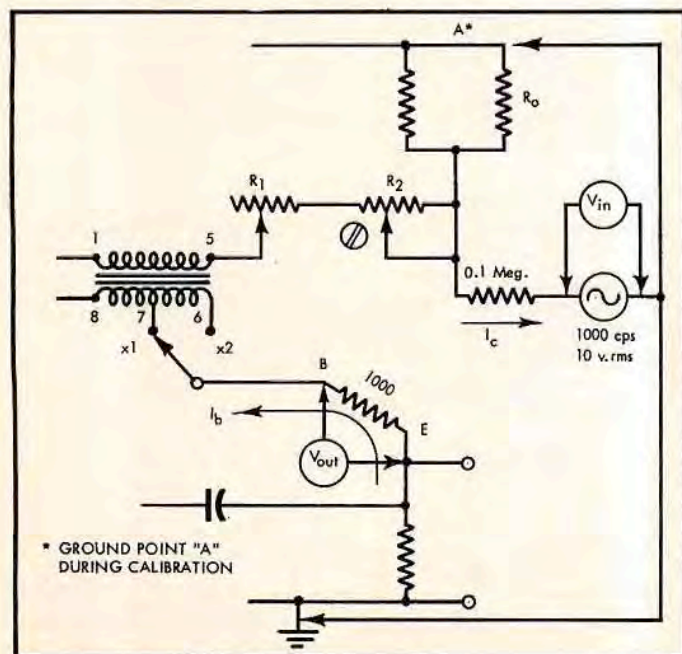


Fig. 3. Circuit used for calibration of the transistor tester.

# TRANSISTOR BETA TESTER

(from page 22)

the values of  $\beta_{min}$  and  $100 + \beta_{min}$  coincide with the meter indications.

It should be emphasized that the meter should be calibrated first to make sure an accurate calibration is obtained for the  $\beta$  tester.

When  $R_o$  and  $R_2$  are adjusted to give the proper values of  $\beta$  at both ends of the scale, all other points in between are automatically calibrated to an accuracy equal to the linearity of the potentiometer used. The points can be checked as a matter of routine, and will be found to coincide exactly with the dial readings. Readings with switch  $S_3$  in the "X2" position will be exactly one-half those taken with  $S_3$  in the "X" position.

## Single-turn Potentiometer

If a more common type, single-turn,

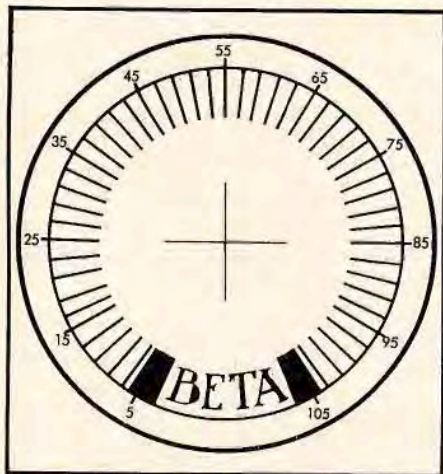


Fig. 4. Dial scale may be cut out and used with the single-turn potentiometer.

wire-wound linear potentiometer is used with a dial marked from "0" to "100," the method of calibration is the same, with the following exception. Since the  $\beta_{min}$  reading should be "5.0", and the dial reads "0", and the  $\beta_{max}$  reading should be "105", and the dial reads "100", the user should always make a note to *add* the quantity "5.0" to every reading he makes with the instrument. Thus, a reading of  $\beta = 42.0$  on the dial, really indicates a true  $\beta$  value of 47.0 and so on. This constant offset between true  $\beta$  and dial reading does not diminish the usefulness of the instrument and enables the builder to save the cost of a more expensive potentiometer. A dial can be especially made to suit the requirements, or Fig. 4 can be cut out and glued to the cabinet to serve as the dial, preferably under a thin piece of transparent plastic for protection.

## Construction

All the components can be placed inside a 3" x 4" x 5" aluminum box. The placement of the parts can be seen from the photographs. All resistors and capacitors can be mounted on a small terminal board, and wires run to the battery, switches, and potentiometers as required. An "L" or "U" shaped bracket is used to secure the battery, or it can be mounted on the bottom cover plate.

Three type X-2146 spring loaded diode clips (manufactured by Cambridge Thermionic Corp.) are used to clip the transistor leads during the measurement other types may be found equally suitable.