BY JAMES B. PENNY A LOW-COST DOT BAR GENERATOR

A DOT/BAR video signal generator is an essential piece of test equipment for the setup and convergence of a color-TV receiver or monitor. The generator can also be used to adjust horizontal and vertical linearity of monochrome receivers and monitors.

The circuit (Fig.1) shown here can be built for about \$15, and is small enough to be permanently installed in a color-TV cabinet. It can also be housed in a small case (including a 9-volt battery) for portable use. Since the output is video, some form of FCC-approved r-f modulator is required if you wish to inject the signal into the antenna of a TV receiver.

Circuit Operation. Oscillator *IC1* is preset to 251,752 Hz (16 times the horizontal scanning rate) by the setting of potentiometer *R1*. When a 555 is operated with D17 as shown, the data sheet formulas for frequency are not valid, and the frequency of oscillations becomes more dependent on the supply voltage. The output of *IC1* (pin 3), drives 12stage counter *IC2* to generate the other frequencies required to create the composite video output signal. Various *IC2* outputs are diode OR'ed to produce the proper pulse widths.

Horizontal and vertical video components are combined in NOR gate IC3A, while the horizontal and vertical sync components are mixed in IC3B. Output transistors Q1 and Q2, arranged as an AND gate, combine video and sync into composite video and provide sufficient drive for a 75-ohm output load.

With S1 in its center (off) position, the video display will be white dots on a black background. The other positions of S1 yield horizontal or vertical white bars on a black field. These are the output signals most commonly used for static and dynamic convergence of color receivers. They can also be used to set linearity of monochrome receivers.

The values of R9 and R10 determine the base currents of Q1 or Q2, and their connections to IC3 determine positive or negative video. Resistor R11 determines the blanking (black) level of the display. Resistor R12 determines the peak-to-peak output voltage level, while R13 determines the output impedance.

When powered by 9 volts, the values shown for *R9* through *R13* provide a nominal one volt peak-to-peak composite video with negative-going sync into a 75-ohm load.

If R9 is disconnected, the unit becomes a sync generator. Increasing the value of R3 (retuning R1) will increase the width of the bars or dots. Eliminating D9 will increase the height of the bars or dots.

Construction. The circuit can be assembled using any type of wiring technique; the foil pattern shown in Fig. 2 may be used. This illustration also shows component installation.

With the generator powered and S1 in

Build this essential instrument for setup and convergence of color TV for \$15.

PARTS LIST

C1—100-pF, disc ceramic
C2-0.1-µF, disc ceramic
C3-220-pF, 35-volt electrolytic (optional)
D1 through D17-1N914 silicon diode
IC1-555 timer
IC2-CD4040, 12-stage ripple counter
(CMOS)
IC3-CD4001, guad 2-input NOR gate
(CMOS)
Q1, Q2-2N5449 npn silicon transistor
The following resistors are 1/4-watt, 10%:
R2-10,000 ohms
R3.R13-75 ohms
R4, R11-2200 ohms
R5, R6, R7-100,000 ohms
R8-27.000 ohms
R9, R10-1000 ohms
R12-470 ohms
R1-10,000-ohm trimmer potentiometer
S1-Spdt, center-off switch
Mise,battery holder, suitable enclosure, in-
terconnect cable, mounting hardware, etc.
Note-A complete kit of parts including
drilled pe board, is available for \$14.95 plus
S1 50 P+H within the continental US from
ABCOR Inc., Box 58216, Houston, TX
77058. Texas residents, please add 5% sales
tax. The r-f modulator is available from AB-
COR, or M&R Enterprises, PO Box 1011.
Sunnyvale, CA 94088 for \$24.95 with 60-

dB isolation switch and cables. Modulator

only is \$14.95.





Fig 2. Actual-size foil pattern and component installation for the generator. The two large end bars are used for mounting, and are not required for operation. the center tor to the checked R1 until tern app

the center position, connect the generator to the *video* input of the receiver to be checked, and turn on the power. Adjust R1 until the sync locks and a stable pattern appears on the screen.

With the manual provided by the color-TV receiver manufacturer or other source, the generator can now be used for convergence. In a monochrome system, the bars or dots can be used in conjunction with the linearity controls to set up the screen for proper proportions.

Two video outputs are provided: One (out 1) is dc coupled to the output stage, while the other (out 2) is dc isolated from the output stage. Use either one, depending on the type of input required. If the video stage will not tolerate a dc offset, then use output 2. If the video stage has capacitor input, use output 1. \diamondsuit