



12 REASONS YOUR CAR NEEDS TIGER CDI

Instant starting in any weather - Eliminates tune-ups - Increases gas mileage - Increases horsepower 15% - Improves acceleration and performance - Spark plugs last up to 70,000 miles - Reduces engine maintenance expense - Amplifies spark plug voltage to 45,000 volts - Maintains spark plug voltage to 10,000 RPM - Reduces exhaust emissions - Dual ignition switch - An Unconditional LIFETIME GUARANTEE - Installs in 10 minutes on any car with 12 volt negative ground - No rewiring - Most powerful, efficient and reliable Solid State Ignition made.

SATISFACTION GUARANTEED or money back

TIGER 500 assembled \$53.95
TIGER SST assembled \$42.95
Post Paid in U.S.A.

Send check or money order with order to:

Tri-Star Corporation
P. O. Box 1727 C
Grand Junction, Colorado 81501

DEALER INQUIRIES INVITED

CIRCLE NO. 59 ON FREE INFORMATION CARD

free **BA**
1976
catalog



244 PAGE
RADIO, TV &
ELECTRONICS
CATALOG

Your buying guide for Everything in Electronics ... Stereo, Hi-Fi, TV's, Radios, Tape Recorders, CB, Kits, Tools, Books and Electronic Parts.


**WRITE FOR YOUR
FREE COPY NOW!**

burstein-applebee

DEPT. PE 3199 MERCIER ST.
KANSAS CITY, MO. 64111

NAME _____
ADDRESS _____
CITY _____
STATE _____ ZIP _____

CIRCLE NO. 65 ON FREE INFORMATION CARD

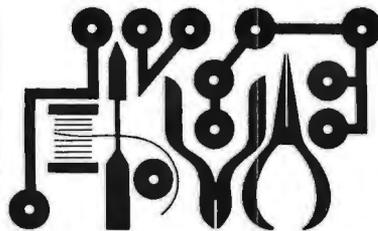

Experimenter's Corner

By Forrest M. Mims

A PROGRAMMABLE TIMER/COUNTER

A FEW years ago, Signetics overwhelmed us all with the introduction of the 555 timer. That chip, as you probably know, is one of the most versatile IC's around, and literally scores of applications for it have been published in POPULAR ELECTRONICS and other magazines.

More recently, Exar capitalized on the 555's popularity by pairing it with a binary counter and putting the whole thing in a 16-pin DIP. They called it the XR-2240 and it is a fully programmable timer/counter with all kinds of fascinating applications. I'm going to describe a few that I've come up with—you will probably think of many others.

With just a few external parts, you can connect the XR-2240 in a free-running mode as shown in Fig. 1. Use anything from 4 to 15 volts for the supply. Current drain is fairly low—about 10 mA for a 9-volt battery. The combination of R and C determines the oscillation period ($T = RC$) of the XR-2240's internal time base. The binary counter outputs (pins 1 through 8) increase T (or reduce the frequency, depending on how you look at it) by factors of 1, 2, 4, 8, 16, 32, 64, and 128. The result is eight square waves with harmonically related frequencies from a single RC timing combination. Figure 2 is a scope photo showing six of the counter outputs from an XR-2240 in its free-running mode ($R = 1.5$ kilohms and $C = 0.022 \mu\text{F}$). Of course, this is impressive, but you haven't seen anything yet!

You can get some really interesting waveforms by connecting the binary counter outputs together. Some of the possible results are shown in Fig. 3. Exar calls the circuit configuration a binary pattern generator, but I call it a super-deluxe audio "chirper." Just connect a crystal or high-impedance magnetic earphone to the output to hear the chirps. By experimenting

with the binary counter output interconnections and installing resistors of various values between some of the outputs, you will be able to obtain a variety of chirps, buzzes, warbles, and other strange sounds. For even more variations, change values of R and C.

If weird-sounding electronic music doesn't interest you, you can always use the pattern generator in more conventional applications. For example, it makes a nifty marker tone generator for a communications system (such as a long-range laser communicator). While a monotone audio oscillator would do the job, it's hard to miss a chirping marker or mistake it for a heterodyne.

Waveform Generator. Another possibility is to use the circuit as a complex waveform generator. I really mean complex, because the XR-2240 can generate all kinds of stepped waveforms. The photo in Fig. 4 shows part of a repetitive, stepped waveform generated by connecting several resistors of different values between the binary counter outputs and the circuit output.

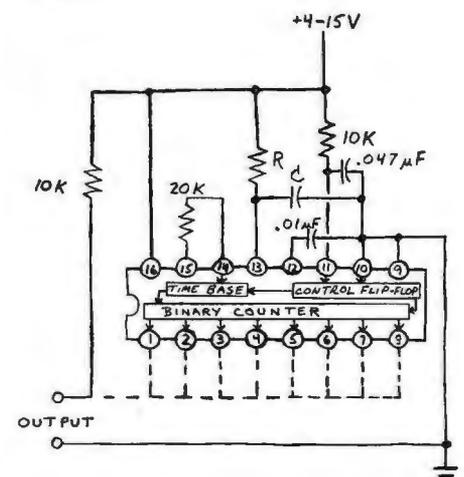


Fig. 1. Schematic of XR-2240 in free-running (astable) mode.

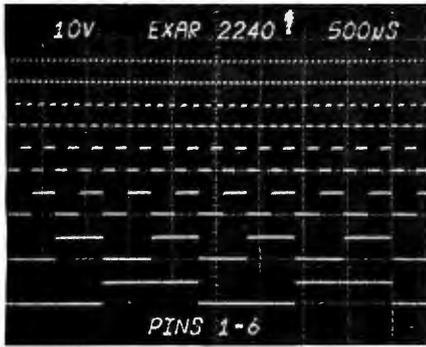


Fig. 2. Output on pins 1 to 6. Scope photos taken with C-59 camera on a Tektronix 7603 scope with 7M13 plug-in readout unit.

If you don't need far-out waveforms like the one in Fig. 4, you can generate more conventional staircases. For a staircase with 256 steps, connect a resistor with a value of about 1000 ohms from pin 8 to the output. Then connect resistors 2, 4, 8, 16, 32, 64, and 128 times that value from pins 7, 6, 5, 4, 3,

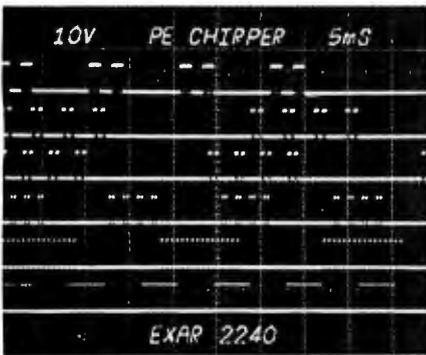


Fig. 3. Six different "chirp" (tone burst) outputs from XR-2240.

2, and 1 (respectively) to the output. You'll have to use precision resistors to get a uniformly spaced staircase. If some values are slightly off, the waveform will be somewhat distorted.

There are lots of other uses for the XR-2240 and they include analog-to-digital conversion, sample-and-hold,

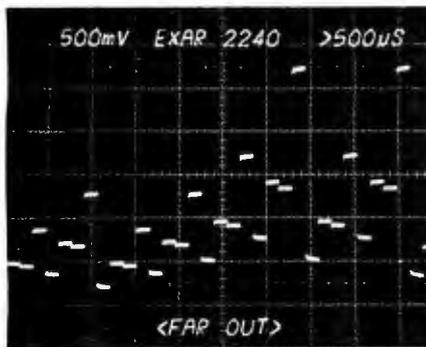


Fig. 4. Complex waveform obtained by connecting resistors to outputs.

harmonic synchronization, and ultra-long "timing" circuits (not true one-shots, but useful nonetheless). The timing properties of the chip are really impressive. For example, the values of R and C in Fig. 1 can be set to provide just one pulse every 10 or 15 minutes. Since pin 8 has a period of 128T, an RC combination which gives a period of 12 minutes would provide an output square wave with a period of 128×12 or 1536 minutes. That's more than a whole day. You can get longer delays by connecting more counter outputs to the output bus. The total time delay will equal the sum of the delays available at each counter output pin.

For truly incredible delays of up to 3 years (!), you can cascade two XR-2240's in series. The delays available from the combination can be used to remind you of birthdays and anniversaries, limit your offsprings' phone calls, and dream up assorted science fiction gadgets.

We'll take a closer look at some of the XR-2240 timing applications in a future column. Meanwhile, latch on to a couple of XR-2240's (see the ads in the back of this magazine), and warm up your soldering iron. ♦

Now...the most enjoyable, do-it-yourself project of your life—a Schober Electronic Organ!

You'll never reap greater reward, more fun and proud accomplishment, more benefit for the whole family, than by assembling your own Schober Electronic Organ.



You need no knowledge of electronics, woodwork or music. Schober's complete kits and crystal-clear instructions show you — whoever you are, whatever your skill (or lack of it) — how to turn the hundreds of quality parts into one of the world's most beautiful, most musical organs, worth up to twice the cost of the kit.

Five superb models, with kit prices from \$575 to around \$2,300, each an authentic musical instrument actually superior to most you see in stores.

Join the thousands of Schober Organ builders — owners who live in every state of the Union. Often starting without technical or music skills, they have the time of their lives — first assembling, then learning to play the modern King of Instruments through our superlative instructions and playing courses.

Get the full story FREE by mailing the coupon TODAY for the big Schober color catalog, with all the fascinating details!

The Schober Organ Corp., Dept. PE-62
43 West 61st Street, New York, N. Y. 10023

Please send me Schober Organ Catalog.
 Enclosed please find \$1.00 for 12-Inch L.P. record of Schober Organ music.

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

CIRCLE NO. 51 ON FREE INFORMATION CARD

FREE McIntosh CATALOG and FM DIRECTORY

Get all the newest and latest information on the new McIntosh Solid State equipment in the McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



MX 113

FM/FM STEREO - AM TUNER AND PREAMPLIFIER

SEND TODAY!

McIntosh Laboratory, Inc.
East Side Station P.O. Box 96
Binghamton, N.Y. 13904
Dept. PE

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

If you are in a hurry for your catalog please send the coupon to McIntosh. For non rush service send the Reader Service Card to the magazine.

CIRCLE NO. 35 ON FREE INFORMATION CARD