Touch-activated timer switch extends battery life

Israel Schleicher, Prescott Valley, AZ

A certain type of cordless optical computer mouse operates on two AA alkaline cells. It has no power on/off switch. When not in use, it automatically reduces power consumption by switching its light source on and off at a low duty cycle. Nevertheless, this function unnecessarily drains the battery, and it is annoying to often find the device inoperable. The solution to the problem is to add a battery switch that automatically disconnects the battery after a preset time. This approach requires no disassembly or other kind of tampering. This Design Idea describes two distinct implementations of a touch-activated timer switch that you can add to many battery-operated gadgets that you might inadvertently leave on.

The circuit in Figure 1 illustrates an analog implementation of the switch. Figures 2 and 3 show digital implementations. The idea is to insert a 30-

THIS DESIGN IDEA
DESCRIBES A TOUCHACTIVATED TIMER
SWITCH THAT YOU
CAN ADD TO MANY
BATTERY-OPERATED
GADGETS.

mil-wide strip of dual-sided PCB (printed-circuit board) between the negative pole of the battery and the spring contact of the battery holder (Item A in the figures). Q3 is a low-threshold MOS transistor that connects between the two sides of the strip and serves as the switching element (Figure 1). C, is a 0603 X7R ceramic-chip capacitor, and R, is a 0603 chip resistor. You mount Q, and all associated components near the upper edge of Item A. You insert a narrow strip of thin brass, Item B, in series with the positive pole of the second cell. You connect it to the circuit with a piece of thin, flexible wire. Touch contacts C and D comprise short strips of self-adhesive copper tape that you attach outside the battery compartment. Thin and flexible wires connect C and D to the circuit.

 Q_1 , Q_2 , and C_1 form a monostable flip-flop. When the switch is off, C_1

designideas

does not charge, and both Q₁ and Q₂ are off. When you momentarily touch both C and D with bare fingers, current through your hand charges C, to the threshold level of Q₂. Both Q_2 and Q_1 turn on, discharging C_1 through Q_1 and your conductive fingers. The voltage level at the gate of Q, is then close to the battery voltage. After you remove your fingers, the leakage through the internal gate protection of Q,—the zener diode in the figures—causes the voltage at the gate of Q, to slowly drift lower until it reaches the threshold level of approximately 1.3 V. Q_2 exits conduction and, with Q₁, causes a regenerative action to quickly turn off Q₃.

The switch remains off until you again touch C and D. Item E is an optional contact similar to C and D. If you touch E and D, the switch turns off. Using a value of 0.01 µF for C₁, you obtain a delay of approximately one hour. Because the gate leakage is on the order of a few picoamperes, you must clean the circuit with a flux solvent and then coat it with a drop of wax or epoxy resin.

In some cases, you might want to be able to adjust the timing of the switch. The circuit in Figure 2 provides that option. It uses a tiny microcontroller in an SOT-23 package. Listing 1, which is available in the Web version of this Design Idea at www.edn.com/080710di1, contains the touch-activated timer switch. Items A, B, C, and D are the same as those in Figure 1. When the switch is off, the PIC10F200T microcontroller is in sleep mode and consumes practically no power. When you simultaneously touch contacts C and D, the level at Pin 1 of IC, goes high, and the microcontroller starts to tally the time that Pin 1 remains high. After 0.5 sec, the buzzer sounds a short beep. The buzzer then sounds two, three, and four fast beeps in 0.5-sec intervals. By immediately releasing contacts C and D after hearing any number of beeps, you can set the switch for 30 seconds, 30 minutes, four hours, and eight hours of operation, respectively. The choices of operating times are arbitrary; you can modify the code in Listing 1 to whatever fits your application. Jump-

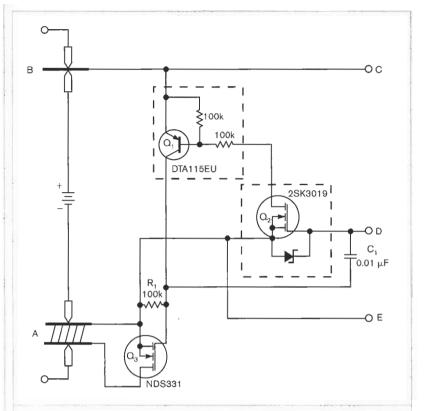


Figure 1 In parallel with the cells of a battery-powered device, this analog circuit disconnects the battery after a delay. Touching contacts C and D with a finger turns on the switch, connecting the cells to the load. The components fit inside the battery compartment.

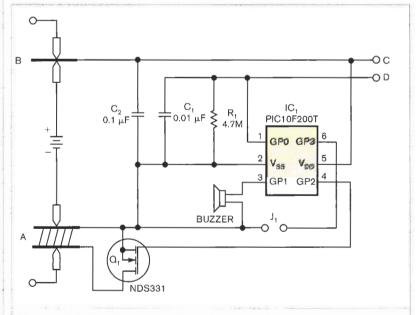


Figure 2 This digital implementation of the battery-disconnect switch uses a PIC10F200T microcontroller to control the disconnect switch.

designideas

er switch J_1 is optional. If you leave it open, touching C and D turns it off. Short-circuiting J_1 disables this option, and the switch will turn off only at the end of the programmed time. As is the case with the analog implementation, you mount all components except the buzzer at the edge of Item A. The buzzer is a small piezoelectric element with a resonant frequency of 4 kHz and can easily fit inside the battery compartment.

In some cases, you may not have access to the negative contact of the battery holder. The circuit in **Figure** 3 addresses this situation. It is essentially the same as the circuit in **Figure** 2, except that you place Item A in series with the positive pole and attach B to the negative pole of the battery. A P-channel MOS transistor acts as a switch, and you modify the microcontroller's program to provide a low level to drive Q_1 . A comment in **Listing 1** indicates the proper line of code for the options in either **Figure 2** or **Figure 3**.**EDN**

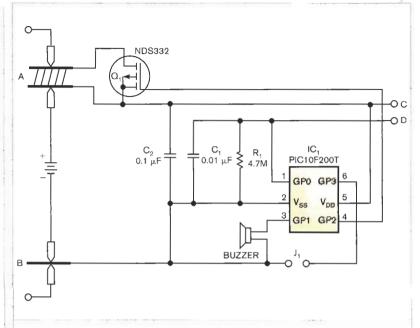


Figure 3 This circuit addresses the problem of a lack of access to the negative contact of the battery holder. It is essentially the same as the circuit in Figure 2, except that you place Item A in series with the positive pole and attach B to the negative pole of the battery.

