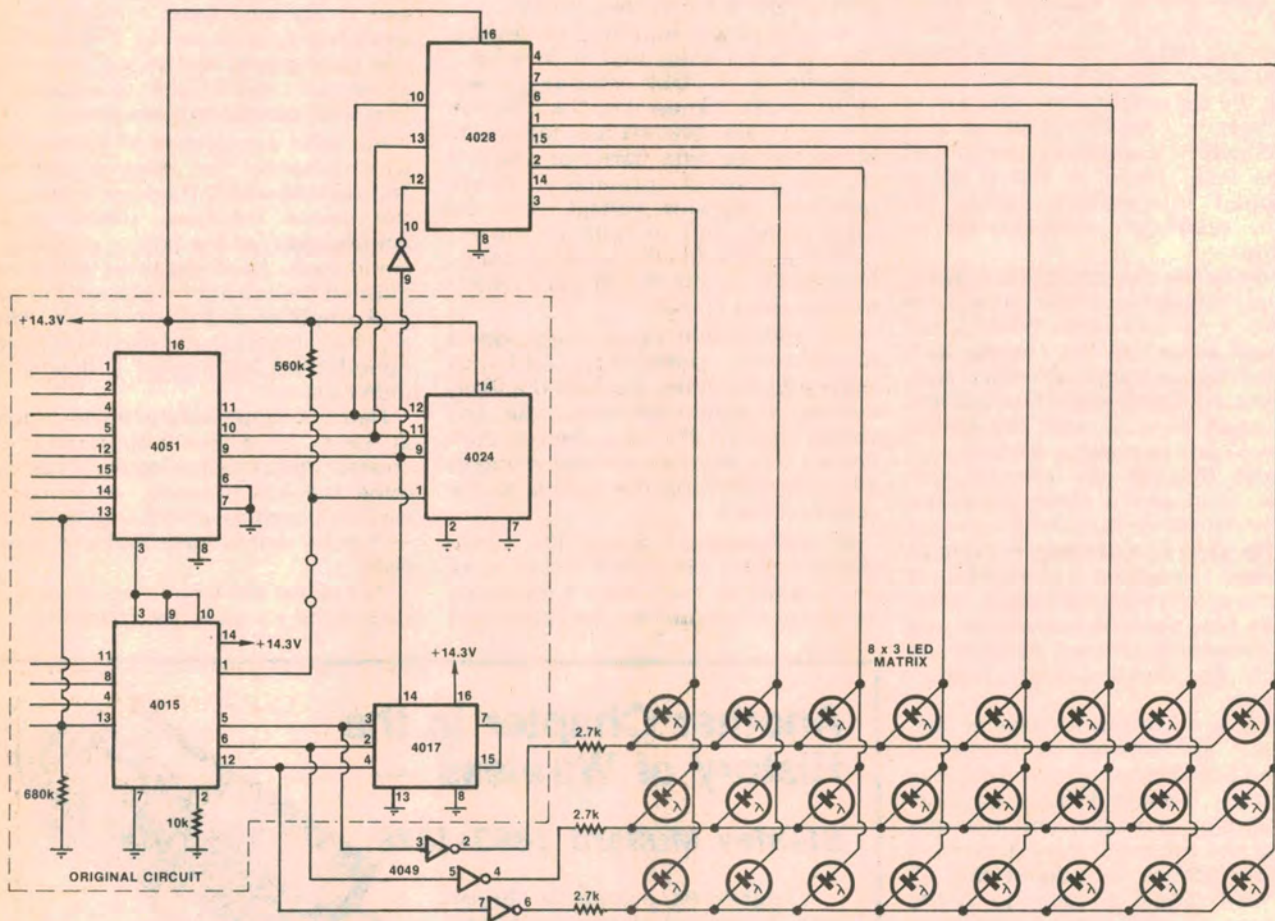


Auto-chime — which tune is next?



I have added some additional circuitry to the Auto-Chime which was described in September, 1979. The additions are arranged to give an indication as to which tune is to be played next. It is quite simple to add, I used a piece of Veroboard to carry the two extra ICs.

I chose LEDs for the indicators in preference to a 7-segment readout because I think that it has a better appearance and it is a simpler approach. I built the LEDs around a square box but they may be arranged as each individual constructor wishes. The repertoire list may also be added to the

LEDs and the next tune may then be read off.

The added circuitry has proved to be very satisfactory and it cost me about \$7.00, including the LEDs.

(By Mr R. Gareb, 17/37-39 O'Donnell Street, Bondi, NSW 2026.)