

# LED Roulette

January 2004, p. 52-55,

030168-1

The PCB has a short-circuit between the anode of D18 and the +5 V rail.

To lift the short-circuit, two tracks have to be cut and a wire link fitted, as shown in the illustration.

