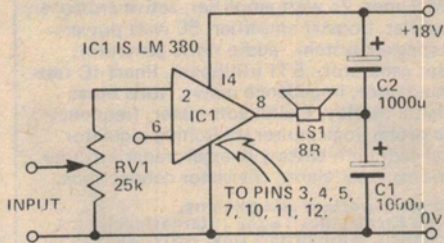


Novel loudspeaker coupling circuit

In most amplifier designs the speaker is fed by a high value capacitor to provide DC blocking, but this may result in a heavy switch-on surge, as the capacitor charges up.

An alternative approach, which is worthy of experiment, is shown in the diagram below. Here the ground side of the speaker is connected to the junction of two equal high value capacitors (1000 uF is typical), across the supply.

The amplifier output voltage will be at $V_s/2$, and so will the voltage across C_1 (if C_1 and C_2 are equal); so as the supply voltage builds up, the DC voltage



across the speaker will remain zero, eliminating the switch-on surge. C_1 and C_2 will also provide supply smoothing. The circuit is shown with the LM380, but could be applied to any amplifier circuit, providing that the DC voltage at the output is half the supply voltage.

Ideas for experimenters

Deaf Touch Switch


Many designs for touch controls suffer from the disadvantage of low noise immunity, and this circuit was designed seeking to rectify this vault.

AC voltage from, for example, the hand is applied to the gate of the FET buffer. The resultant positive signal is applied via the diode, to the input of IC1. This IC is made up from three triple gates connected in a Schmidt trigger configuration. At the threshold voltage, a positive pulse is fed to the clock input of IC2, a D-type flip-flop. Connection is made between Q and the

D input, so as to cause the flip-flop to run in the 'triggered' mode. Thus the input signals are divided by two and the output appears at the Q terminal.

In operation, a single positive pulse sets the Schmidt trigger to its low level. (Removal of the hand causes reversion to the 'high' state). This, in turn, feeds the clock input of IC2, which changes the state of the Q output. When this is high, the output stage is driven on, enabling current to flow in the external load and the current limiting resistor, R.

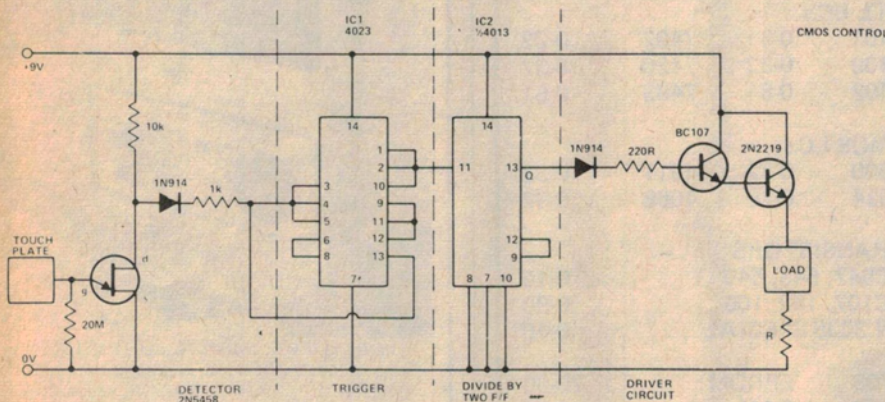A second positive pulse changes the state of Q to its low level, causing the output stage to be biased off.




Car Lights Reminder

Many circuits to warn motorists that they have left their headlights on after switching the engine off have appeared in the past. I feel this circuit is an improvement over many of these in that it requires no switches, and it is only necessary to make three connections to the car's electrical system.


If the ignition is switched off while the lights are on, an audible warning is sounded for about ten seconds. This tone is produced by NAND gates IC1/2, IC1/3 and IC1/4. Operation of this oscillator is inhibited by an '0' on the gating input of IC1/2. This in turn corresponds to a logic '1' present at the input to IC1/1 while the ignition switch is on, supplying a high logic level to IC1/1, the oscillator is thus disabled.

When the ignition is switched off, the output of IC1/1 goes high, enabling the oscillator. At this stage C2, which has until now been charged up via D1, begins to discharge via R4. While the voltage on C2 is high, the gating input of IC1/4 allows oscillator operation, however as C2 discharges, this action is inhibited. This occurs after about ten seconds.

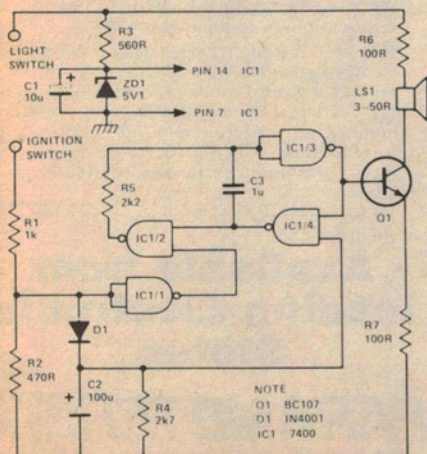Power for the circuit is provided by R3 and ZD1 from the vehicle's 12 V rail.



FRG -7 SYNTHESIZED RECEIVER

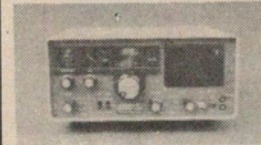

for amateurs,
novices
and
short-wave
listeners

Latest model includes fine-tune adjustment

MANUFACTURER'S TECHNICAL DATA

- Electronic band changing.
- 0.5-29.9 MHz continuous coverage.
- Uses Wadley loop (drift cancellation circuit) to derive synthesized heterodyne oscillator signal.
- LSB, USB, AM and CW.
- Frequency readout better than 10 KHz (readable to 5 KHz).
- Stability within 500 Hz during any 30-minute period after warm-up.
- Better than 0.7 V for 10 dB S N/SSB and CW. Better than 2 V for 10 dB S N/N AM.
- Selectivity 3 KHz at -6 dB, 7 KHz at -50 dB.
- Input Impedance high 0.5-1.6 MHz. 50-75 ohm 1.6-29.9 MHz.
- 234V AC 50-60 Hz or 12V DC (external or internal B dry cell).
- Size 340 mm x 153 mm x 285 mm.

• Price \$338.00

- Prices include S/tax, freight extra. Prices and Specs subject to change.

Explore the wonderful world of short-wave listening.

Hear broadcast stations, amateurs, ships, aircraft and Morse code from stations all over the globe.

Provides an introduction into many aspects of electronics and communications, CB'ers upgrade and widen your scope of operation. The FRG-7 will provide the means of listening to the amateur bands so that you can get the "feel" of amateur "ham" radio.

You can tune into the Morse practice transmissions and broadcasts conducted by the Wireless Institute of Australia; the Radio Amateurs representative Society in Australia.

Write for a descriptive brochure and ask for information on study procedures etc. for the novice amateur licence.

Remember, BAIL has been the authorised agent for the YAESU MUSEN CO LTD since 1963. Our experience gathered over these years, and a lifelong participation in electronics, places us in a superior position to handle warranty, after sales service and advice on the wide range of Yaesu amateur radio equipment.

Avoid unauthorised handlers of equipment as it generally results in the supply of non-export 110V sets with 2-core AC power cables, instruction manuals printed in Japanese, lack of service etc. Consult us for advice on your requirements in the field of short-wave listening and amateur radio.


For further information call or write to the Amateur radio specialists.

Australian agents since 1963

bail 60 Shannon St., Box Hill North
ELECTRONIC SERVICES Vic. 3129
Ph 89 2213


NESSEL LOUDSPEAKERS

PROFESSIONAL SERIES

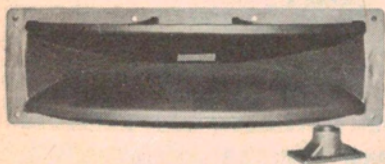

Rugged cast aluminium

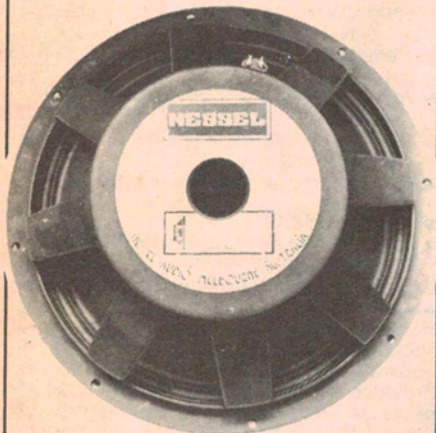27½" W x 7" High x 19" deep.
90° lip horn
Throat adaptors for screw-on
1 ⅜" and 1" entry.
500 c/s crossover



Range of speakers

Model:

SL1201: 12" 4" coil, 100W, Guitar Bass
PA, 8 kg, 80 c/s.
SL1502: 15" 4" coil, 150W, Guitar Bass
PA, 9 kg, 55 c/s.
SL1403: 15" 4" coil, 200W, Bass PA, 14
kg, 70 c/s.
SL1803: 18" 4" coil, 200W, Bass, 14 kg,
50 c/s.

TRADE ENQUIRIES WELCOME

Available from



NESSSEL AUDIO

9 Nellbern Rd,
Moorabbin East, Vic. 3189
Ph (03) 95 9510

EASTERN
ELECTRONIC
COMPONENTS
35 Mahoneys Road,
Forest Hill. 3131.
Telephone 878-7876.

A NEW SUPPLIER OF
ELECTRONIC COMPONENTS
IN THE EASTERN SUBURBS

HERE ARE A FEW EXAMPLES
OF OUR WIDE RANGE

LINEAR I.C.s

LM 555	0-40	LM 741	0-45
LM 301	0-45	LM 380	1-32
LM3900	0-80	7805	1-20

TTL I.C.s

7401	0-31	7402	0-32
7408	0-32	7420	0-32
7492	0-81	7493	0-81

CMOS I.C.s

4000	0-32	4011	0-32
4024	0-70	4068	0-32

TRANSISTORS

BC547, 548, 549	0-19
BC107, 108, 109	0-30
2N 3638 SPECIAL	0-10

2708	EPROM	20-00
2102	RAM	1-75
2513	ROM	19-80
93427	PROM	3-00
3850	F8 CPU	14-95
3853	F8 SMI	12-95

THIS MONTH'S SPECIALS

7400	0-16	4001	0-22
FND 357	7-SEGMENT		1-00
BC208	0-10	7815	0-80

OTHER ITEMS INCLUDE

RESISTORS ¼, ½, 1&5 Watt
CAPACITORS disc, electro, tags
and greencaps.
R.F. CHOKES 3.3µH – 800µH
SWITCHES and HARDWARE
MICROPROCESSORS including
6800, SC/MP, PACE, 2650,
F8, 6100.
CHARTPACK PCB ARTWORK
PRINTED CIRCUIT BOARDS for
ETI and EA projects.

All of the above prices include
sales tax.

Quantity discounts available
Mail orders catered for. Pack and
post 50 cents.

BK PRECISION

B&K 2810 is STILL
best buy in portable
3½ digit DMM's with
its .01Ω resolution,
RF shielding and
selectable Hi/Lo
Power Ohms ranges.



\$159.00
\$182.85 inc. S.T.

The B&K-PRECISION Model 2810 has
a combination of features uncommon in a
portable digital VOM. Basic DC accuracy is
0.5% with a 3½ digit display.
Auto zeroing on all but the 10Ω range
minimizes set-up time while the 100%
overranging capability reduces the need for
frequent range changes.

A highly valuable feature is the 10Ω range.
This range, with its .01Ω resolution, is ideal
for locating a shorted winding in a
transformer, motor or coil. For high
accuracy, a front panel 10Ω ZERO control
allows the user to zero-out the minute
amount of test lead resistance.

The low power ohms position permits
resistance measurements in solid-state
circuitry without biasing semiconductor
junctions.

Unlike many voltmeters, the 2810 can also
be used in R-F energy fields: Near business
band, CB and amateur radio transmitters.
When working with R-F circuitry, the
optional PR-21 probe is also helpful.

The 2810 is well protected against overloads
on all ranges. The ohms circuitry is
protected against momentary overloads up
to 1000 volts, DC or AC peak. Continuous
ohms range protection is ±100V and
-450VDC or 300VAC. Current ranges
receive the double protection of diodes and
a fuse.

If you only need 1% accuracy, save with
the B&K 2800.


Available from
leading Electronic
Stores

PARAMETERS PTY LTD

Sydney: 439 3288 Melbourne: 90 7444

Blob — Board for Digital Electronics by Experiment

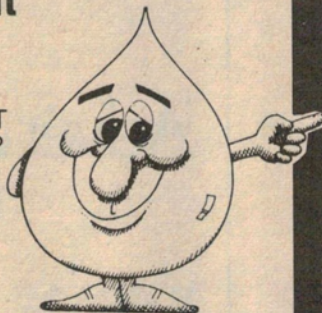YOUR NEAREST
BLOB DEALER?
THAT'S EASY.
WRITE TO:



BLOB BOARD ASSOCIATES

P.O. Box 23, SURREY HILLS,
VIC. 3127. or RING (03) 89-1019.


Mr. Blob says "The Technique of inserting components on one side of a board and soldering on the other is done for reasons which are now completely out of date; Namely this technique was established originally because heavy and bulky components were used. This no longer applies and has big disadvantages, the circuit is impossible to follow unless the board is continually turned over to inspect each side, its difficult to work on both sides of the board and soldering basically needs three hands. A common fault is to mount both leadout wires on the same tract.

Blob — Boards give you the modern, low cost, easy to build circuits. Blob — Boards are roller tinned circuit boards on which each roller tinned copper track is identified by the letter and or number system. Simply tin the end of the component, butt the component lead against the roller tinned track, apply a blob of solder and the component is blobbed into place. All construction is from one side, component location could not be simpler, soldering is much easier, sub-circuits can be tested, then assembled together, the plain side of the Blob-Board is free and so the Blob-Board can be mounted flush on case walls. And they can be re-used simply apply a soldering iron to the Blob and remove the component."

Now start Digital Electronics by Experiment.

No need to lose your way round a circuit board that needs a layout drawing — Blob-Boards make construction easy. Blob-Boards have numbered tracks that make layout drawing out of date, the tinning ensures easy soldering, and the tracks don't strip off when you unsolder components. Blobbing components on to the tracks (no holes, no drilling) makes layout easy to follow. Use the 8-IC board for 'Digital Electronics by Experiment' in this issue, but remember that we have "A Blob for every job".

FRONT PANEL DISPLAY

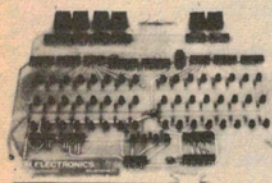

Designed for 8080 but will suit most systems. Input lines are 16 ADD. Lines, 8 Data lines, 2 x 8 Bit prog. output port, status Flags etc. All inputs buffered, flat cable interface. Also available as an option a HEX DISPLAY with 1/2" high 7 seg. Led display for Address & Data Bus. 4 displays for address bus and 2 displays for data bus. 10 x 8 ins board size.

STANDARD PANEL
KIT PRICE **\$75.00**


WITH HEX DISPLAY
KIT PRICE **\$105.00**

NUMBER CRUNCHER

MM57109 Number Cruncher. Buffered I/O will suit 8080, 6800, SCAMP, etc., will perform floating point and scientific calculations under software control. Full data and software support.

KIT PRICE **\$52.00** | BUILT AND TESTED **\$72.00**


PAPER TAPE READER

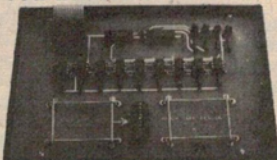

Manual operation, self contained in case 160X110X50. Flat cable interface to I/O port. Handshake logic, Status LEDs, Data & software supplied. Simple to use on all systems. 8080, 6800, etc.

KIT PRICE **\$75**

BACKPLANE BOARDS

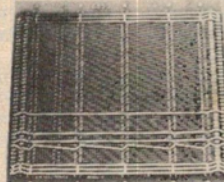

Quality fibreglass boards, 5 sockets per board with wide spacing, provision for linking boards together even different types, 8" x 8" 6800 board with wide centres, 12" x 6" 8080 board with provision for both sockets

PRICE **\$24.50**

GOLD PLATED SOCKETS

To suit 8080 & 6800 43 way double sided \$9.50 or 5/ \$45.00

Built & Tested Prices and Tax Free Prices on application.

S.M. ELECTRONICS 10 Stafford Crt, Doncaster East,
3109. Box 19, Doncaster East, 3109. (03) 842-3950 (03) 842-3950.

U.V. EPROM ERASER

Erase up to 4 eproms at once such as 2708 etc in 15/30 mins. 240V operation, small size, 3" x 4" x 8". Assembled and tested only

\$47.50

SINGLE STEP CONTROL for 8080

Push button single step mode. Auto. step low speed (Variable speed) mode, Interrupt facility. Run mode LED, will suit other systems, works off wait, & ready, lines. Panel mount.

KIT PRICE
\$23.00

ALL PARTS POST FREE

See adv. JAN 78 Elec. Aust. for digital tacho, stop watches, trans. Ign. system, burglar alarm etc.

FACT SYMPOSIUM

" FUTURE AMATEUR COMMUNICATIONS TECHNIQUES "

20 - 21 May. Venue: The Strata Motor Inn,
287 Military Rd CREMORNE

Organised by Roger Harrison VK2ZTB and the NSW VHF & TV Group, WIA.

This symposium will be of interest to the beginner and advanced amateur alike. It promises to be the amateur radio event of 1978. Papers will be presented covering the following topics:- SUNSPOT CYCLE 21' SOLID STATE POWER AMPLIFIERS, MICROPROCESSORS & AMATEUR APPLICATIONS, PULSE TECHNIQUES, MODERN REPEATER TECHNIQUES, SOLID STATE SSB ON 1296 MHZ, REVIEW OF ANTENNAS FOR UHF, ATV TECHNIQUES FOR 420 & 1290 MHZ, USING ANOMOLOUS PROPAGATION FOR HF/VHF DX.

There will be, in addition, a number of workshops associated with the papers demonstrating equipment using state of the art techniques. Papers and workshops will be presented by many well-known amateurs:- Les Jenkins VK3ZBJ, Ken MacCracken VK2CAX, Peter Cossins VK3BFG Jeff Pages VK2BYY, Roger Harrison VK2ZTB, Phil Wait VK2ZZQ, Les Bell GM4CFM.

For further information, registration forms etc, contact:
THE FACT SYMPOSIUM ORGANISER
C/- WIA, 14 ATCHISON ST
CROWS NEST 2065 NSW

or see page 85 this issue.

SPEEDY, EFFICIENT



Service for CB Radio

FULLY EQUIPPED
WORKSHOP.

FULL RANGE OF SPARES FOR
DICK SMITH AND MIDLAND
CB RADIOS — AS WELL AS
MOST OTHER BRANDS.

DICK SMITH SERVICE DEPT.
5/4 Carlotta Street. Artarmon.
(entrance in Clarendon Street.)
Telephone: 439 5164.

READERS' LETTERS

No charge for replies but a foolscap-size stamped addressed envelope must be enclosed. Project queries can only be answered if related to item as published. We cannot assist if project is modified nor if components are otherwise than specified. We regret we cannot answer readers' enquiries by telephone.

SUBSCRIPTIONS AND BACK ISSUES

ETI subscriptions cost \$17.00 per year (inc. postage) within Australia. Cost elsewhere is \$17.65 (inc. postage — surface mail). Airmail rates on application.

Back issues cost \$1.25 (Sept. onwards) each plus post and packing.

We can supply only the following issues.

1976: Nov., Dec.

1977: All issues except Jan, Feb, March.

Photostats are available of any article ever published in ETI. We charge a flat \$1.00 regardless of page quantity from any one issue of ETI. Thus if the article is in three issues the cost is \$3.00. Send orders to address below.

Binders \$4.50 plus 80c post NSW, \$1.70 other States.

COPYRIGHT

The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

LIABILITY

Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available, no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any component parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

A MODERN MAGAZINES PUBLICATION

Managing Director: Arnold Quick
Secretary: Charles O'Leary
Publisher: Collyn Rivers

PRODUCTION

Art Director: Jim Hattersley
Assembly: Bill Crump
Production Manager: Bob Izzard
Subscriptions & Circulation: John Oxenford
Project Design: Nebula Electronics
Acoustical Consultants: Louis A Challis & Assoc.

ADVERTISING

Sydney:	Bob Taylor (Manager), Geoff Petschler (NSW Manager), 15 Boundary St, Rushcutters Bay 2011. Tel: 33-4282.	Perth:	Aubrey Barker, 133 St. George's Terrace, Perth. 6000. Tel: 322 3184.
Melbourne:	Tom Bray (Manager), Poppe Davis, Suite 24, 553 St. Kilda Rd, Melbourne. Tel: 51-9836.	Hobart:	H.W. Lincolne Advance Publicity, 281 Elizabeth St, North Hobart, 7000.
Brisbane:	Geoff Horne, 199 Jesmond Rd, Indooroopilly, Brisbane, 4068. Tel: 378-3273.	Tokyo:	Genzo Uchida, Bancho Media Service, 15 Sanyecho, Shintuku-Ku, Tokyo 160.
Adelaide:	Ad Media Group of SA, 37 Fullarton Rd, Kent Town 5067. Tel: 42-4858.	London:	Electronics Today International, 25-27 Oxford St, London, W1R 1RF. Tel: 01-434-1781/2.

Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St., Rushcutters Bay NSW 2011. It is printed (in 1978) by Wilke & Co., Browns Rd, Clayton, Victoria and distributed by Australian Consolidated Press.

Advertisers: Index:

Applied Technology	38-39
Areana Distributors	27
A & R Sonar	66
Audio Telex	99
Auditec	100
Automation Statham	50
Bail Electronics	103
Blob-Board Associates	105
Cema	54
Chan Merchandising	42
Communications Devices	8
Convoy	24
Davred Electronics	68
Delsound	42
Dick Smith	60-61, 92, 105
Diggerman	29
Director of Recruiting	74
Eastern Electronic Components	104
Electrocraft	95
Electronic Concepts	44
Electronic Disposals	53
Ellistrions	107
Elmeasco Instruments	37
Emac	66
Emona	31
Ferguson Transformers	101
Freedman	12
Futuretronics	6
Haco	108
Hagemeyer	2
Harman	22
I. C.'s Unlimited	47
Instant Component Service	84, 85
International Components	91
International Correspondence Schools	67
International Electronics Unlimited	98
Impact	50
IRH Components	43
Jaycar	29
JR Components	76
Leroya	72
Madjenk	66
Nessel Audio	104
Nomis Electronics	30
Non-Linear Systems	100
Parameters	104
PDK Hi-Fi	76
Philips Elcoma	11
Photo Scan Distributors	30
Pioneer	20-21
Pre-Pak Electronics	10
Quest Electronics	102
Rave	91
Roadrunner	76
Rod Irving Electronics	73
Scalar Industries	52
Semcon Microcomputers	52
SM Electronics	105
Texas Instruments	59
Unique Electronic Security	102

**ELECTRONICS
ENTHUSIASTS**

Melbourne's
newest


ELECTRONICS SUPERMARKET

is

NOW OPEN

JUST THREE DOORS WEST OF ELIZABETH STREET

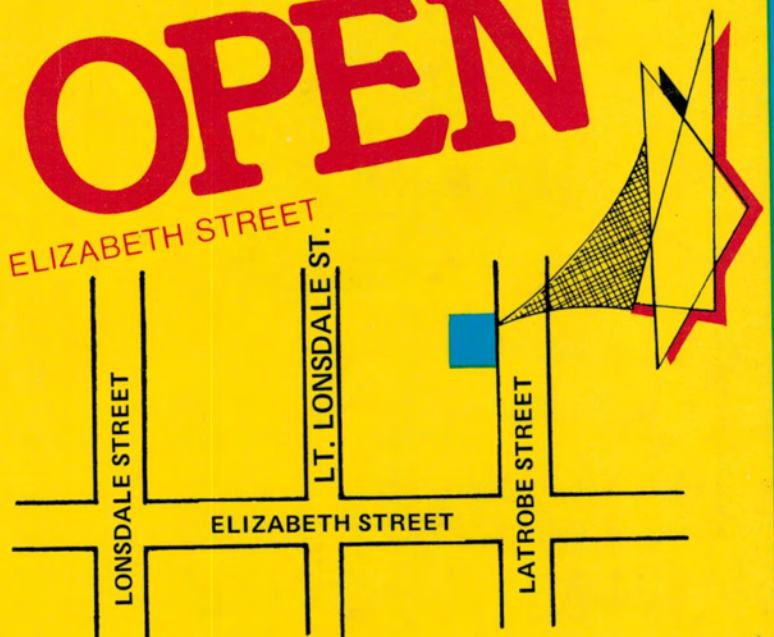Centrally located in the city, this is the only place to choose your project equipment in bright, colour co-ordinated surroundings



PRODUCTS AVAILABLE AS LISTED:

Semi-conductors, potentiometers, resistors, capacitors, aluminium and plastic project boxes. Project kit boards, amateur and CB radio plus accessories. Test equipment, vero board, transformers, knobs, wire, radio/TV antennae, speakers, turntables. In fact just about everything electronic.

CALL IN AND CHECK OUR LOW LOW PRICES

ELLISTRONICS

MAIL ORDERS
AVAILABLE TOO

289 LATROBE STREET, MELBOURNE. Ph (03) 602-3282.


ST-9030

SU-9070

SH-9010

SH-9020

SE-9060

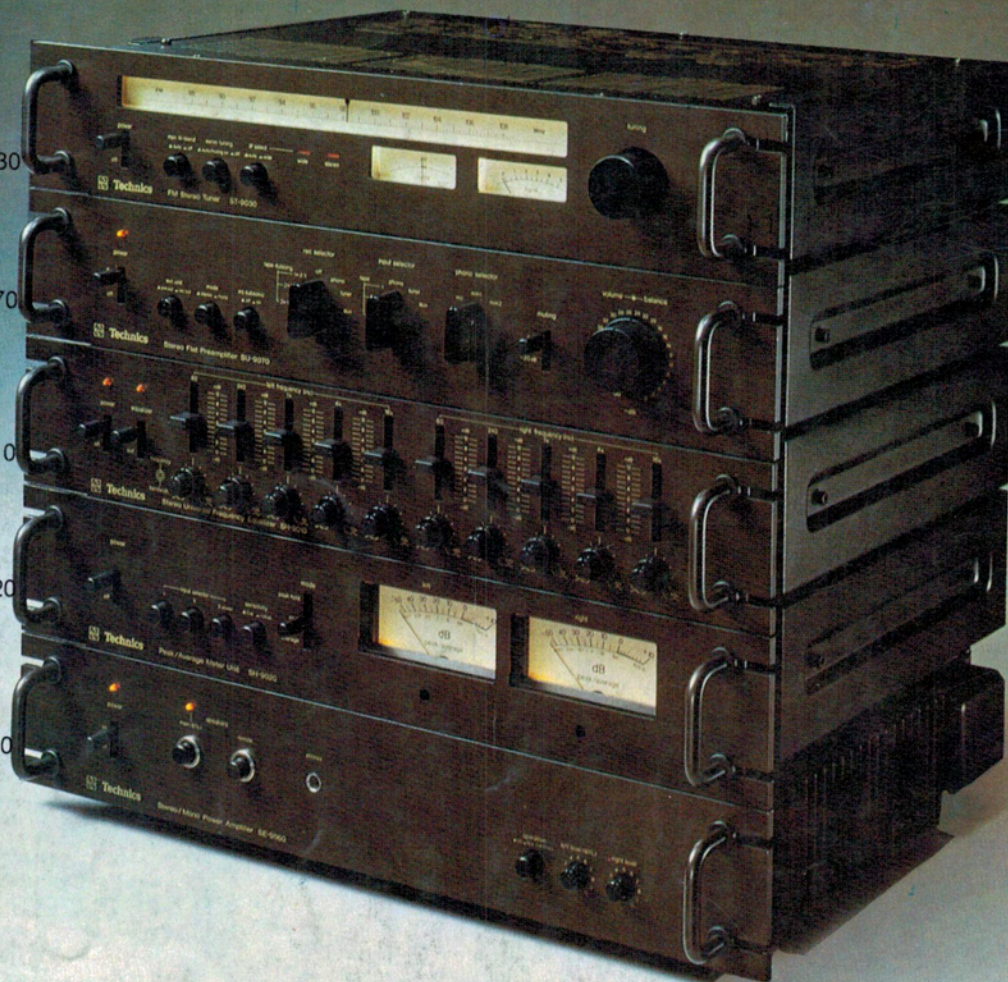

**Technics DC
'Flat Series'
Components
literally made
for each
other.**

In creating the 'flat' system, Technics engineers separated the basic amplifier / tuner into five components, researched and developed each, then recombined them into a system of audio excellence.

The system consists of: Stereo Tuner (ST-9030) with wide and narrow IF bands.

Stereo DC Preamp. (SU-9070) with phono signal-to-noise ratio of 88dB (for 2.5 mV input).

Stereo Universal Frequency Equaliser (SH-9010) for exact response control in any acoustic environment.

Peak / Average Meter Unit

(SH-9020) for exact response measurement.

Stereo/Mono DC Power Amplifier (SE-9060) with all-stage direct-coupled pure complementary symmetry circuitry. Total harmonic distortion is 0.02%.

Each individual component offers a degree of fidelity in sound reproduction, and a flexibility and ease of operation that makes it a natural choice for the audio fan who cannot be content with less than the best.

 **Technics**
hi-fi

